



EEE 3101: Digital Logic and Circuits

Magnitude Comparator

Course Teacher: Nafiz Ahmed Chisty

**Associate Professor, Department of EEE & CoE
Head (UG), Department of EEE
Faculty of Engineering
Room# DNG03, Ground Floor, D Building
Email: chisty@aiub.edu
Website: <http://engg.aiub.edu/>
Website: www.nachisty.com**



The Digital Comparator

Another common and very useful combinational logic circuit is that of the **Digital Comparator** circuit. Digital or Binary Comparators are made up from standard AND, OR and NOT gates that compare the digital signals present at their input terminals and produce an output depending upon the condition of those inputs.


There are two main types of Digital Comparator available, and these are.

1. **Identity Comparator** – an *Identity Comparator* is a digital comparator that has only one output terminal for when $A = B$ either “HIGH” $A = B = 1$ or “LOW” $A = B = 0$
2. **Magnitude Comparator** – a *Magnitude Comparator* is a type of digital comparator that has three output terminals:

$$A > B, A = B, A < B$$

Which means: A is greater than B, A is equal to B, and A is less than B

1-bit Digital Magnitude Comparator

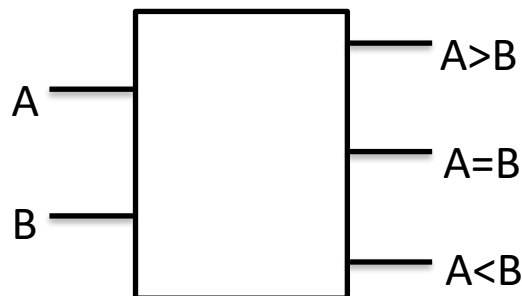

Truth Table:

Inputs		Outputs		
A	B	A < B	A = B	A > B
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0


Logic Expression:

$$(A=B) = A'B' + AB = (A \odot B) = X$$

$$(A > B) = AB'$$

$$(A < B) = A'B$$

Logic Diagram:

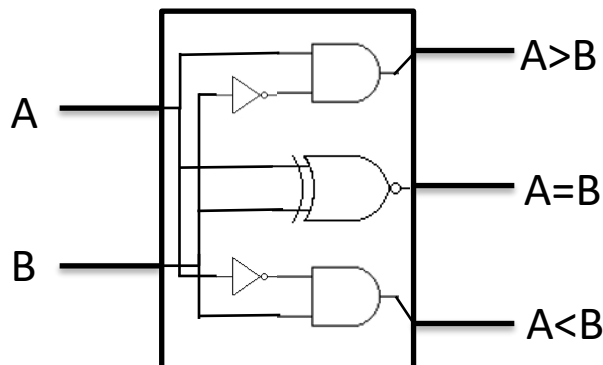

2-bit Digital Magnitude Comparator

$$A = A_1 A_0$$

$$B = B_1 B_0$$

Logic Expression:


$$X_n = A_n B_n + A_n' B_n'$$

$$(A=B) = X_1 X_0$$

$$(A>B) = A_1 B_1' + X_1 A_0 B_0'$$

$$(A<B) = A_1' B_1 + X_1 A_0' B_0$$

Block Diagram:

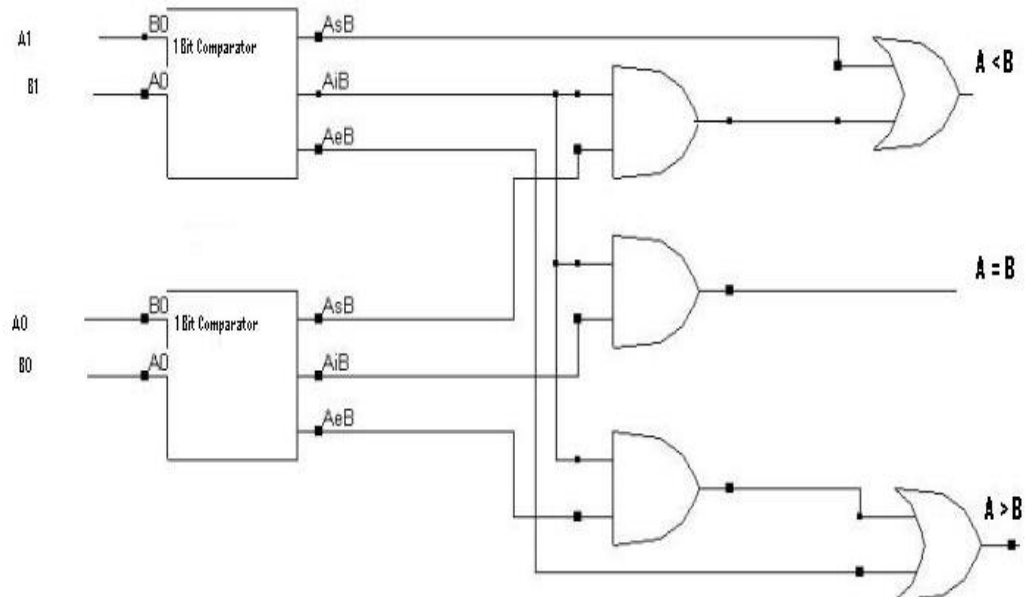

3-bit Digital Magnitude Comparator

$$A = A_2 A_1 A_0$$

$$B = B_2 B_1 B_0$$

Logic Expression:


$$X_n = A_n B_n + A_n' B_n'$$

$$(A=B) = X_2 X_1 X_0$$

$$(A>B) = A_2 B_2' + X_2 A_1 B_1' + X_2 X_1 A_0 B_0'$$

$$(A<B) = A_2' B_2 + X_2 A_1' B_1 + X_2 X_1 A_0' B_0$$

Block Diagram:

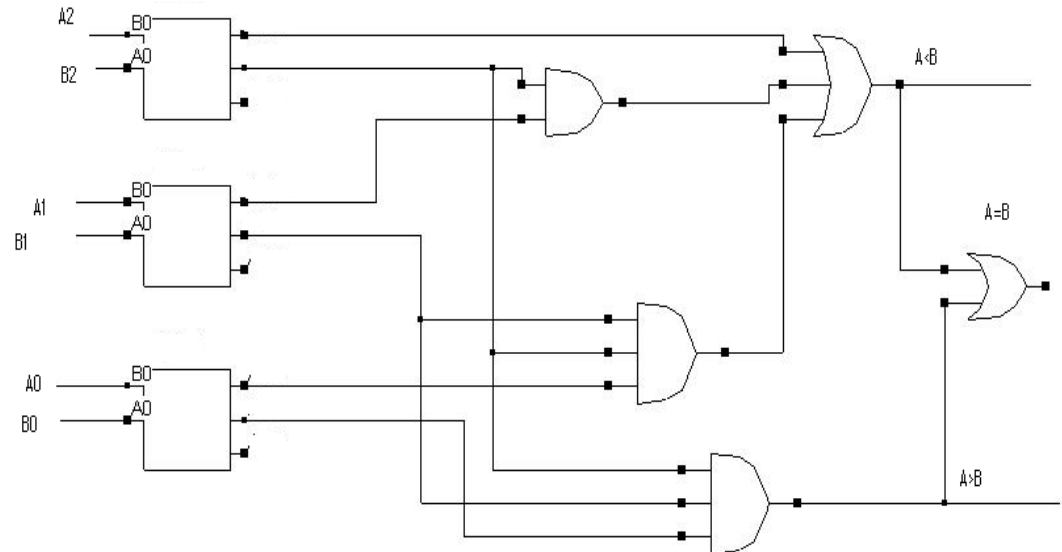

5-bit Digital Magnitude Comparator

$$A = A_4 A_3 A_2 A_1 A_0$$

$$B = B_4 B_3 B_2 B_1 B_0$$

Logic Expression:


$$X_n = A_n B_n + A_n' B_n'$$

$$(A=B) = X_4 X_3 X_2 X_1 X_0$$

$$(A>B) = A_4 B_4' + X_4 A_3 B_3' + X_4 X_3 A_2 B_2' + X_4 X_3 X_2 A_1 B_1' + X_4 X_3 X_2 X_1 A_0 B_0'$$

$$(A<B) = A_4' B_4 + X_4 A_3' B_3 + X_4 X_3 A_2' B_2 + X_4 X_3 X_2 A_1' B_1 + X_4 X_3 X_2 X_1 A_0' B_0$$

Block Diagram:

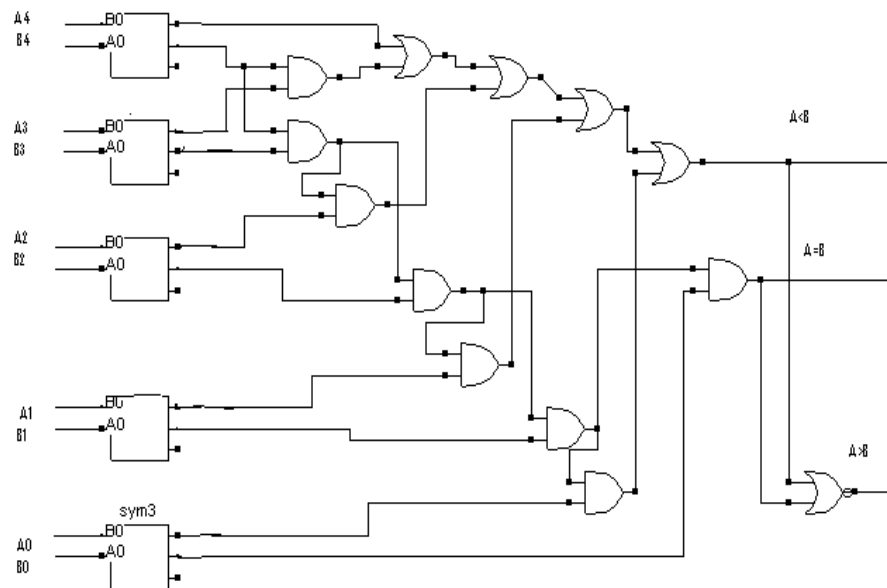

Reference:

- [1] Thomas L. Floyd, “Digital Fundamentals” 11th edition, Prentice Hall.
- [2] M. Morris Mano, “Digital Logic & Computer Design” Prentice Hall.



Thanks

