



AMERICAN INTERNATIONAL UNIVERSITY–BANGLADESH (AIUB)
FACULTY OF SCIENCE & TECHNOLOGY

DIGITAL LOGIC AND CIRCUITS LAB

Summer 2022-2023

Section: F
Group Number: 02

EXPERIMENT NO. 3

NAME OF THE EXPERIMENT

Design of adder, subtractor and comparator circuits.

Supervised By

SHAHRIYAR MASUD RIZVI
Faculty of Engineering, AIUB

Submitted By:

Name of the Student	ID Number
1. NOKIBUL ARFIN SIAM	21-44793-1
2. AHNAF AHMED	20-42173-1
3. SAIFUL ISLAM	20-42585-1
4. MAHADI HASAN	19-39711-1
5. SHEIKH FAHIM FUAD	21-44721-1

Abstract:

The purpose of this experiment is to learn the design and behavior of adder, subtractor and comparator logic circuits. Adders and subtractors are the most basic and most important part of digital electronics.

Part I (Adder):

Adders are digital circuits which are capable of adding binary digits. They are the most important part in the design of Arithmetic Logic Unit (ALU). In this experiment different types of adders will be designed and their behavior will be observed.

Theory and Methodology:

An adder or summer is a combinational circuit that adds binary numbers. There are mainly two kinds of adders, half adder and full adder. The half adder can add only two single bits of binary digit and outputs the sum of the bits and a carry which is the overflow of the sum. A full adder can add two single bit digits and one carry bit which is the overflow of the sum of the previous stage of addition and outputs the sum and the carry.

 


Fig.1.1: Schematics of Half Adder and Full Adder

Half adder–

$$S = A \oplus B$$

$$C_{out} = AB$$

Full adder –

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = C_{in} (A \oplus B) + AB$$

Truth table for half adder –

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Truth table for full adder –

A	B	Cin	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Using Full Adder blocks for the addition of n- bit systems:

Full adder blocks can be connected for the summation of n-bit systems. To design a 2-bit full adder, two 1-bit full adders are connected in parallel, as shown in the figure below. The exact process can be used for designing n-bit Full Adder for adding words with a length of n-bits.

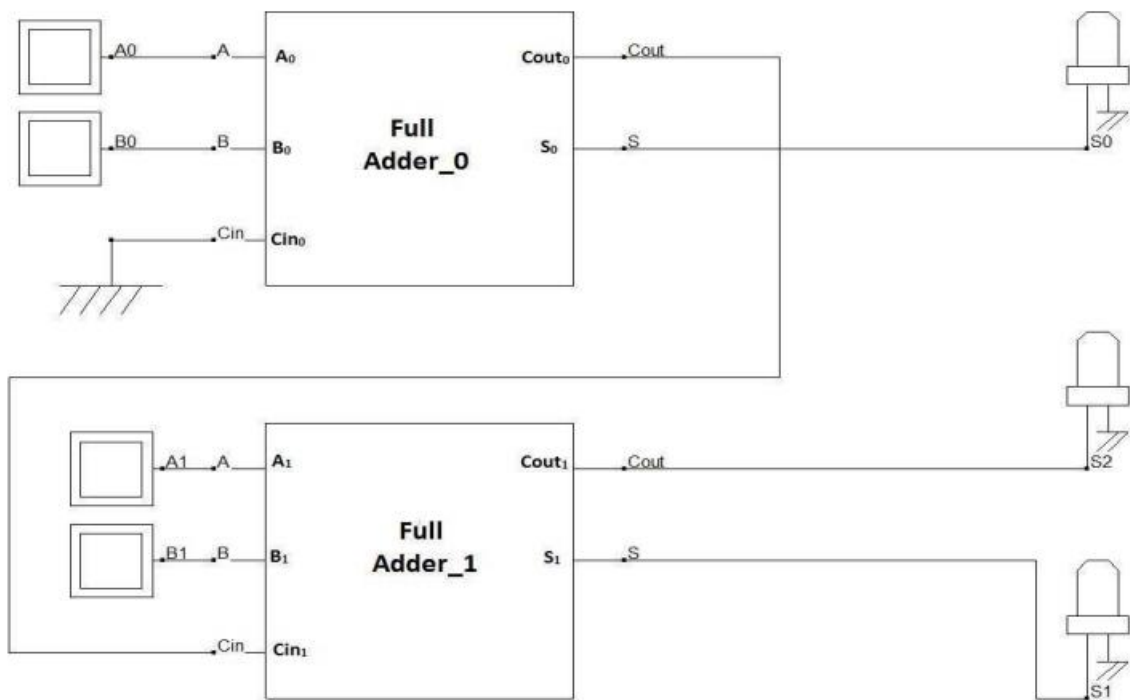


Fig. 1.3: 2-bit Full adder design using 1-bit full adder blocks

Here, the LSB of both words A and B (A₀ and B₀) are connected in the first stage full adder block, and Cin of this block (Cin₀) is connected to ground (as there is no carry-in available at the initial stage). The MSB of both words A and B (A₁ and B₁) are connected in the first stage full adder block, and Cin of this block (Cin₁) is connected to the previous stage Cout (Cout₀). Summation output for the LSB is available from the first stage, Sum (S₀). The next stage block outputs Sum (S₁) and carry out (Cout₁) provide the MSBs for the following stage output (S₁ and S₂).

Part II (Comparator): A magnitude comparator is a device that takes in two sets of inputs in its input and compares them to provide an output if they are equal, greater than, or less than the other. In this experiment, a 1-bit comparator will be designed first and using the 1-bit comparator block, a 2-bit comparator will be designed.

Theory and Methodology: Magnitude Comparators are combinational logic circuits that take two sets of data as their inputs and test whether the value represented by one binary word is more significant than, less than, or equal to the value represented by another word.

 


Fig.2.1: Block Diagram of 1-Bit Magnitude Comparator

Depending on the input combination for a 1-bit magnitude comparator, the following behavior table can be developed using the logic expressions.

A=B if A=B=0 or A=B=1;

A>B if A=1 and B=0;

A<B if A=0 and B=1;

A	B	A=B	A>B	A<B
0	0	1	0	0
0	1	0	0	1
1	0	0	1	0
1	1	1	0	0

The SOP expressions for the output lines can be written as

$$(A=B) = +A'B' + AB;$$

$$(A<B) = AB';$$

$$(A>B) = A'B;$$

 


Fig.2.2: 1-Bit Comparator



Fig.2.3: Timing Diagram for 1-BitComparator

2-Bit Comparator design using bit block:

Using 1-bit blocks, an n-bit Magnitude comparator can be designed.

 


Fig.2.4: 1-Bit
Comparator Block

Designing a 2-bit comparator using 1-bit blocks:

Let us consider two words,

Word A $\rightarrow A_1A_0$

Word B $\rightarrow B_1B_0$

For comparison, the following process is used for writing the logic equations.

For A=B,

If $(A_1=B_1) \& (A_0=B_0)$, then $(A=B)$;

For A>B,

If $(A_1>B_1)$ then $(A>B)$ or

if $(A_1=B_1) \& (A_0>B_0)$, then $(A>B)$;

For A<B,

If $(A_1<B_1)$ then $(A<B)$ or

if $(A_1=B_1) \& (A_0<B_0)$, then $(A<B)$

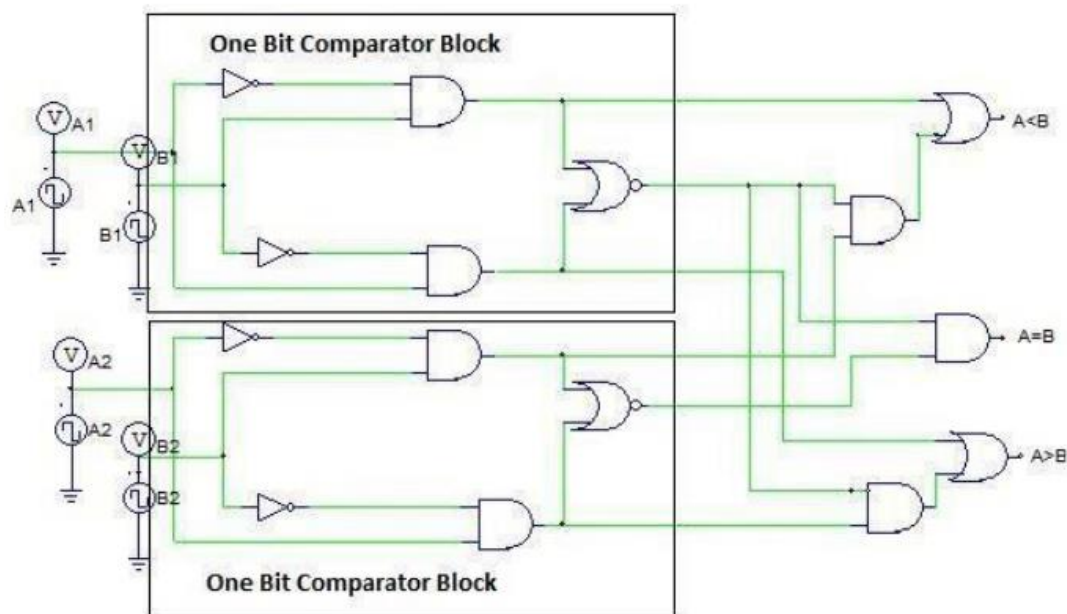




Fig.2.5: 2-Bit Comparator using 1_bit Comparator Block



For designing a 2-bit comparator using a 1-bit comparator block, two 1-bit comparator blocks, 3 AND gates, and 2 OR gates are needed, as shown in Fig.4.



Apparatus:


1. Digital trainer board
2. IC 7408:2pcs
3. IC 7404:2pcs
4. IC 7486:2pcs
5. IC 7431:2pcs
6. IC 7483:1pcs
7. Connecting wires

Hardware Implementation:

  

  

  




 










Simulation:


2-Bit Full Adder using 1-Bit Full Adder:

Truth Table

A_1	A_0	B_1	B_0	C_{out}	S_1	S_0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

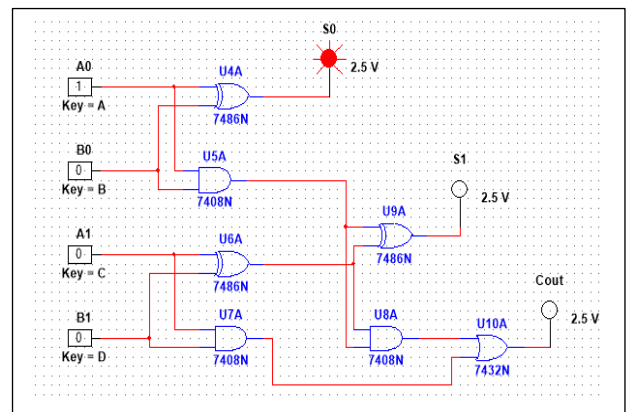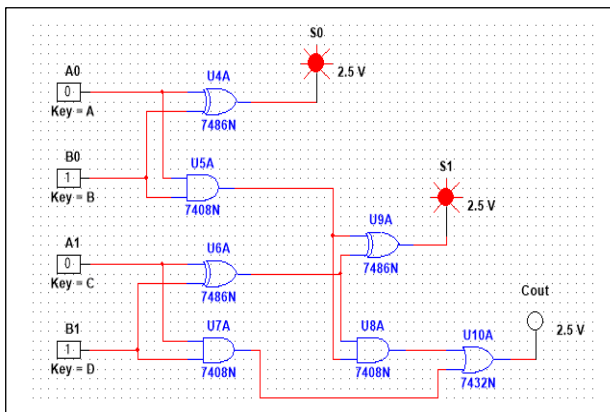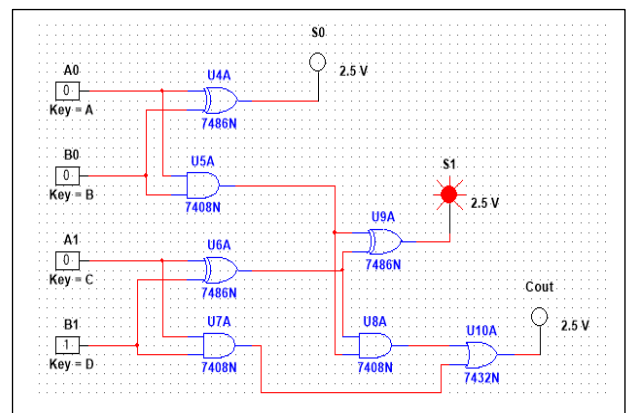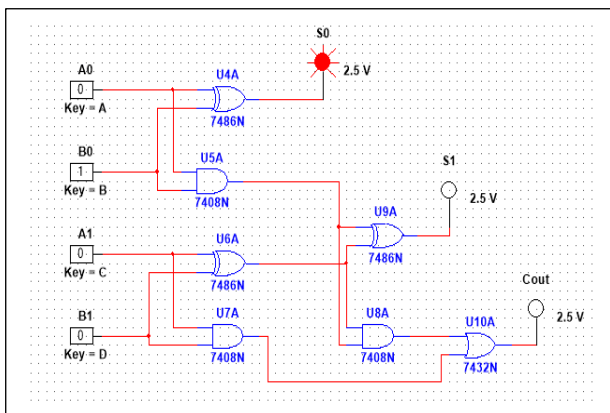

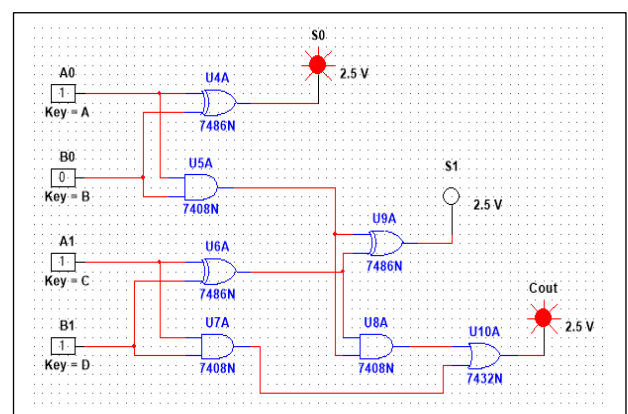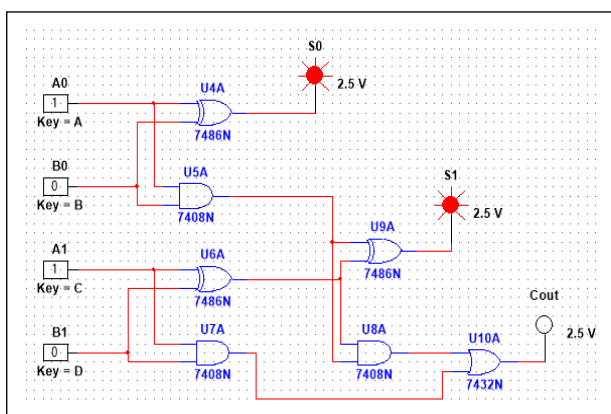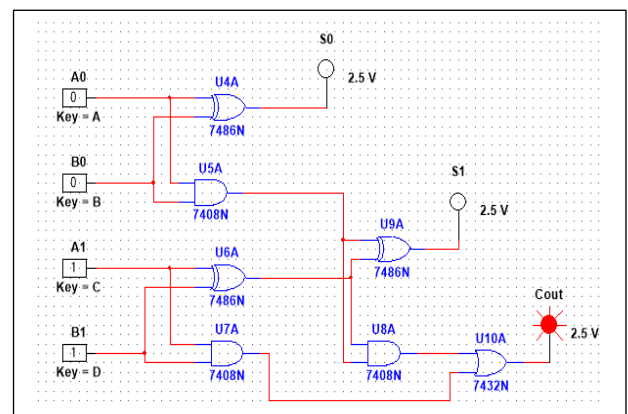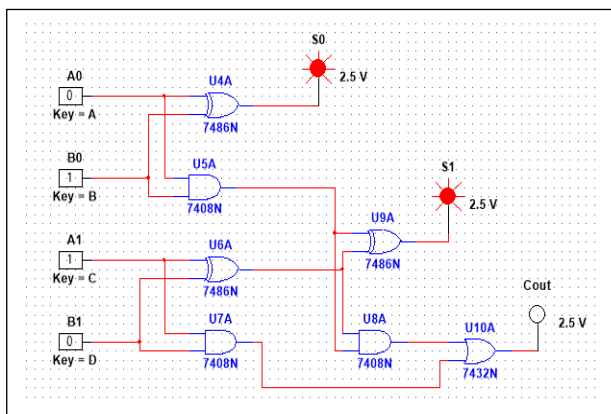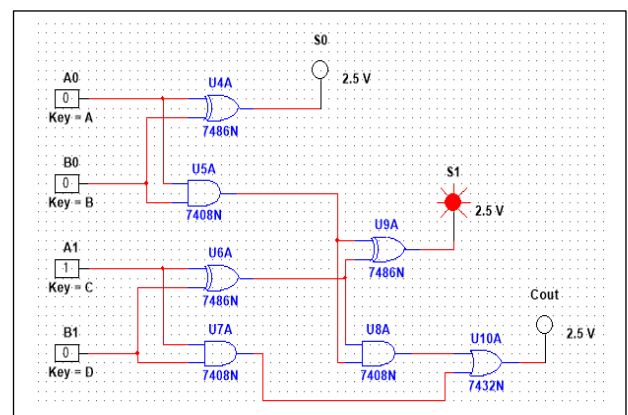
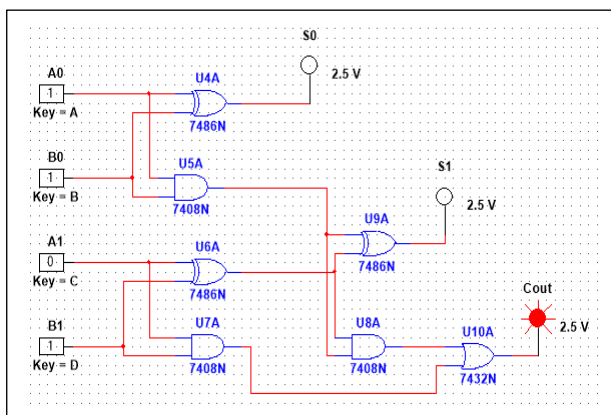
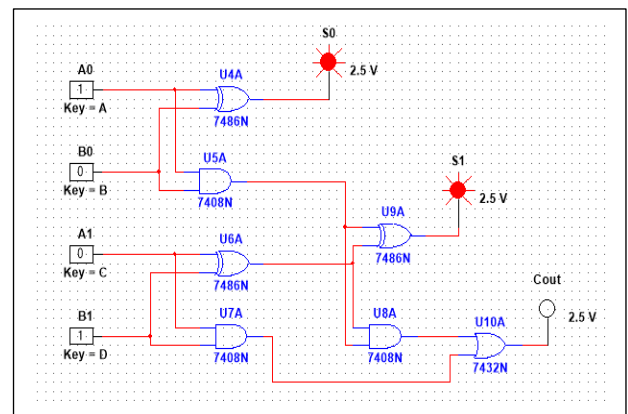
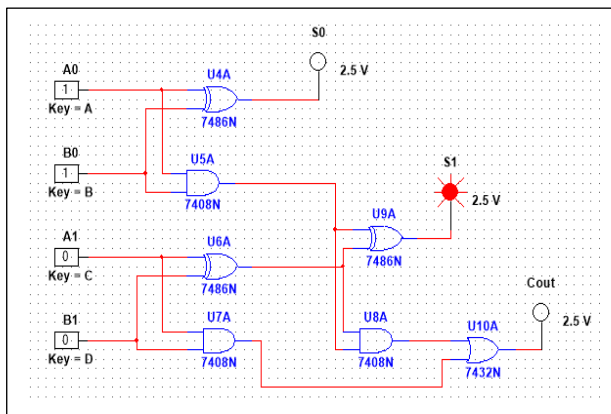


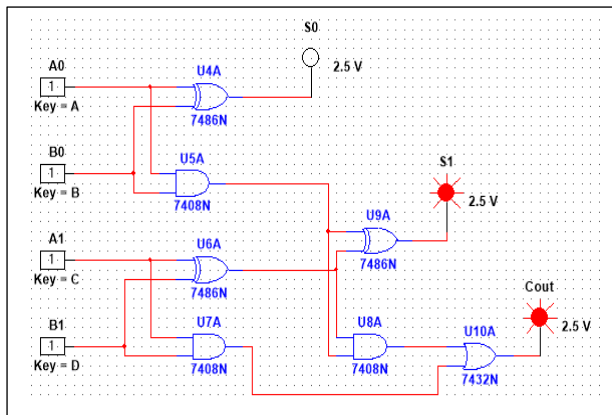

1-Bit Comparator:

Truth Table


A	B	A=B	A>B	A<B
0	0	1	0	0
0	1	0	0	1
1	0	0	1	0
1	1	1	0	0

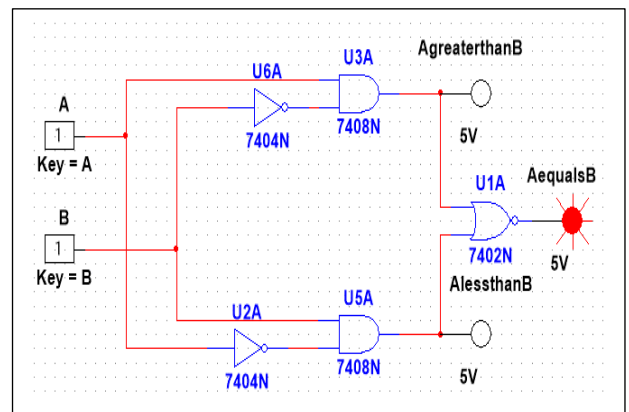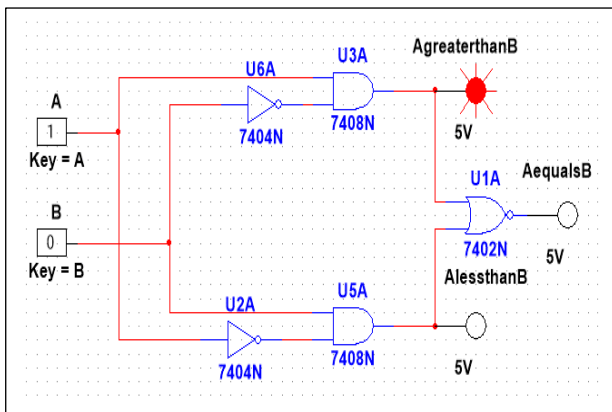
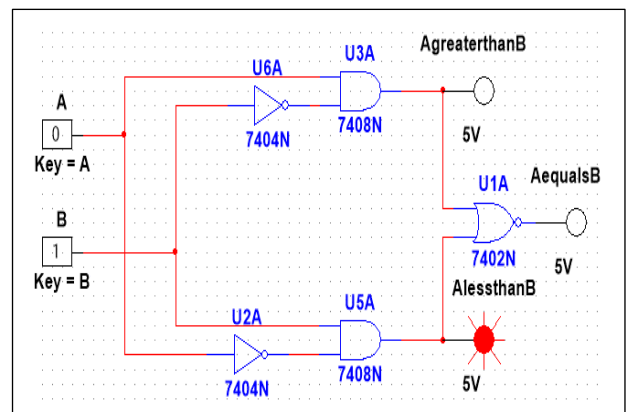
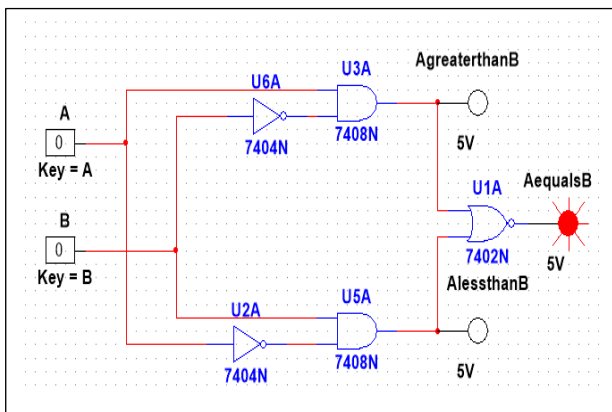





2-Bit Comparator Using 1-Bit Comparator:




Truth Table




INPUTS				OUTPUTS		
A1	A0	B1	B0	A=B	A>B	A<B
0	0	0	0	1	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	1	0	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	1	0
1	0	0	1	0	1	0
1	0	1	0	1	0	0
1	0	1	1	0	0	1
1	1	0	0	0	1	0
1	1	0	1	0	1	0
1	1	1	0	0	1	0
1	1	1	1	1	0	0



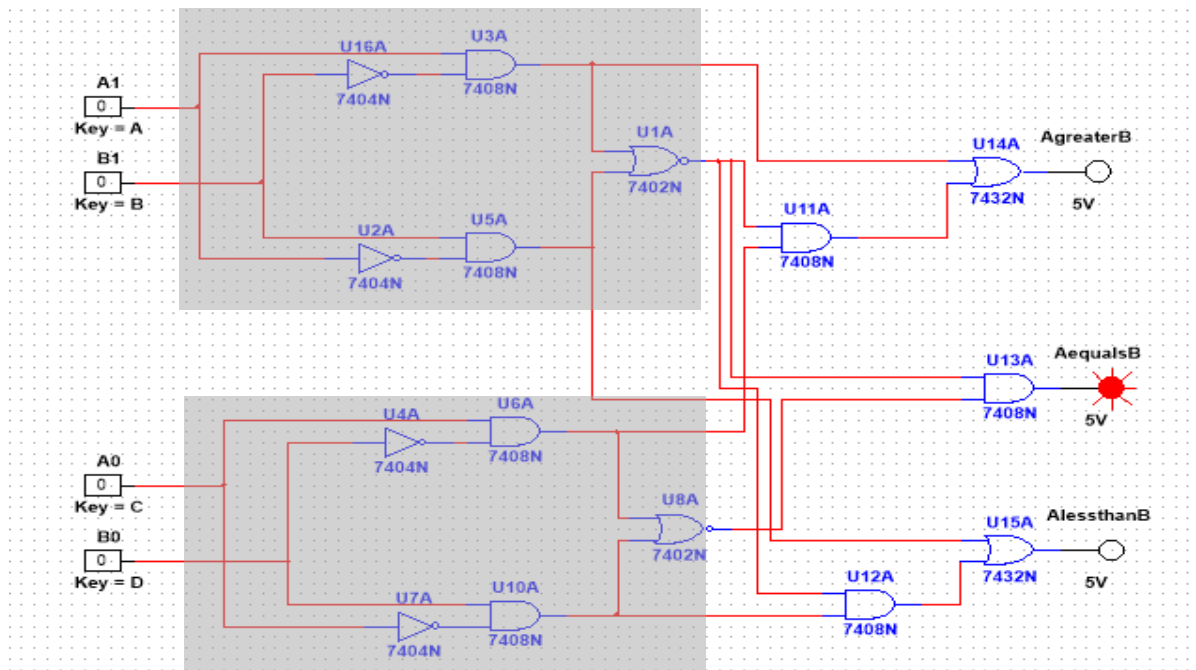


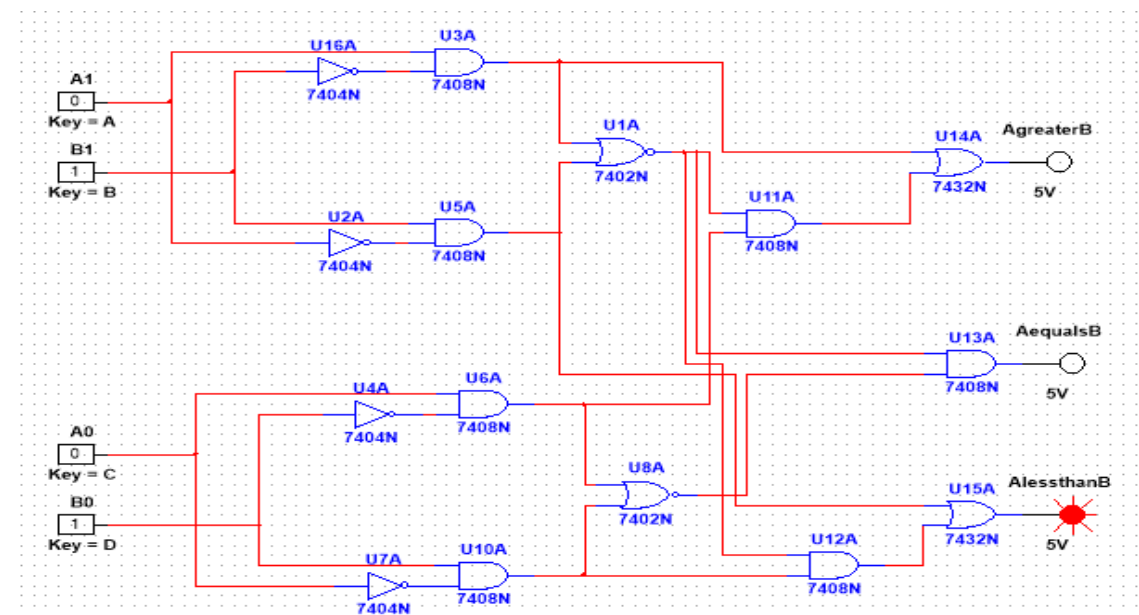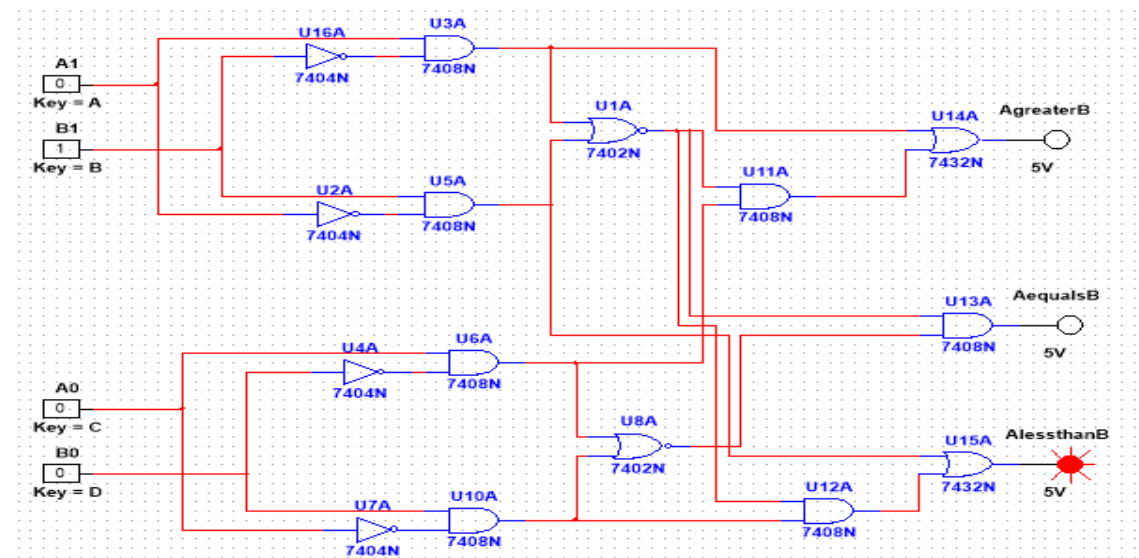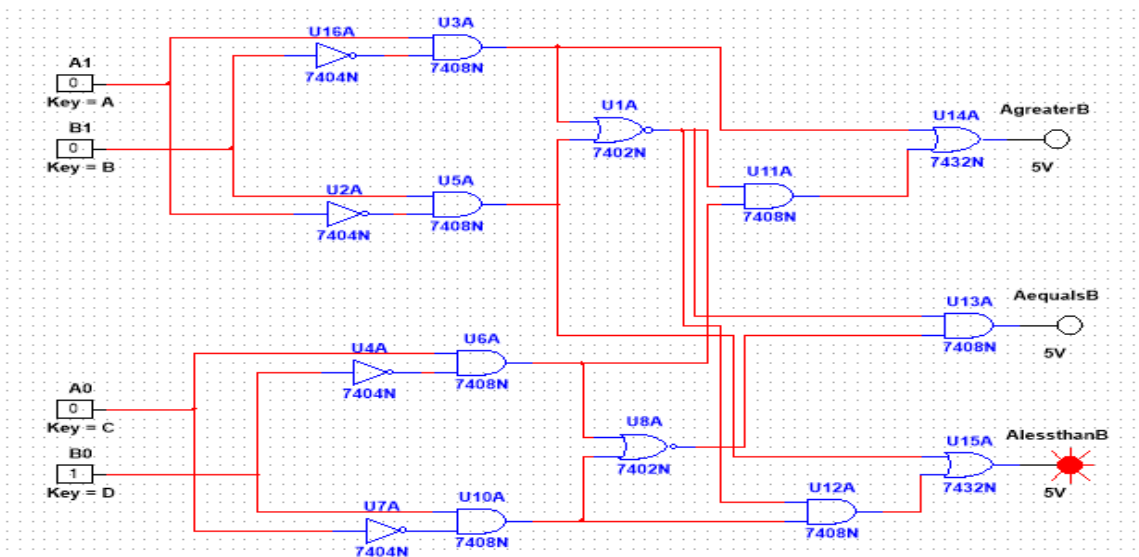

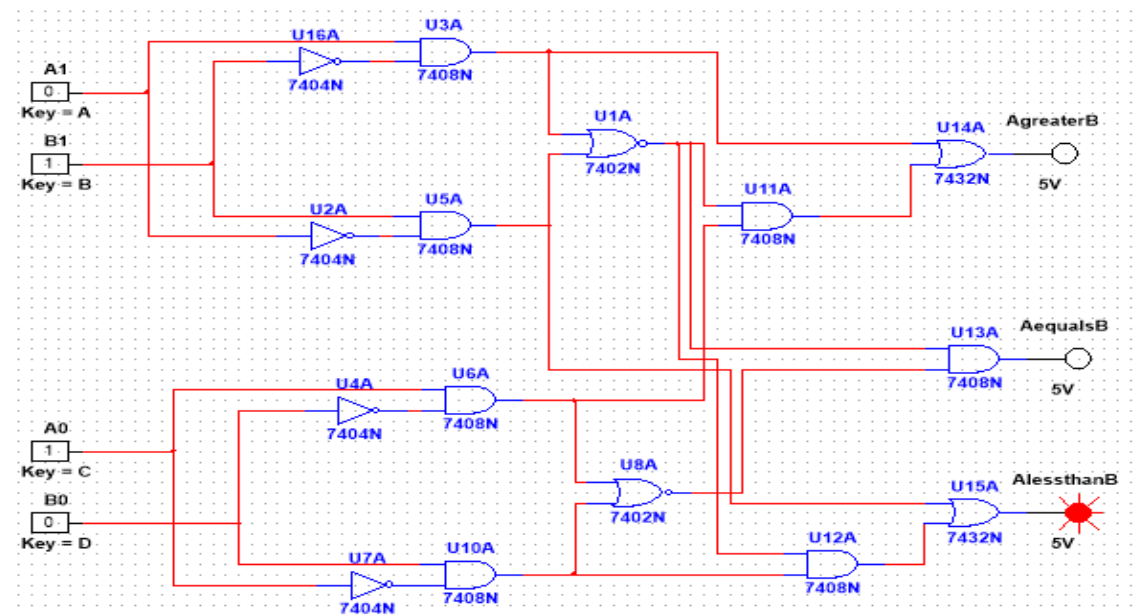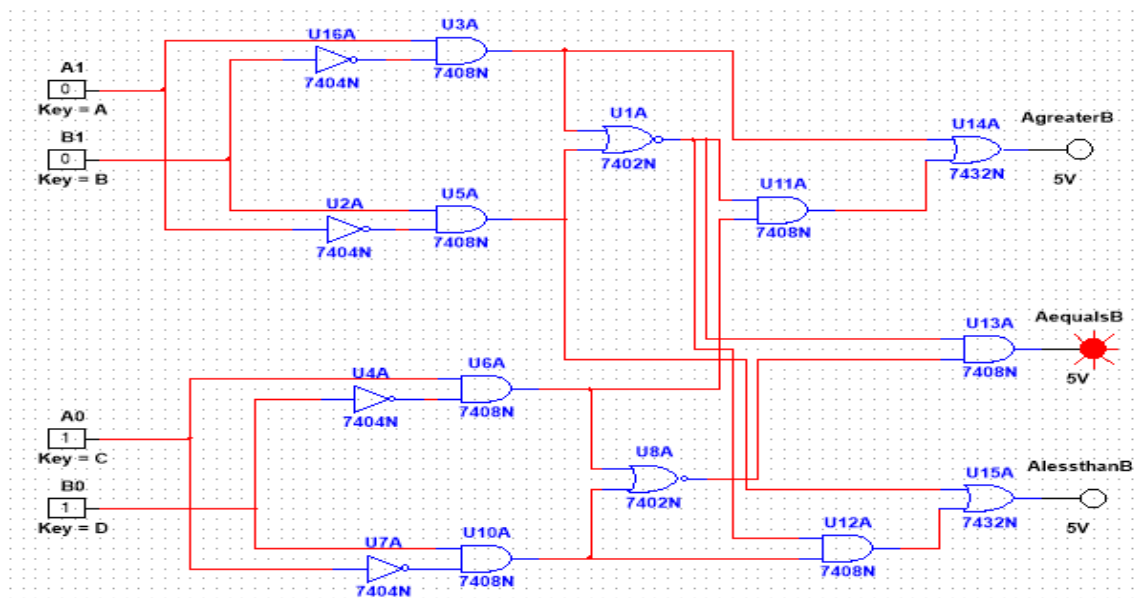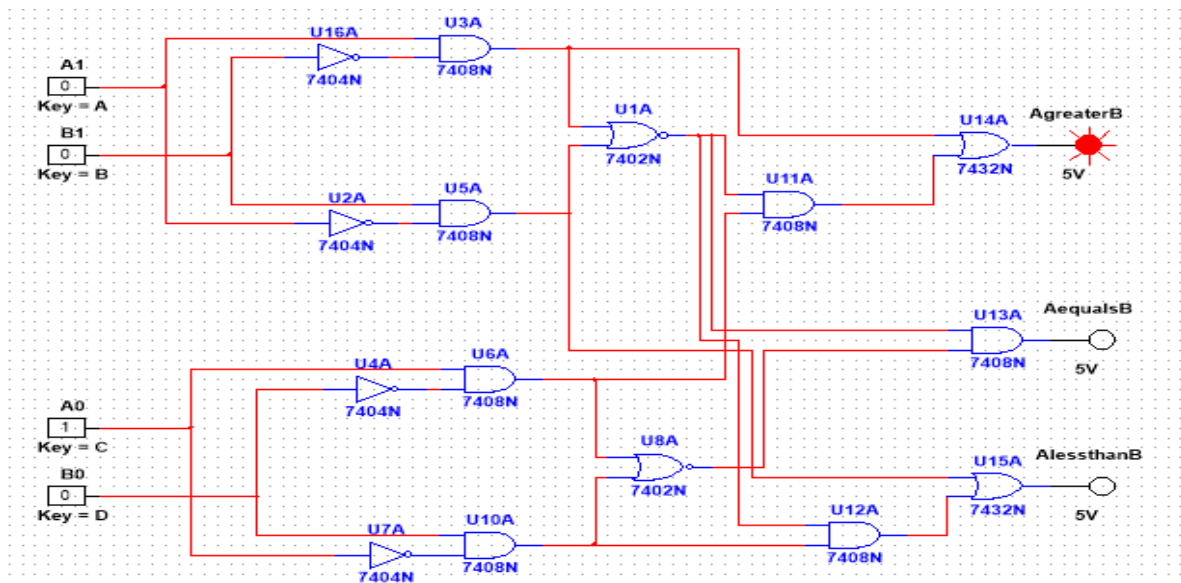

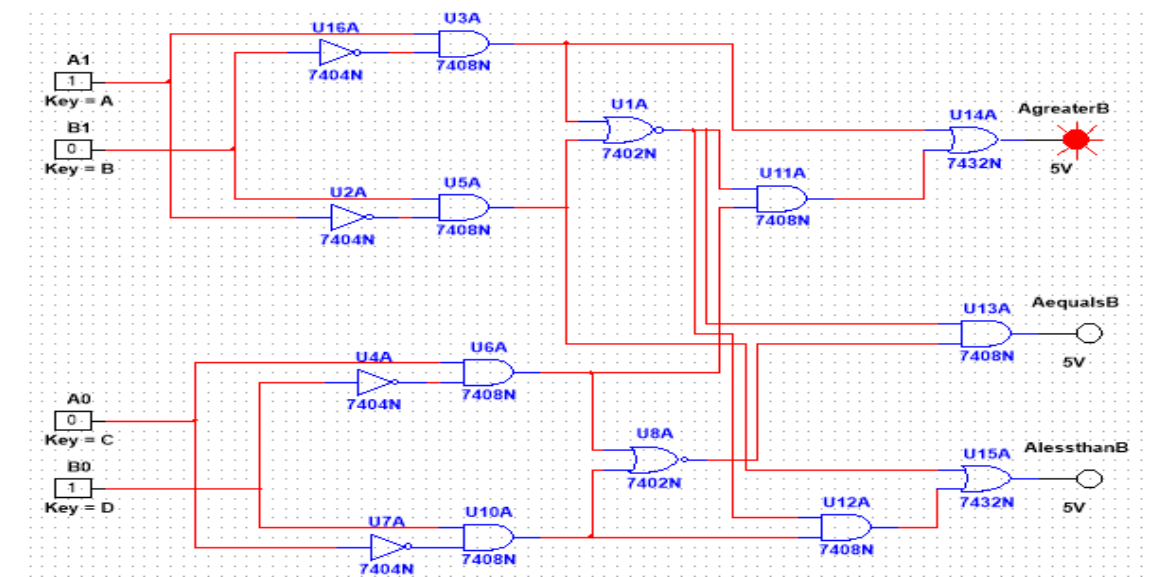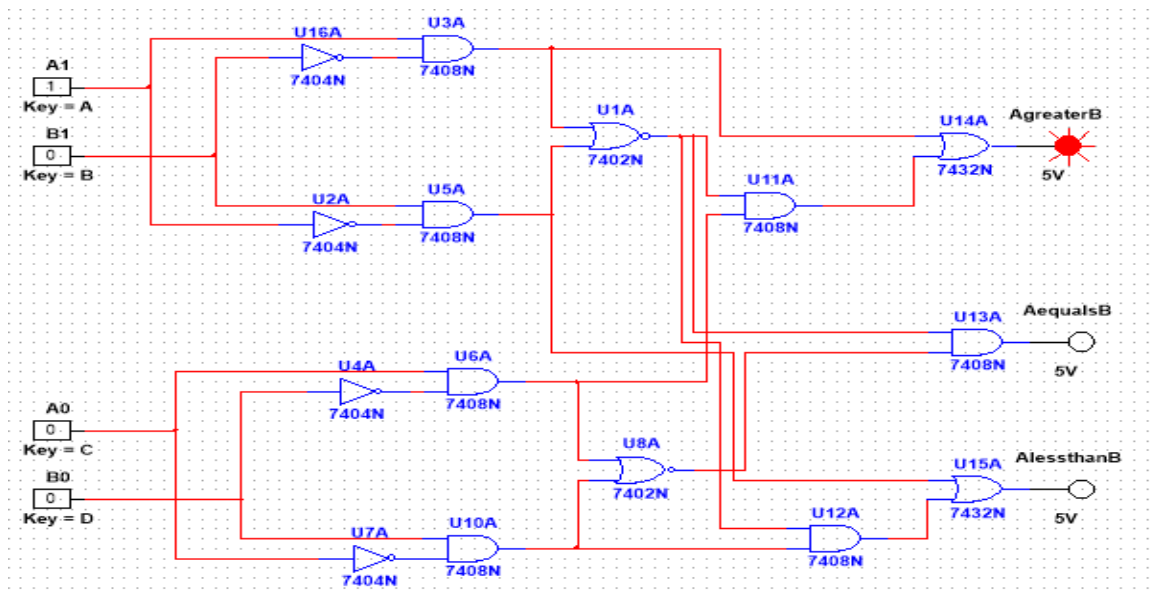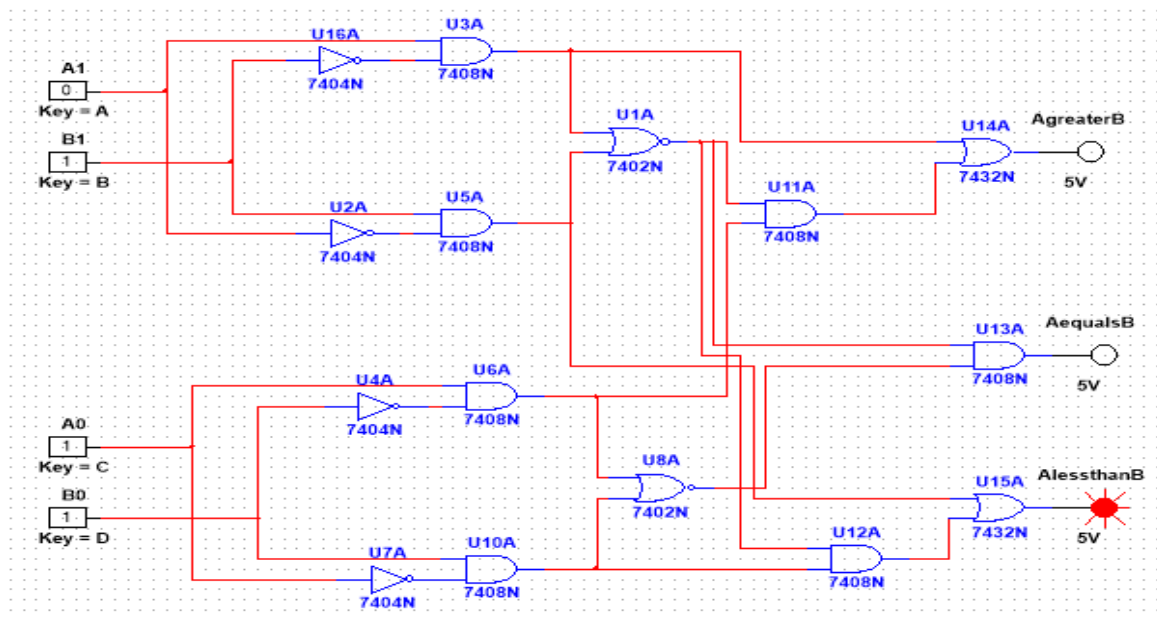


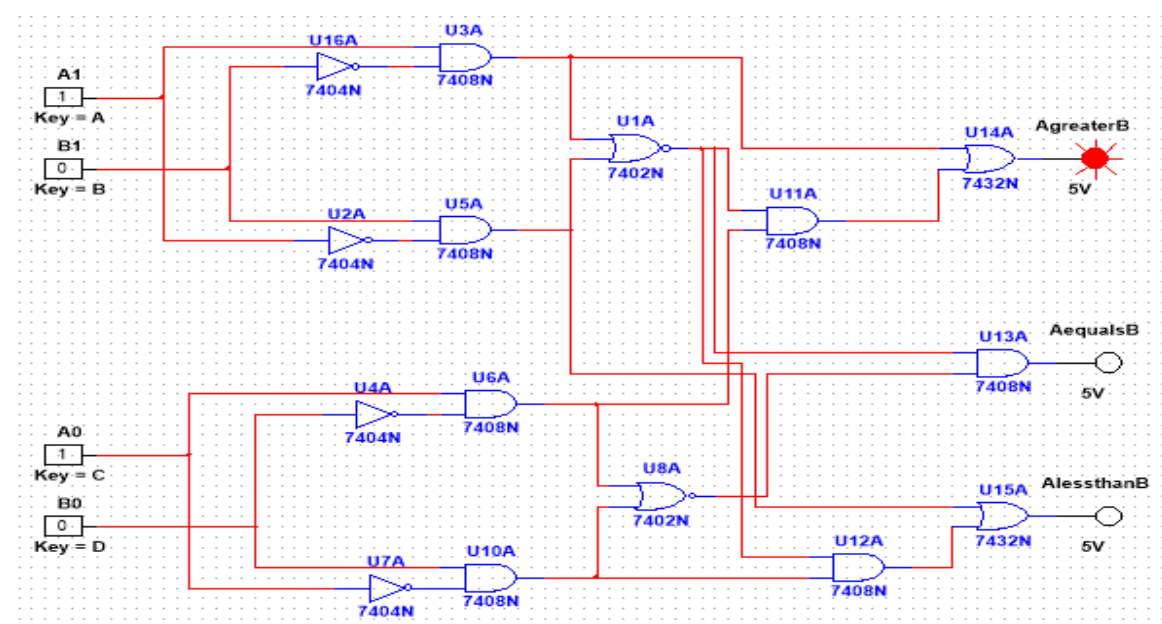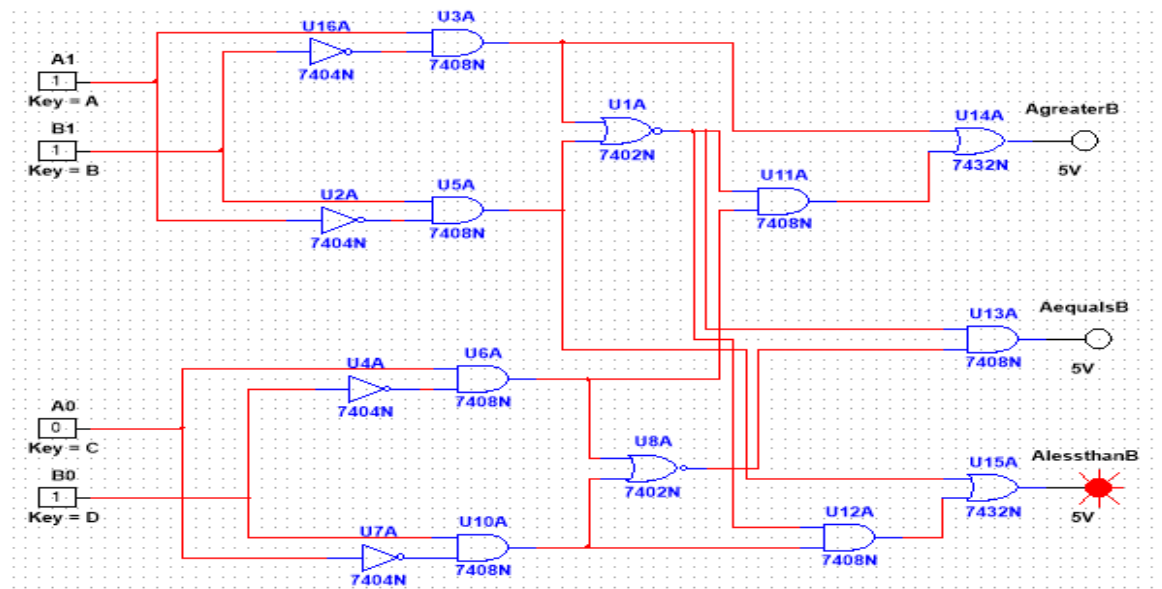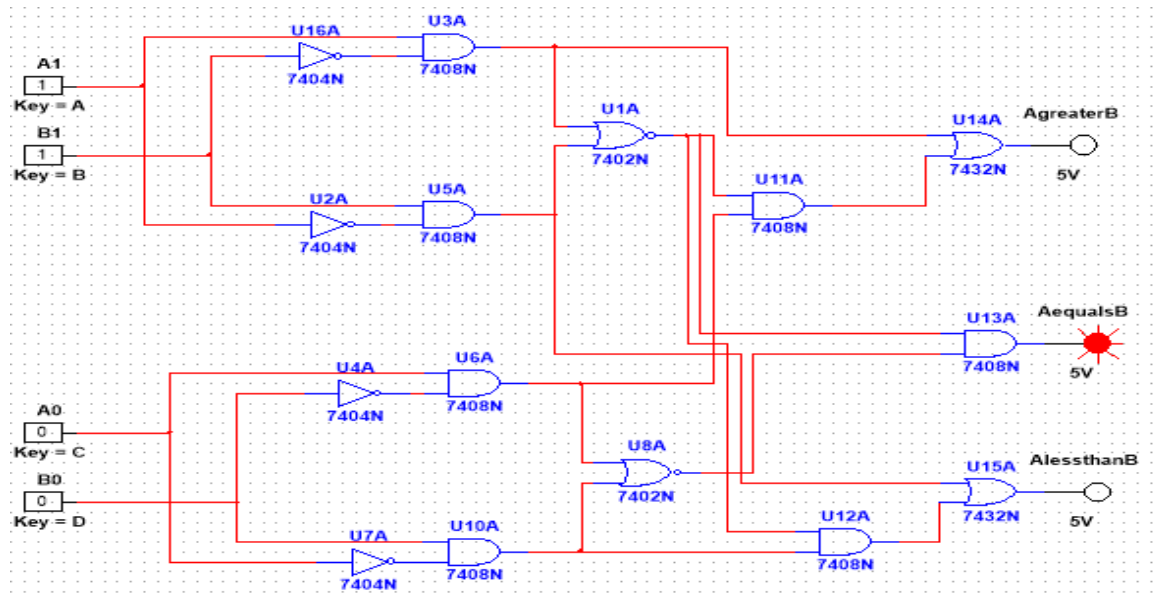

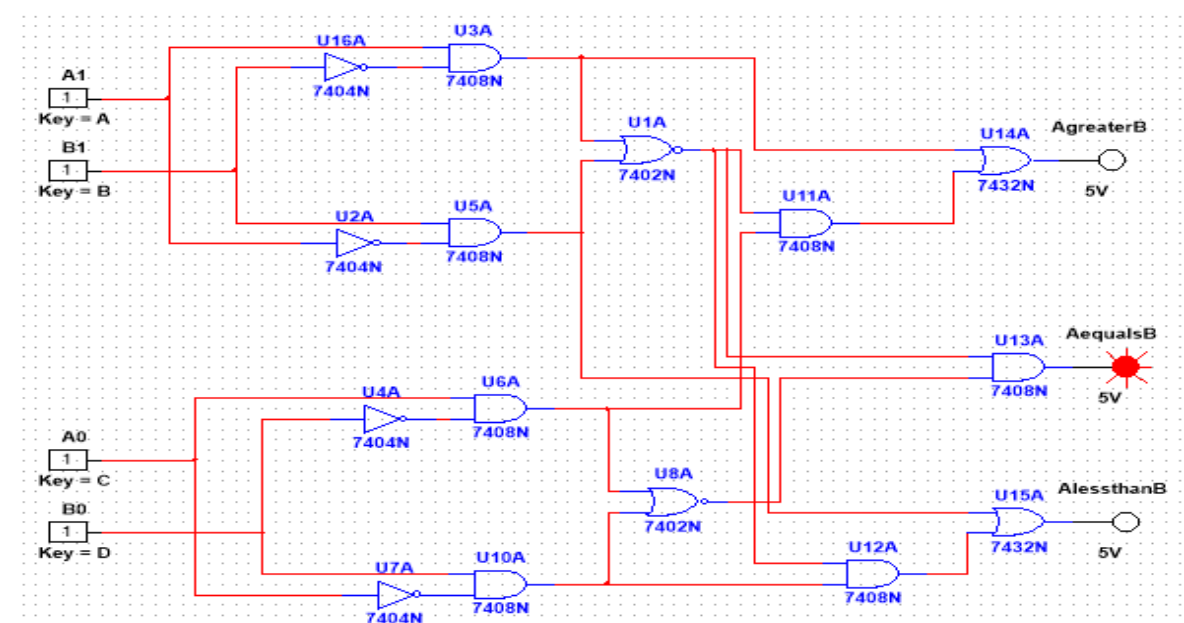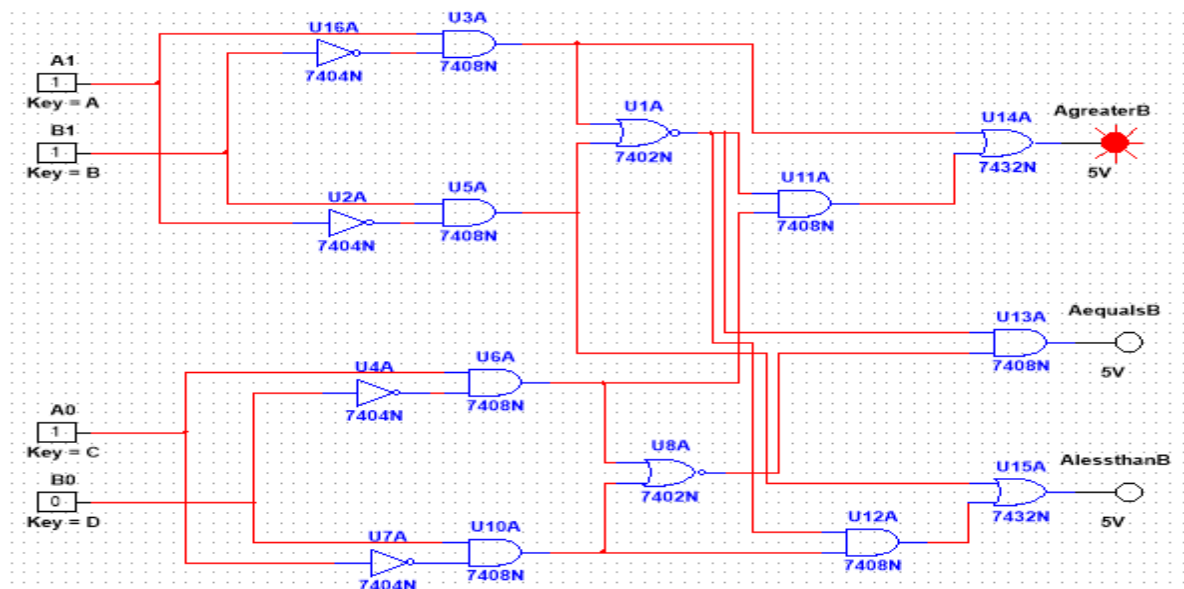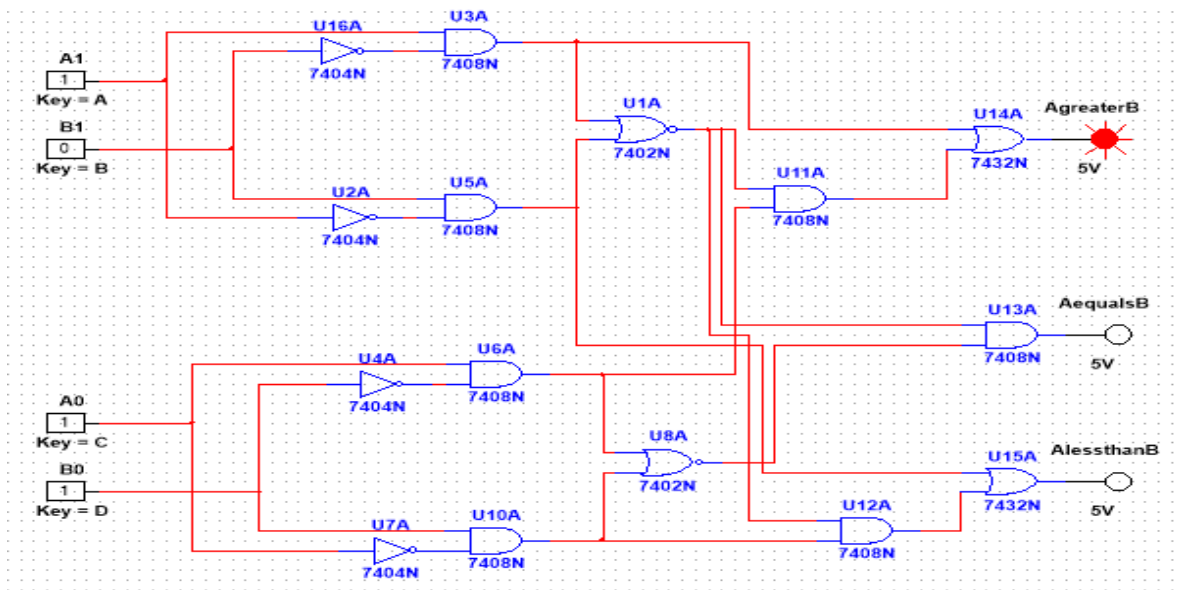


Report Question:

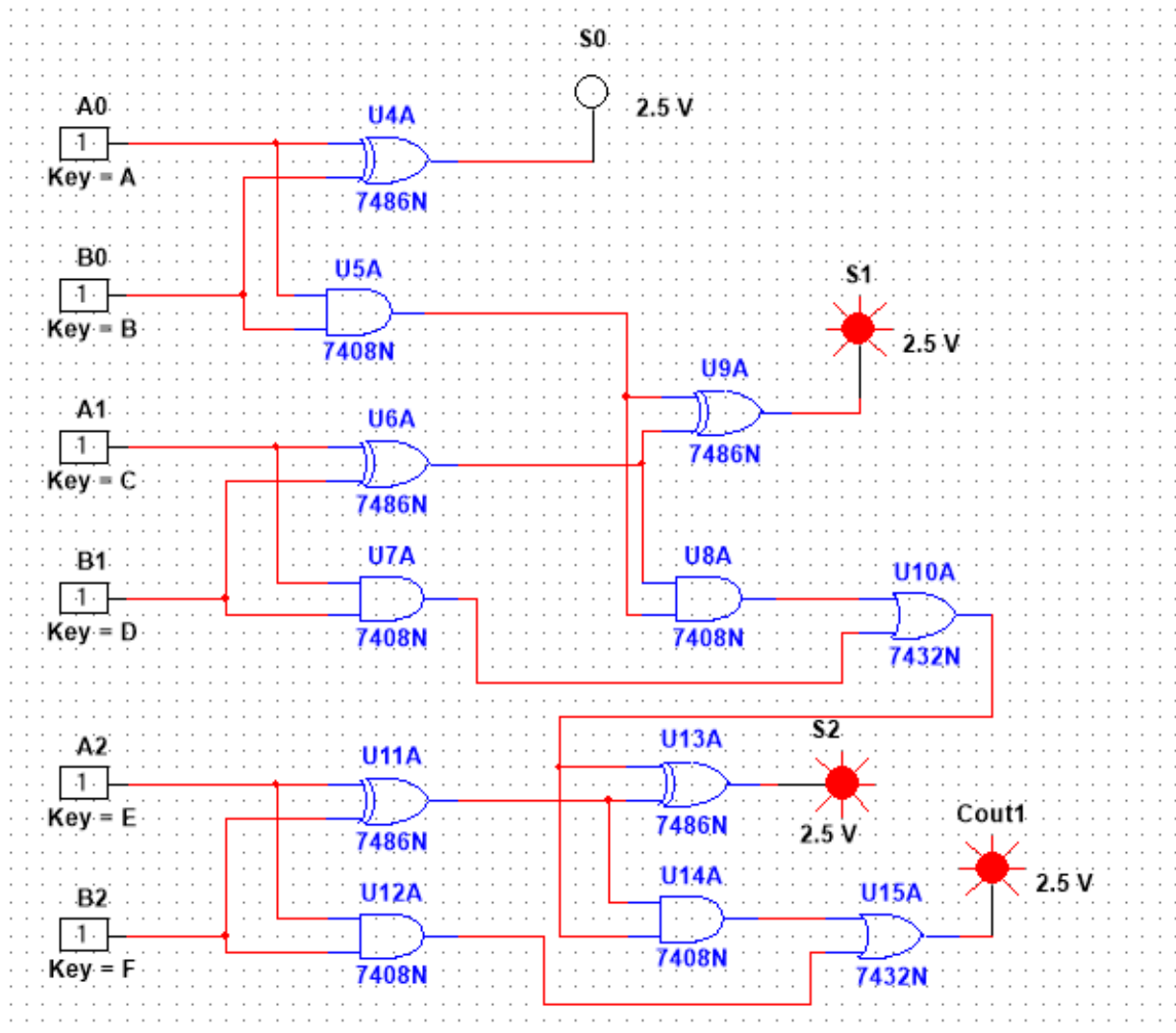
1. Design a full adder circuit for performing 3-bit binary addition.



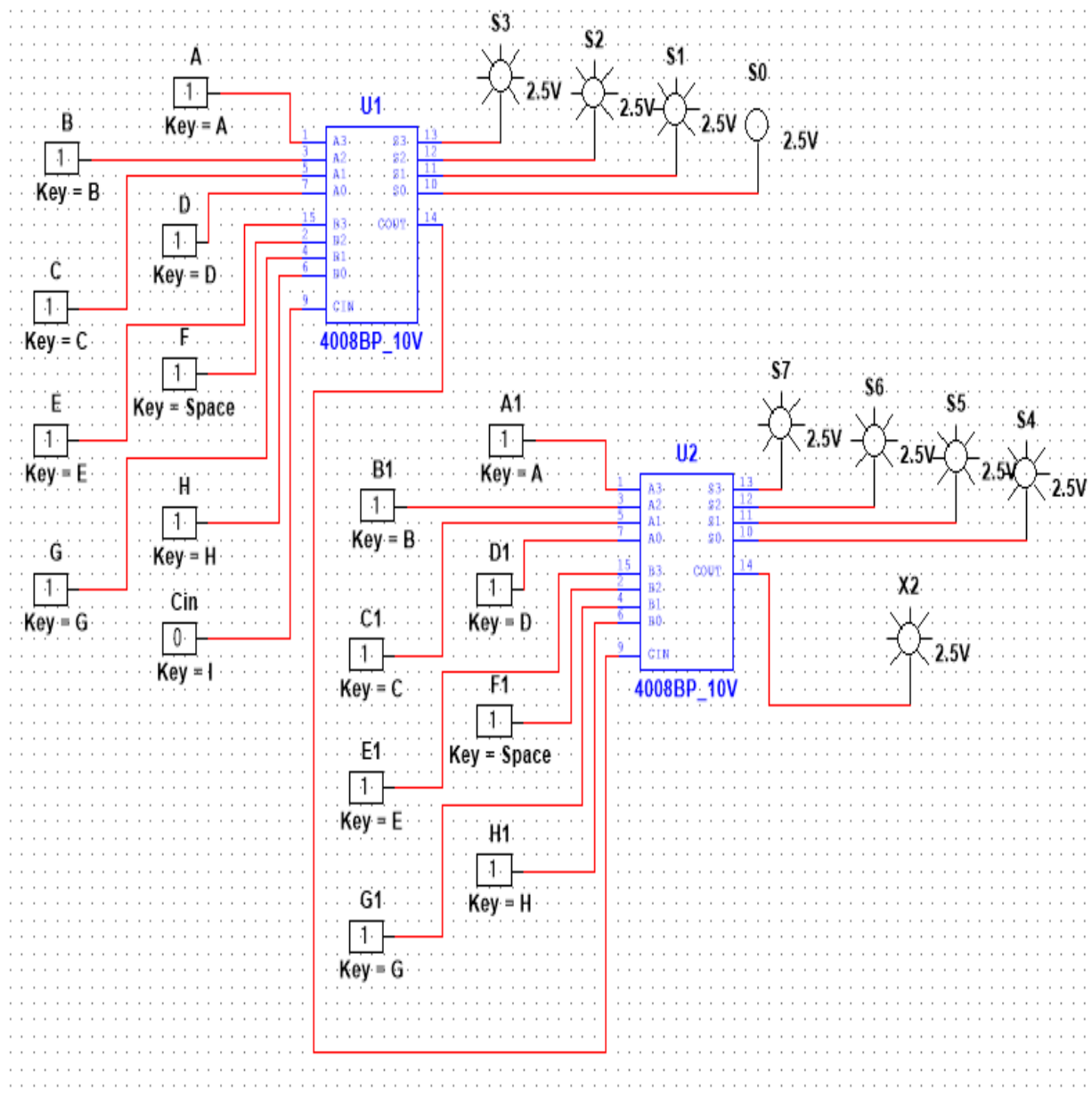2. Design an 8 bit full adder using 4 bit full adder IC 4008 from PSIM.



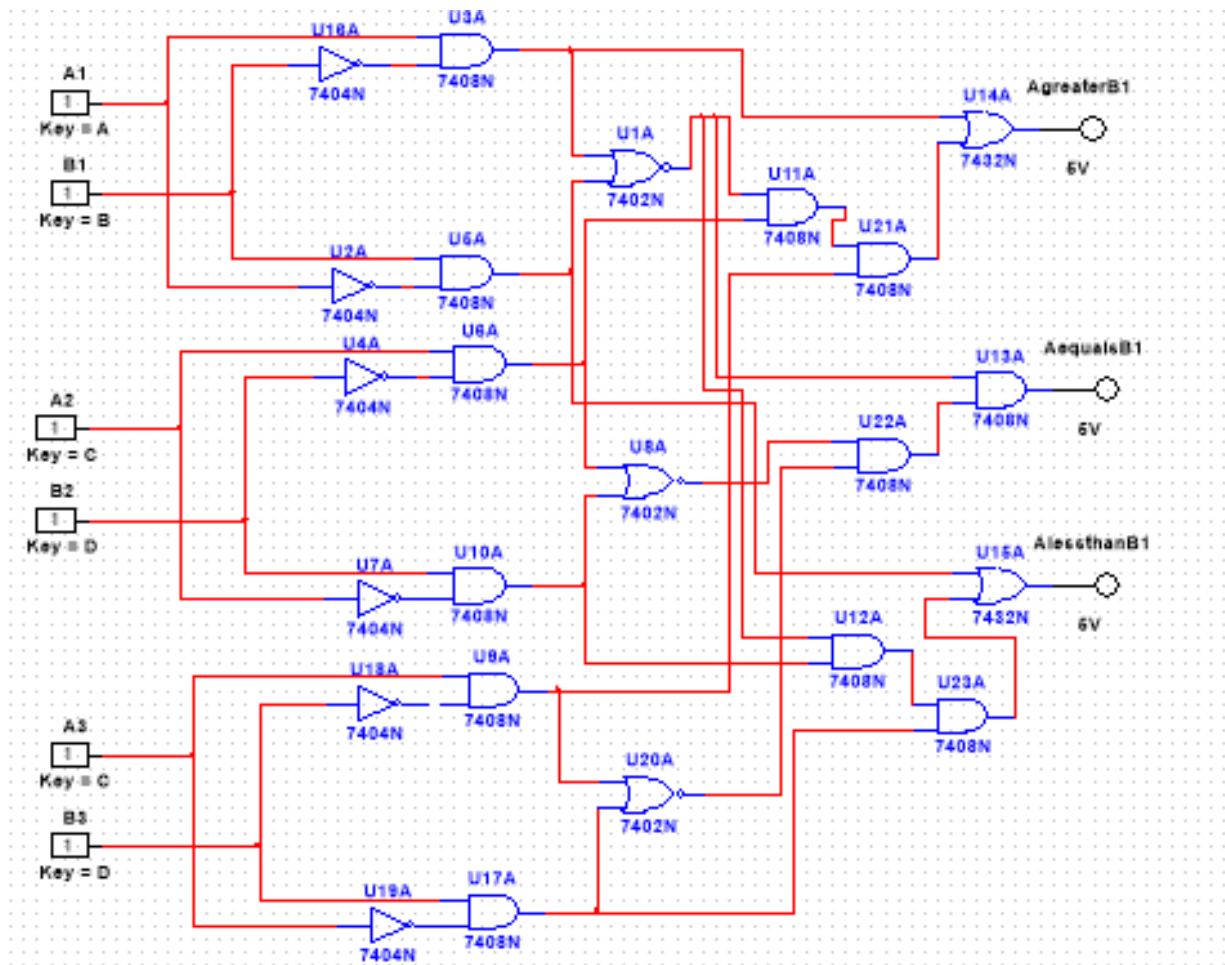3. Design a comparator circuit for comparing two words, each of 3 bits of input using 1 bit block.



Discussion and Conclusion:

In this experiment, we acquired fundamental understanding of learning and implementing an Adder and Comparator. The performance of our system was flawless throughout the simulation phase, as confirmed by the truth table. Ultimately, we conducted a thorough comparison between the simulation results and our truth table, and they were found to be completely identical.

Reference:

<http://www.circuitstoday.com/half-adder-and-full-adder>

