

Welcome to Final Term

[Fall 2021-22 Semester]

Final-Term Evaluation

Attendance	: 10 Marks
Quiz	: 20 marks
[Mainly Two (2) Quizzes and Two (2) Make up Quizzes]	
Assignments	: 20 marks
Viva	: 10 marks
Home Exam [MCQ/FB/TF in Final-Term Full Syllabus]	: 20 marks
Home Exam [Math on Final-Term Full Syllabus]	: 20 marks
Total	: 100 marks

Final-Term Course Descriptions

AC Circuits:

- Phasor Algebraic, Phasor or Vector Diagram.
- R branch, L branch, C branch, RL series/Parallel, RC series/parallel, RLC series/parallel, series-parallel circuits with AC source: Equation of instantaneous voltage, current and power; Total impedances/admittance calculation; power factor, reactive factor, real power, reactive power, apparent power calculation; and Application of VDR, CDR, KVL and KCL
- Source Conversion, Mesh Analysis, Nodal Analysis, Wye–Delta ($Y-\Delta$) or Tee–Pai ($T-\Pi$) conversion and Delta–Wye ($\Delta-Y$) or Pai – Tee ($\Pi - T$)
- Super position Theorem, Thevenin's Theorem, Norton's Theorem and Maximum Power Transfer Theorem

Electrical Machine:

- **Basic Theories for Electrical Machines:** Electromagnetism, Flemings hand rules, Transformer,
- **DC Machines:** DC generator and DC motor,
- **AC Machines:** Induction motor, Synchronous generator or Alternator, Synchronous Motor, Single phase induction Motor
- **Special Machines:** Stepper Motor, Universal Motor, Servo Motor, Permanent-magnet Synchronous motor, hysteresis motor, Reluctance motor, Linear motor



Review on AC Circuit

Instantaneous value: $e(t)$, $v(t)$, $i(t)$, $p(t)$ etc.

Peak or Crest value: E_m , V_m , I_m

Peak-to-peak value: E_{p-p} , V_{p-p} , I_{p-p}

Period: T [s]

Frequency: f [Hz]

Angular Frequency: ω [rad/s]

Phase angle: $[\theta_e, \theta_v \text{ and } \theta_i]$

Initial Angle: $[\theta_{e0}, \theta_{v0} \text{ and } \theta_{i0}]$

Angle Difference: Voltage Angle – Current Angle

Phase Difference: | Angle Difference |

Phase Relation: [in phase, leading, lagging]

$$f = \frac{1}{T} \text{ Hz}$$

$$\omega = \frac{\alpha}{t} \text{ rad/s}$$

$$\omega = \frac{2\pi}{T} \text{ rad/s} \\ = 2\pi f \text{ rad/s}$$

The instantaneous or time domain equation

$$e(t) = E_m \sin(\alpha + \theta_e) \text{ V} = E_m \sin(\omega t + \theta_e) \text{ V}$$

$$v(t) = V_m \sin(\alpha + \theta_v) \text{ V} = V_m \sin(\omega t + \theta_v) \text{ V}$$

$$i(t) = I_m \sin(\alpha + \theta_i) \text{ A} = I_m \sin(\omega t + \theta_i) \text{ A}$$

Initial Angle = – Phase Angle

Angle Difference = Voltage angle – Current Angle = 0°

Phase Relation: $v(t)$ and $i(t)$ are **in phase**.

Angle Difference = Voltage angle – Current Angle $> 0^\circ$

Phase Relation: $v(t)$ **leads** $i(t)$, or $i(t)$ **lags** $v(t)$

Angle Difference = Voltage angle – Current Angle $< 0^\circ$

Phase Relation: $v(t)$ **lags** $i(t)$, or $i(t)$ **leads** $v(t)$

$$\cos \alpha = \sin(\alpha + 90^\circ)$$

$$-\cos \alpha = \sin(\alpha - 90^\circ)$$

$$-\sin \alpha = \sin(\alpha \pm 180^\circ)$$

Average Value or Mean Value

For asymmetrical wave:


$$\text{Average Value} = \frac{\text{Area under the curve in one cycle}}{\text{Duration of one cycle}}$$

$$I_{ave} = \frac{1}{T} \int_0^T i(t) dt = \frac{1}{2\pi} \int_0^{2\pi} i(\theta) d\theta$$

For symmetrical wave:

$$\text{Average Value} = \frac{\text{Area under the curve in half-cycle}}{\text{Duration of half-cycle}}$$
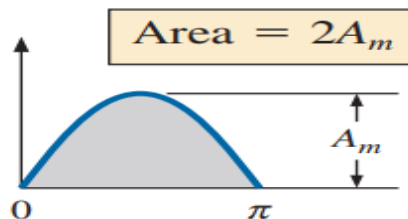
$$I_{ave} = \frac{1}{T/2} \int_0^{T/2} i(t) dt = \frac{1}{\pi} \int_0^{\pi} i(\theta) d\theta$$



RMS or Effective Value

Analytical or Integral Method:

$$I_{rms} = \sqrt{\frac{\int_0^T i^2(t) dt}{T}} \quad (13.31)$$

$$I_{rms} = \sqrt{\frac{\text{area}(i^2(t))}{T}} \quad (13.32)$$

$$I_{ave} = \frac{\pi}{2} I_m = 0.637 I_m$$

$$E_{ave} = \frac{\pi}{2} E_m = 0.637 E_m$$

$$V_{ave} = \frac{\pi}{2} V_m = 0.637 V_m$$

$$I = I_{rms} = \frac{I_m}{\sqrt{2}} = 0.707 I_m$$

$$E = E_{rms} = \frac{E_m}{\sqrt{2}} = 0.707 E_m$$

$$V = V_{rms} = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

Chapter 14

The Basic Elements and Phasors

Phasor Algebra/Complex Number



Vector Quantities Represent by Complex Number :

1. Magnitude
2. Direction

Phasor Quantities Represent by Complex Number:

1. Magnitude (RMS value for voltage and current)
2. Direction (Phase angle)
3. Continuously change with respect to time [such as sine and cosine waves]

Complex Number can be represented by three different ways:

1. Polar or Phasor form
2. Cartesian or Rectangular form
3. Exponential form

14.7 RECTANGULAR FORM:

$$C = X + jY \quad (14.17)$$

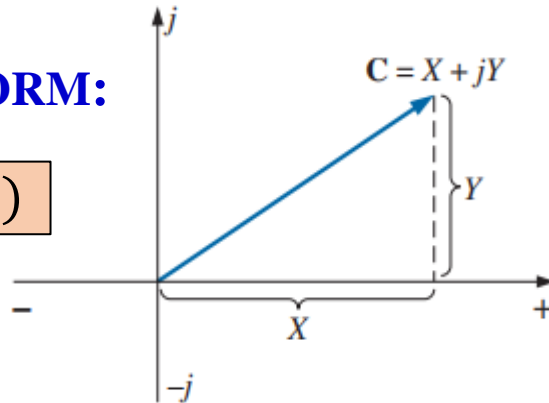





FIG. 14.39 Defining the rectangular form.

EXAMPLE 14.13 Sketch the following complex numbers in the complex plane:

a. $C = 3 + j4$

b. $C = 0 - j6$

c. $C = -10 - j20$

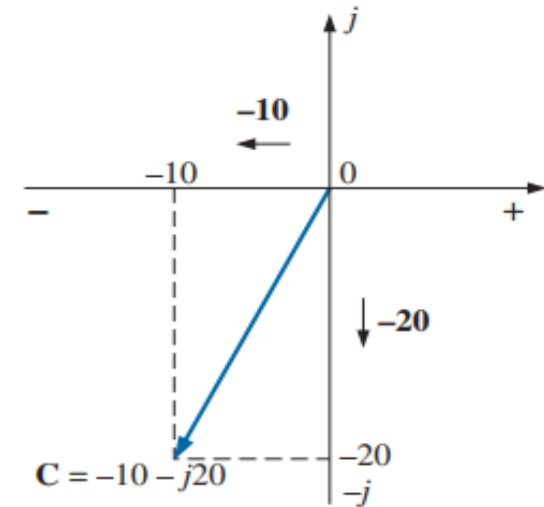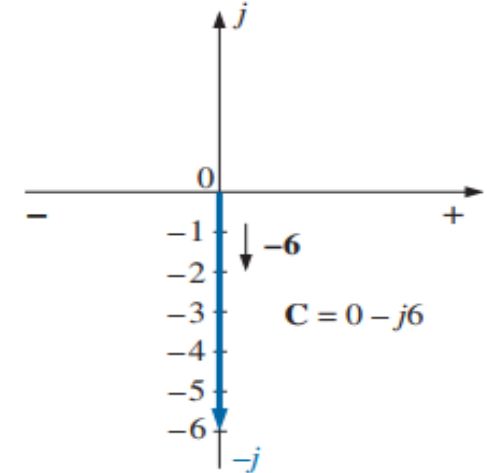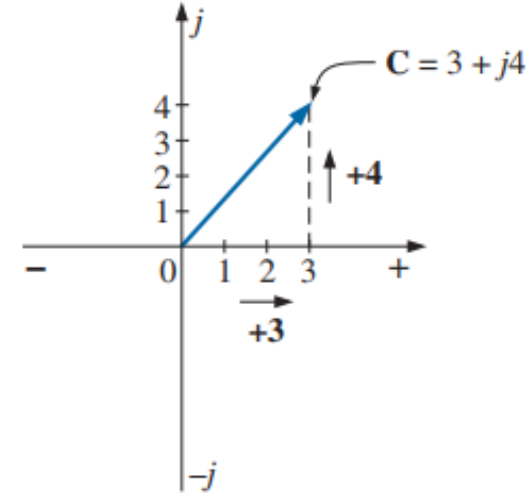

$$j = \sqrt{-1} \quad (14.24)$$

$$j^2 = -1 \quad (14.25)$$

$$\frac{1}{j} = -j \quad (14.26)$$

14.8 POLAR OR PHASOR FORM:

$$C = Z \angle \theta \quad (14.18)$$

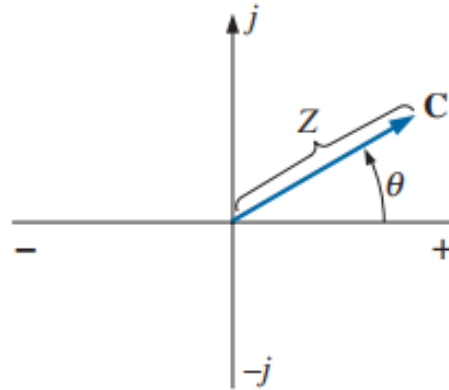


FIG. 14.43 Defining the polar form.

$$C = -Z \angle \theta = -Z \angle \theta \pm 180^\circ \quad (14.19)$$


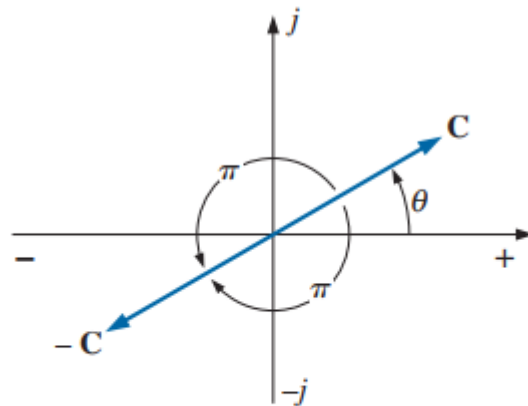
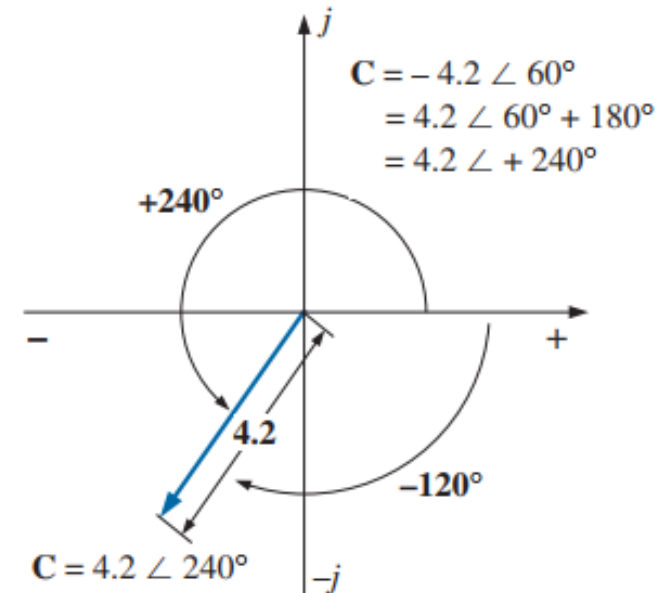
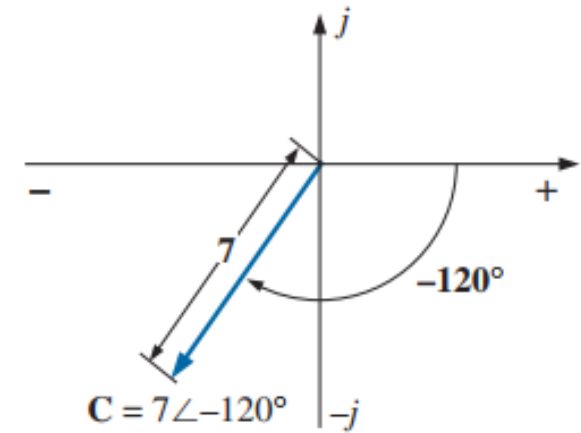


FIG. 14.44

Demonstrating the effect of a negative sign on the polar form.

EXAMPLE 14.14 Sketch the following complex numbers in the complex plane:

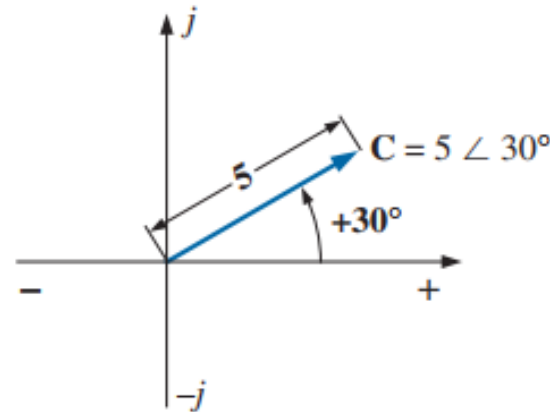- a. $C = 5 \angle 30^\circ$ b. $C = 7 \angle -120^\circ$ c. $C = -4.2 \angle 60^\circ$



14.9 CONVERSION BETWEEN FORMS

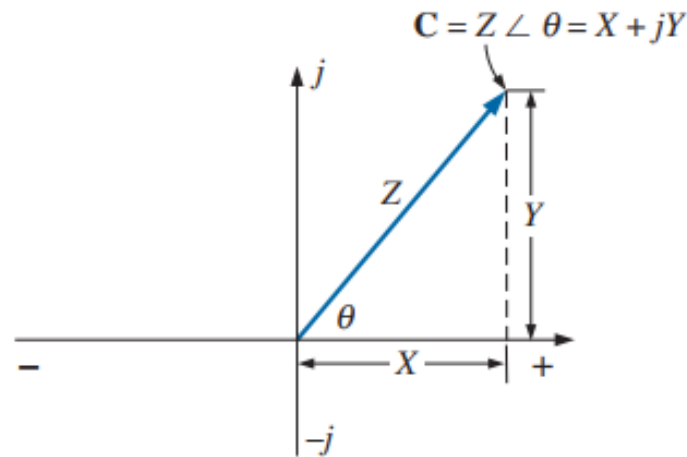


FIG. 14.48 Conversion between forms.

Rectangular to Polar

$$Z = \sqrt{X^2 + Y^2} \quad (14.20)$$

$$\theta = \tan^{-1} \frac{Y}{X} \quad (14.21)$$


Polar to Rectangular

$$X = Z \cos \theta \quad (14.22)$$

$$Y = Z \sin \theta \quad (14.23)$$

EXAMPLE 14.15 Convert the following from rectangular to polar form:

$$C = 3 + j4 \quad (\text{Fig. 14.49})$$

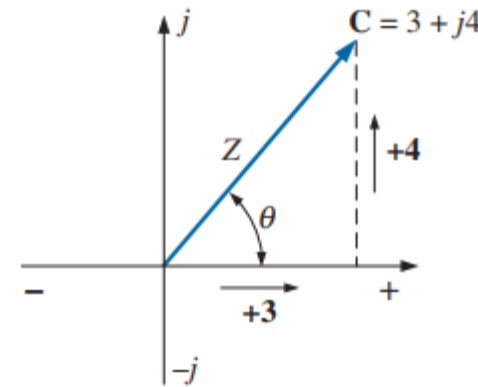


Solution: $Z = \sqrt{(3)^2 + (4)^2}$
 $= \sqrt{25} = 5$
 $\theta = \tan^{-1} \left(\frac{4}{3} \right) = 53.13^\circ$

and $C = 5 \angle 53.13^\circ$

FIG. 14.49 Example 14.15.

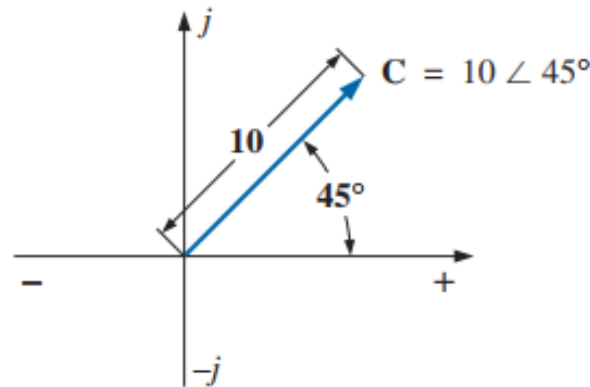EXAMPLE 14.16 Convert the following from polar to rectangular form:

$$C = 10 \angle 45^\circ \quad (\text{Fig. 14.50})$$



Solution: $X = 10 \cos 45^\circ$
 $= (10)(0.707)$
 $= 7.07$

$$Y = 10 \sin 45^\circ$$

$$= (10)(0.707)$$

$$= 7.07$$

FIG. 14.50 Example 14.16.

and $C = 7.07 + j7.07$

14.10 MATHEMATICAL OPERATIONS WITH COMPLEX NUMBERS


Addition

$$C_1 = \pm X_1 \pm jY_1 \quad \text{and} \quad C_2 = \pm X_2 \pm jY_2$$

$$C_1 + C_2 = (\pm X_1 \pm X_2) + j(\pm Y_1 \pm Y_2) \quad (14.27)$$

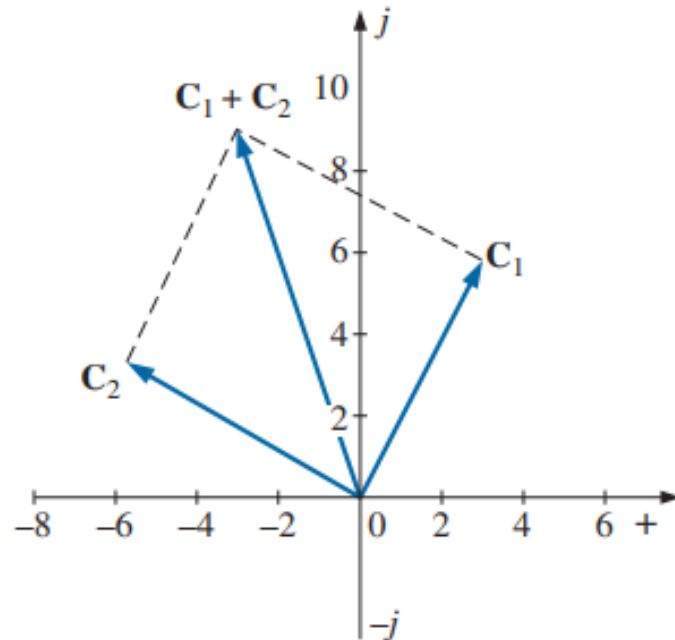EXAMPLE 14.19 Add $C_1 = 3 + j6$ and $C_2 = -6 + j3$.

Solutions: $C_1 + C_2 = (3 - 6) + j(6 + 3) = -3 + j9$




Subtraction

$$C_1 = \pm X_1 \pm jY_1 \quad \text{and} \quad C_2 = \pm X_2 \pm jY_2$$

$$C_1 - C_2 = [\pm X_1 - (\pm X_2)] + j[\pm Y_1 - (\pm Y_2)] \quad (14.28)$$

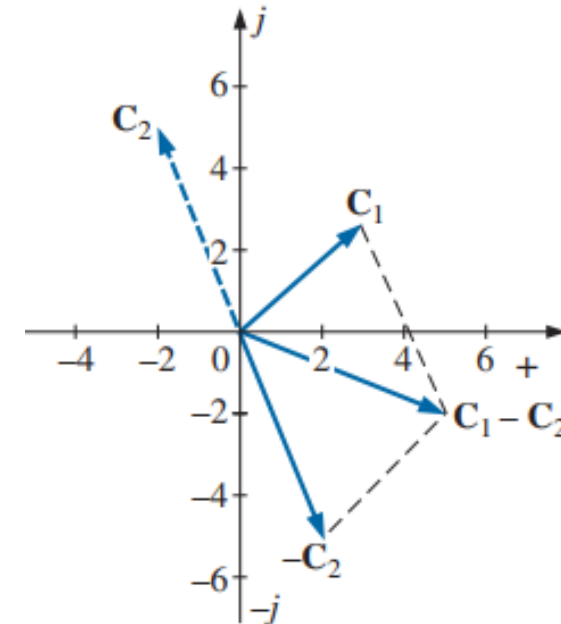EXAMPLE 14.20 Subtract $C_2 = -2 + j5$ from $C_1 = +3 + j3$.

Solutions: $C_1 - C_2 = [3 - (-2)] + j(3 - 5) = 5 - j2$



Multiplication

$$\mathbf{C}_1 = X_1 + jY_1 \quad \text{and} \quad \mathbf{C}_2 = X_2 + jY_2$$

then $\mathbf{C}_1 \cdot \mathbf{C}_2$:

$$\begin{array}{r} X_1 + jY_1 \\ \times X_2 + jY_2 \\ \hline X_1X_2 + jY_1X_2 \\ + jX_1Y_2 + j^2Y_1Y_2 \\ \hline X_1X_2 + j(Y_1X_2 + X_1Y_2) + Y_1Y_2(-1) \end{array}$$

$$\boxed{\mathbf{C}_1 \cdot \mathbf{C}_2 = (X_1X_2 - Y_1Y_2) + j(Y_1X_2 + X_1Y_2)} \quad (14.29)$$

Multiplication in Polar Form:

$$\mathbf{C}_1 = Z_1 \angle \theta_1 \quad \text{and} \quad \mathbf{C}_2 = Z_2 \angle \theta_2$$

$$\boxed{\mathbf{C}_1 \cdot \mathbf{C}_2 = Z_1Z_2 \angle \theta_1 + \theta_2} \quad (14.30)$$

Division

$$\mathbf{C}_1 = X_1 + jY_1 \quad \text{and} \quad \mathbf{C}_2 = X_2 + jY_2$$

$$\begin{aligned} \frac{\mathbf{C}_1}{\mathbf{C}_2} &= \frac{(X_1 + jY_1)(X_2 - jY_2)}{(X_2 + jY_2)(X_2 - jY_2)} \\ &= \frac{(X_1X_2 + Y_1Y_2) + j(X_2Y_1 - X_1Y_2)}{X_2^2 + Y_2^2} \end{aligned}$$

$$\boxed{\frac{\mathbf{C}_1}{\mathbf{C}_2} = \frac{X_1X_2 + Y_1Y_2}{X_2^2 + Y_2^2} + j \frac{X_2Y_1 - X_1Y_2}{X_2^2 + Y_2^2}} \quad (14.31)$$

Division in Polar Form:

$$\mathbf{C}_1 = Z_1 \angle \theta_1 \quad \text{and} \quad \mathbf{C}_2 = Z_2 \angle \theta_2$$

$$\boxed{\frac{\mathbf{C}_1}{\mathbf{C}_2} = \frac{Z_1}{Z_2} \angle \theta_1 - \theta_2} \quad (14.32)$$

EXAMPLE 14.23

- a. Find $C_1 \cdot C_2$ if $C_1 = 5 \angle 20^\circ$ and $C_2 = 10 \angle 30^\circ$
b. Find $C_1 \cdot C_2$ if $C_1 = 2 \angle -40^\circ$ and $C_2 = 7 \angle +120^\circ$

Solutions:

- a. $C_1 \cdot C_2 = (5 \angle 20^\circ)(10 \angle 30^\circ) = (5)(10) \angle 20^\circ + 30^\circ = \mathbf{50 \angle 50^\circ}$
b. $C_1 \cdot C_2 = (2 \angle -40^\circ)(7 \angle +120^\circ) = (2)(7) \angle -40^\circ + 120^\circ$
 $\quad \quad \quad = \mathbf{14 \angle +80^\circ}$

EXAMPLE 14.25

- a. Find C_1/C_2 if $C_1 = 15 \angle 10^\circ$ and $C_2 = 2 \angle 7^\circ$.
b. Find C_1/C_2 if $C_1 = 8 \angle 120^\circ$ and $C_2 = 16 \angle -50^\circ$.

Practice Problem 39 ~ 49 [Ch. 14]

Solutions:

- a. $\frac{C_1}{C_2} = \frac{15 \angle 10^\circ}{2 \angle 7^\circ} = \frac{15}{2} \angle 10^\circ - 7^\circ = \mathbf{7.5 \angle 3^\circ}$
b. $\frac{C_1}{C_2} = \frac{8 \angle 120^\circ}{16 \angle -50^\circ} = \frac{8}{16} \angle 120^\circ - (-50^\circ) = \mathbf{0.5 \angle 170^\circ}$



APPLICATION OF COMPLEX NUMBERS IN AC CIRCUIT

Instantaneous Form (Time Domain) Equation:

$$\begin{aligned} e(t) &= E_m \sin(\omega t + \theta_e) \text{ V} \\ v(t) &= V_m \sin(\omega t + \theta_v) \text{ V} \\ i(t) &= I_m \sin(\omega t + \theta_i) \text{ A} \end{aligned}$$

Phasor Form (Polar Form) Equation:

$$\begin{aligned} \mathbf{E} = \vec{E} &= E_{rms} \angle \theta_e = E \angle \theta_e \text{ V} \\ \mathbf{V} = \vec{V} &= V_{rms} \angle \theta_v = V \angle \theta_v \text{ V} \\ \mathbf{I} = \vec{I} &= I_{rms} \angle \theta_i = I \angle \theta_i \text{ A} \end{aligned}$$

Rectangular Form (Cartesian Form) Equation:

$$\begin{aligned} \mathbf{E} = \vec{E} &= E_r + jE_i \text{ V} \\ \mathbf{V} = \vec{V} &= V_r + jV_i \text{ V} \\ \mathbf{I} = \vec{I} &= I_r + jI_i \text{ A} \end{aligned}$$

EXAMPLE 14.27 Convert the following from the time to (i) the phasor domain, and (ii) the rectangular domain.


Time Domain	Phasor Domain	Rectangular Domain
(a) $v(t) = 70.7 \sin(\omega t - 60^\circ) \text{ V}$	$\vec{V} = (0.707 \times 70.7) \text{ V} \angle -60^\circ = \mathbf{50 \text{ V} \angle -60^\circ}$	$\mathbf{V = 25 - j43.3 \text{ V}}$
(b) $i(t) = 21.21 \cos(\omega t + 20^\circ) \text{ A}$ $= 21.21 \sin(\omega t + 110^\circ) \text{ A}$	$\vec{I} = (0.707 \times 21.21) \text{ A} \angle 110^\circ = \mathbf{15 \text{ A} \angle 110^\circ}$	$\mathbf{I = 15 [\cos(110^\circ) + j \sin(110^\circ)]}$ $= -5.13 + j14.1 \text{ A}$
(c) $e(t) = -200 \cos \omega t \text{ V}$ $= 200 \sin(\omega t - 90^\circ) \text{ V}$	$\vec{E} = (0.707 \times 200) \text{ V} \angle -90^\circ = \mathbf{141.42 \text{ V} \angle -90^\circ}$	$\mathbf{E = 141.42 [\cos(-90^\circ) + j \sin(-90^\circ)]}$ $= 0 - j141.42 \text{ V}$
(d) $i(t) = -4.5 \sin(\omega t + 30^\circ) \text{ A}$ $= 4.5 \sin(\omega t - 150^\circ) \text{ A}$ $= 4.5 \sin(\omega t + 210^\circ) \text{ A}$	$\vec{I} = (0.707 \times 4.5) \text{ A} \angle -150^\circ = \mathbf{3.18 \text{ A} \angle -150^\circ}$ $\vec{I} = (0.707 \times 4.5) \text{ A} \angle 210^\circ = \mathbf{3.18 \text{ A} \angle 210^\circ}$	$\mathbf{I = 3.18 [\cos(210^\circ) + j \sin(210^\circ)]}$ $= -2.75 - j1.59 \text{ A}$



EXAMPLE 14.27.1 Convert the following from Cartesian form to (i) the phasor domain, and (ii) the instantaneous form for 50 Hz.

Rectangular Form	Phasor Form	Instantaneous Form
<p>(a) $\vec{V} = 25 - j43.3 \text{ V}$</p> <p>RMS value: 50 V Phase Angle: -60° Peak Value: 70.7 V</p>	<p>$V = \sqrt{25^2 + (-43.3)^2} = 50 \text{ V}$</p> <p>$\theta_v = \tan^{-1} \left[\frac{-43.3}{25} \right] = -60^\circ$</p> <p>$V = 50\text{V} \angle -60^\circ$</p>	<p>$\omega = 2\pi \times 50 = 314 \text{ rad/s}$</p> <p>$v(t) = (\sqrt{2}) \times 50 \sin(314t - 60^\circ) \text{ V}$ $= 70.7 \sin(314t - 60^\circ) \text{ V}$</p>
<p>(b) $\vec{E} = j150 \text{ V}$</p> <p>RMS value: 150 V Phase Angle: 90° Peak Value: 212.13 V</p>	<p>$E = \sqrt{0^2 + 150^2} = 150 \text{ V}$</p> <p>$\theta_e = \tan^{-1} \left[\frac{150}{0} \right] = 90^\circ$</p> <p>$E = 150\text{V} \angle 90^\circ$</p>	<p>$e(t) = (\sqrt{2}) \times 150 \sin(314t + 90^\circ) \text{ V}$ $= 212.13 \sin(314t + 90^\circ) \text{ V}$ $= 212.13 \cos 314t \text{ V}$</p>
<p>(d) $\vec{I} = -j5 \text{ A}$</p> <p>RMS value: 5 A Phase Angle: -90° Peak Value: 7.07 A</p>	<p>$I = \sqrt{0^2 + (-5)^2} = 5 \text{ A}$</p> <p>$\theta_i = \tan^{-1} \left[\frac{-5}{0} \right] = -90^\circ$</p> <p>$I = 5\text{A} \angle -90^\circ$</p>	<p>$i(t) = (\sqrt{2}) \times 5 \sin(314t - 90^\circ) \text{ A}$ $= 7.07 \sin(314t - 90^\circ) \text{ A}$ $= -7.07 \cos 314t \text{ A}$</p>
<p>(e) $\vec{V} = -100 \text{ V}$</p> <p>RMS value: 100 V Phase Angle: $\pm 180^\circ$ Peak Value: 141.42 V</p>	<p>$V = 100\text{V} \angle \pm 180^\circ$</p>	<p>$v(t) = (\sqrt{2}) \times 100 \sin(314t \pm 180^\circ) \text{ V}$ $= 141.42 \sin(314t \pm 180^\circ) \text{ V}$ $= -141.42 \sin 314t \text{ V}$</p>

IMPEDANCE

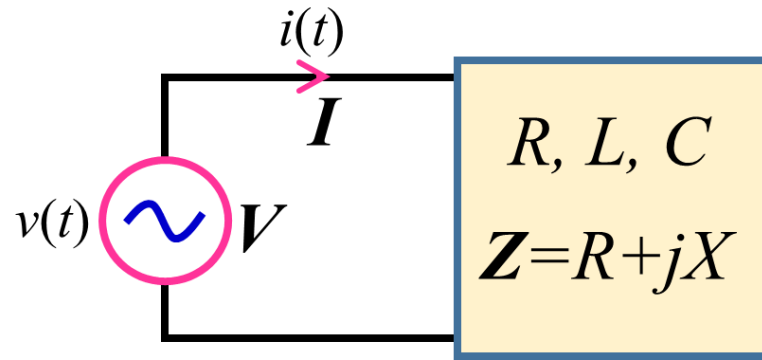

Impedance: Impedance is the ratio of **voltage** to **current**.

Impedance opposes the flow of current.

Impedance represent by **Z**. Its unit is **ohm** (Ω).

$$Z = \frac{V}{I} = \frac{V_{rms} \angle \theta_v}{I_{rms} \angle \theta_i} = \frac{V \angle \theta_v}{I \angle \theta_i} = \frac{V}{I} \angle (\theta_v - \theta_i) = Z \angle \theta_z = R + jX \quad \Omega$$

Magnitude of Impedance: $Z = \frac{V_m}{I_m} = \frac{V_{rms}}{I_{rms}} = \frac{V}{I} \quad \Omega$

Angle of Impedance: $\theta_z = \theta_v - \theta_i$

Resistance (Real Part of Impedance): $R = Z \cos \theta_z \quad \Omega$

Reactance (Imaginary Part of Impedance): $X = Z \sin \theta_z \quad \Omega$

Practically, $-90^\circ \leq \theta_z \leq 90^\circ$

Reactance is the property of inductor and capacitor to oppose the flow of current.

There are two reactance in electrical circuit:
(i) **inductive reactance** (X_L), and (ii) **capacitive reactance** (X_C).

Inductive Reactance:


$$X_L = \omega L = 2\pi f L \quad [\Omega] \quad X_L \propto f$$

Capacitive Reactance:

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} \quad [\Omega] \quad X_C \propto \frac{1}{f}$$

Impedance (**Z**) is not a phasor quantity because for a circuit it is constant. That means impedance does not change with respect to time.

ADMITTANCE

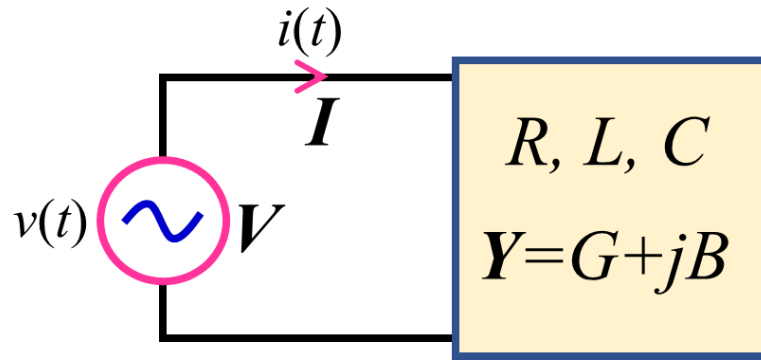

Admittance (Y) is also not a phasor quantity.

Admittance: Admittance is the ratio of **current** to **voltage**.

Admittance is **reciprocal of impedance**.

Admittance is a measure of how well an ac circuit will *admit*, or allow, current to flow in the circuit.

Admittance represent by Y . Its unit is **Siemens** (S).

$$Y = \frac{1}{Z} = \frac{I}{V} = \frac{I_{rms} \angle \theta_i}{V_{rms} \angle \theta_v} = \frac{I \angle \theta_i}{V \angle \theta_v} = \frac{I}{V} \angle (\theta_i - \theta_v) \\ = Y \angle \theta_y = G + jB \text{ S}$$

Magnitude of Admittance: $Y = \frac{1}{Z} = \frac{I_m}{V_m} = \frac{I_{rms}}{V_{rms}} = \frac{I}{V} \text{ S}$

Angle of Admittance: $\theta_y = -\theta_z = \theta_i - \theta_v$

Conductance (Real Part of admittance):

$$G = \frac{1}{R} = Y \cos \theta_y \quad \text{S}$$

Susceptance (Imaginary Part of admittance):

$$B = \frac{1}{X} = Y \sin \theta_y \quad \text{S}$$

Susceptance is the property of inductor and capacitor to help the flow of current. There are two susceptance in electrical circuit: (i) **inductive susceptance** (B_L), and (ii) **capacitive susceptance** (B_C).

Inductive Susceptance:

$$B_L = \frac{1}{X_L} = \frac{1}{\omega L} = \frac{1}{2\pi f L} \text{ [S]} \quad B_L \propto \frac{1}{f}$$

Capacitive Susceptance:

$$B_C = \frac{1}{X_C} = \omega C = 2\pi f C \text{ [S]} \quad B_C \propto f$$

EXAMPLE The supply voltage and current of a circuit are $v(t) = 100\sin 314t$ V and $i(t) = 15\cos(314t - 120^\circ)$ A.

(a) Find (i) the magnitude of impedance, (ii) the angle of impedance, (iii) the value of resistance, and (iv) the value of reactance.

(b) Find (i) the magnitude of admittance, (ii) the angle of admittance, (iii) the value of conductance, and (iv) the value of susceptance.

(c) Write the impedance and admittance in both polar and cartesian or rectangular form.

Solution: Converting current from cosine to sine, we have: $i(t) = 15\sin(314t - 30^\circ)$ A.

Now, $V_m = 100$ V, $I_m = 15$ A, $\theta_v = 0^\circ$ and $\theta_i = -30^\circ$

$$(a) (i) Z = \frac{V}{I} = \frac{V_m}{I_m} = \frac{100\text{V}}{15\text{A}} = \mathbf{6.67 \Omega}$$

$$(ii) \theta_Z = \theta_v - \theta_i = 0^\circ - (-30^\circ) = \mathbf{30^\circ}$$

$$(iii) R = Z \cos \theta_Z = 6.67 \times \cos(30^\circ) = \mathbf{5.78 \Omega}$$

$$(iv) X = Z \sin \theta_Z = 6.67 \times \sin(30^\circ) = \mathbf{3.34 \Omega}$$

$$(b) (i) Y = \frac{1}{Z} = \frac{I}{V} = \frac{I_m}{V_m} = \frac{15\text{A}}{100\text{V}} = \mathbf{0.15 \text{ S} \text{ or } 150\text{mS}}$$

$$(ii) \theta_y = -\theta_Z = \theta_i - \theta_v = -30^\circ - 0^\circ = \mathbf{-30^\circ}$$

$$(iii) G = Y \cos \theta_y = 150 \times \cos(-30^\circ) = \mathbf{129.9 \text{ mS}}$$

$$(iv) B = Y \sin \theta_y = 150 \times \sin(-30^\circ) = \mathbf{-75 \text{ mS}}$$

$$(c) \vec{Z} = Z \angle 30^\circ = 6.67\Omega \angle 30^\circ$$

$$\vec{Z} = Z = 5.78 + j3.34 \Omega$$

$$\vec{Y} = Y \angle -30^\circ = 150\text{mS} \angle -30^\circ$$

$$\vec{Y} = Y = 129.9 + j75 \text{ mS}$$

EXAMPLE The supply voltage and current of a circuit are $V = 200\text{V} \angle 90^\circ$ and $I = 10\text{A} \angle 30^\circ$.

(a) Find the impedance and admittance in both polar and cartesian or rectangular form.

(b) Find (i) the magnitude of impedance, (ii) the angle of impedance, (iii) the value of resistance, and (iv) the value of reactance.

(c) Find (i) the magnitude of admittance, (ii) the angle of admittance, (iii) the value of conductance, and (iv) the value of susceptance.

Solution:

$$(a) Z = \frac{V}{I} = \frac{200\text{V} \angle 90^\circ}{10\text{V} \angle 30^\circ} = 20\Omega \angle 60^\circ = 10 + j17.32 \Omega$$

$$Y = \frac{1}{Z} = \frac{I}{V} = \frac{10\text{V} \angle 30^\circ}{200\text{V} \angle 90^\circ} = 0.05\text{S} \angle -60^\circ = 0.025 + j0.0433 \text{ S} = 25 + j43.3 \text{ mS}$$

$$(b) (i) Z = 20 \Omega; \quad (ii) \theta_Z = 60^\circ; \quad (iii) R = 10 \Omega; \quad (iv) X = 17.32 \Omega$$

$$(c) (i) Y = 0.05 \text{ S}; \quad (ii) \theta_Y = -60^\circ; \quad (iii) G = 25 \text{ mS}; \quad (iv) B = 43.3 \text{ mS}$$

EXAMPLE The supply voltage and impedance of a circuit are $v(t) = 282.84\cos 314t$ V and $Z = 20\Omega\angle 60^\circ$. Find the current $i(t)$.

Solution: Converting voltage from cosine to sine, we have: $v(t) = 282.84\sin(314t + 90^\circ)$ V.

Now, $V_m = 282.84$ V, $\theta_v = 90^\circ$ and $Z = 20\Omega$, $\theta_z = 60^\circ$

We know that: $Z = \frac{V_m}{I_m}$ $\theta_z = \theta_v - \theta_i$

$$I_m = \frac{V_m}{Z} = \frac{282.84}{20} = 14.142 \text{ A}$$

$$\theta_i = \theta_v - \theta_z = 90^\circ - 60^\circ = 30^\circ$$

Thus, $i(t) = 14.142\sin(314t + 30^\circ)$ A

EXAMPLE The supply current and impedance of a circuit are $i(t) = 15\sin 377t$ V and $Z = 17.32 + j10\Omega$. Find the voltage $v(t)$.

Solution: Converting impedance from Cartesian to Polar form:

$$Z = 17.32 + j10\Omega = 20\Omega\angle 30^\circ$$

Now, $I_m = 15$ V, $\theta_i = 0^\circ$ and $Z = 20\Omega$, $\theta_z = 30^\circ$

We know that: $Z = \frac{V_m}{I_m}$ $\theta_z = \theta_v - \theta_i$

$$V_m = ZI_m = 20 \times 15 = 300 \text{ V}$$

$$\theta_v = \theta_i + \theta_z = 0^\circ + 30^\circ = 30^\circ$$

Thus, $v(t) = 300\sin(377t + 30^\circ)$ V

