



EEE 3101: Digital Logic and Circuits

Multiplexer & De-Multiplexer


Course Teacher: Nafiz Ahmed Chisty

**Associate Professor, Department of EEE & CoE
Head (UG), Department of EEE
Faculty of Engineering
Room# DNG03, Ground Floor, D Building
Email: chisty@aiub.edu
Website: <http://engg.aiub.edu/>
Website: www.nachisty.com**




Multiplexer or Mux or Data Selector

 
In the old days, several machines could share an I/O device with a **Switch**. The **Switch** allows one computer's output to go to the printer's input.



 Multiplexer (or mux), also known as a data selector, is a device that selects between several input signals and forwards the selected input to a single output line. A multiplexer of 2^n inputs has n select lines, which are used to select which input line to send to the output.




 - This is a 2-to-1 multiplexer or mux.
- The multiplexer routes one of its data inputs (D0 or D1) to the output Q, based on the value of S:
 - If **S=0**, then D0 is the output (**Q=D0**).
 - If **S=1**, then D1 is the output (**Q=D1**).



Block diagram, Truth table and Circuit

Block Diagram:

 

Truth table:

S	D1	D0	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1



S	Q
0	D0
1	D1

$$Q = S' D0 + S D1$$

When **S=0**

$$Q = 0' D0 + 0 D1$$

$$Q = 1 D0 + 0$$

$$Q = D0$$


When **S=1**

$$Q = 1' D0 + 1 D1$$

$$Q = 0 D0 + 1 D1$$

$$Q = D1$$


Circuit Diagram:

 


$$Q = S' D0 + S D1$$

4x1 Multiplexer

- Block Diagram:

 

- Circuit Diagram:


 


- Truth table:

Select Input		Output (selected input)
S_1	S_0	Q
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3


$$Q = S_1' S_0' D_0 + S_1' S_0 D_1 + S_1 S_0' D_2 + S_1 S_0 D_3$$

Timing Diagram

  

Select Input		Output (selected input)
S ₁	S ₀	Q
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃

Enable inputs

 

- Many devices have an additional **enable** input, which "activates" or "deactivates" the device.
- We could design a 2-to-1 multiplexer with an enable input that's used as follows.
 - EN=0 disables the multiplexer, which forces the output to be 0. (It does *not* turn off the multiplexer.)
 - EN=1 enables the multiplexer, and it works as specified earlier.
- Enable inputs are especially useful in combining smaller muxes together to make larger ones, as we'll see later today.

EN	S	D1	D0	Q
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1



EN	S	D1	D0	Q
0	x	x	x	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1





EN	S	Q
0	x	0
1	0	D0
1	1	D1

Implementation of Higher-order Multiplexers using lower-order Multiplexers

8x1 Mux using **ONLY** 4x1 Mux

Select Input			Output (selected input)
S_2	S_1	S_0	Q
0	0	0	D_0
0	0	1	D_1
0	1	0	D_2
0	1	1	D_3
1	0	0	D_4
1	0	1	D_5
1	1	0	D_6
1	1	1	D_7

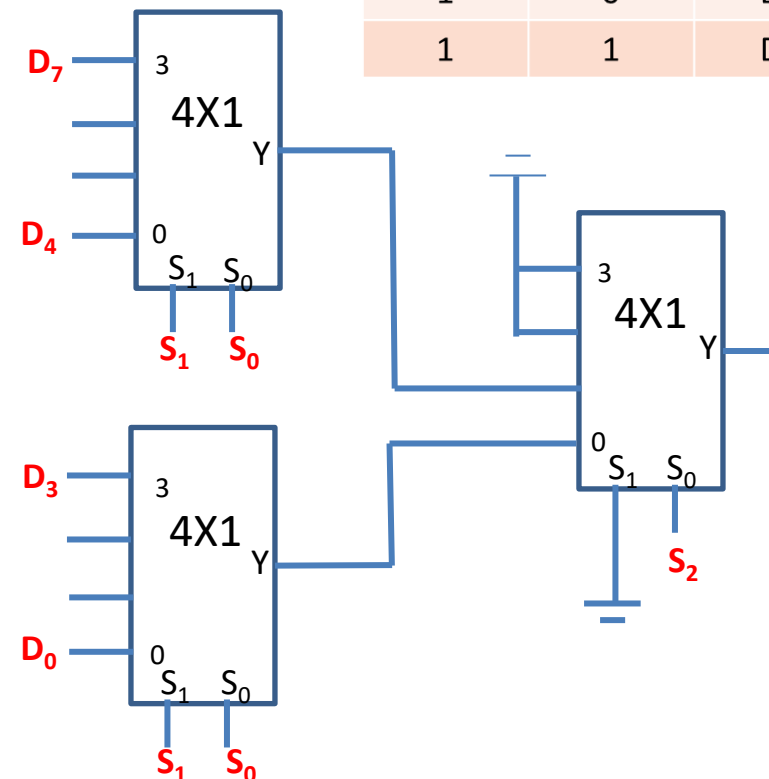 


Select Input		Output (selected input)
S_1	S_0	Q
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

Implementing functions with multiplexers

- Muxes can be used to implement arbitrary functions.
- One way to implement a function of n variables is to use an 2^n -to-1 mux:**
- For example, let's look at $f(x,y,z) = \Sigma(1,2,6,7)$.

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Select Input			Output (selected input)
S_2	S_1	S_0	Q
0	0	0	D_0
0	0	1	D_1
0	1	0	D_2
0	1	1	D_3
1	0	0	D_4
1	0	1	D_5
1	1	0	D_6
1	1	1	D_7

 

MULTIPLEXER

Boolean Function Implementation ([advanced](#))

Question: Implement the following function with **only one 4-to-1** multiplexer:

$$F(A,B,C) = \Sigma (1, 3, 5, 6)$$

For **3 variables**, it takes:

- a) One 8-to-1 Mux, or
- b) Three 4-to-1 Mux

Only ONE 4-to-1 ..???



Procedure:

- Implement the truth table and write the SOP expression in the decimal format:

Minterms	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0


$$F(A,B,C) = \Sigma (1, 3, 5, 6)$$

- If the Boolean function has $n+1$ Variables, then connect n of these variables to the select lines of a MUX maintain the order.

$$n+1 = 3$$

$$\Rightarrow n = 2$$

 - Based on the select lines, find the total number of input lines for the MUX. The remaining variable will be used for the inputs of the MUX.



- Consider now the single variable **A**. It can either be **0** or **1**.
- From the truth table, find the minterms for which **A** is **0**. The minterms are 0, 1, 2 & 3.
- From the truth table, find the minterms for which **A** is **1**. The minterms are 4, 5, 6 & 7.

Minterms	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

	I_0	I_1	I_2	I_3
A'	0	1	2	3
A	4	5	6	7

- List the inputs of the MUX and under them list all the minterms in two rows.
- The first row lists all those minterms where **A** is **0**, and the second row all the minterms with **A** is **1**.

- Circle all the minterms of the function and inspect **each column** separately.

$$F(A,B,C) = \Sigma (1, 3, 5, 6)$$


	I_0	I_1	I_2	I_3
A'	0	1	2	3
A	4	5	6	7
	0	1	A	A'

- If the two minterms in a column are not circled, **apply 0** to the corresponding MUX input.
- If the two minterms are circled, **apply 1** to the corresponding MUX input.
- If the bottom minterm is circled and the top is not circled, **apply A** (for this example) to the corresponding MUX input.
- If the top minterm is circled and the bottom is not circled, **apply A'** (for this example) to the corresponding MUX input.

$$F(A,B,C) = \Sigma (1, 3, 5, 6)$$

Minterms	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

	I_0	I_1	I_2	I_3
A'	0	1	2	3
A	4	5	6	7
	0	1	A	A'

 


Example: Implement the following function using 4x1 MUX:


$$F(A,B,C) = \Sigma (2, 3, 4, 6)$$

Minterms	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	0


	I_0	I_1	I_2	I_3
A'	0	1	2	3
A	4	5	6	7
	A	0	1	A'

 

	I_0	I_1	I_2	I_3
B'	0	1	4	5
B	2	3	6	7
	B	B	1	0

 

	I_0	I_1	I_2	I_3
C'	0	2	4	6
C	1	3	5	7
	0	1	C'	C'

 

Example:


$$F(A,B,C) = AB+BC$$

$$\begin{aligned}
 F(A,B,C) &= AB+BC \\
 &= AB(C+C')+(A+A')BC \\
 &= ABC+ABC'+ABC+A'BC \\
 &= \underset{7}{ABC}+\underset{6}{ABC'}+\underset{3}{A'BC}
 \end{aligned}$$

$$F(A,B,C) = \Sigma (3,6,7)$$

	I_0	I_1	I_2	I_3
A'	0	1	2	3
A	4	5	6	7
	0	0	A	1


Minterm	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	1
7	1	1	1	1

 

Demultiplexers

1-line-to 4-line demux

 A **demultiplexer (DEMUX)** basically reverses the multiplexing function. It takes digital information from one line and distributes it to a given number of output lines. For this reason, the demultiplexer is also known as a data distributor. As you will learn, decoders can also be used as demultiplexers.




$$D_0 = S_1' S_0' D_{in}$$

$$D_1 = S_1' S_0 D_{in}$$


$$D_2 = S_1 S_0' D_{in}$$

$$D_3 = S_1 S_0 D_{in}$$


DATA-SELECT INPUTS		OUTPUT SELECTED
S_1	S_0	
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

 

Timing Diagram


 


DATA-SELECT INPUTS		OUTPUT SELECTED
S_1	S_0	
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

 

Cascading DEMUX

Designing a 1x11 DEMUX using 1x2 DEMUX

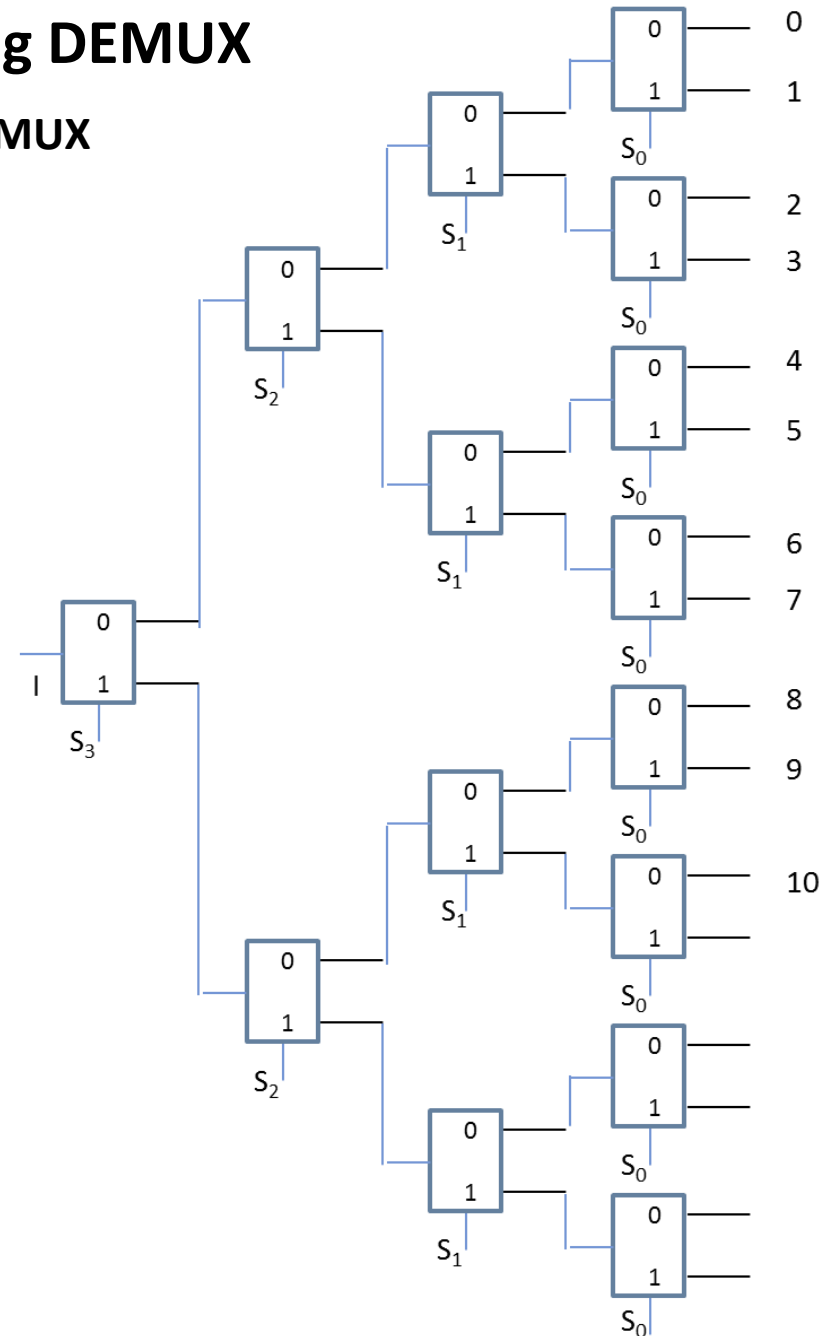 



Reference:

- [1] Thomas L. Floyd, "Digital Fundamentals" 11th edition, Prentice Hall.
- [2] M. Morris Mano, "Digital Logic & Computer Design" Prentice Hall.
- [3] Mixed contents from Vahid And Howard.





Thanks

