

Electronic Devices

Final Term Lecture - 03

Reference book:

Electronic Devices and Circuit Theory (Chapter-6)

Robert L. Boylestad and L. Nashelsky , (11th Edition)



Faculty of Engineering

American International University-Bangladesh

OBJECTIVES


- Become familiar with the construction and operating characteristics of Junction Field Effect (JFET), Metal-Oxide Semiconductor FET (MOSFET), and Metal-Semiconductor FET (MESFET) transistors.
- Be able to sketch the transfer characteristics from the drain characteristics of a JFET, MOSFET, and MESFET transistor.
- Understand the vast amount of information provided on the specification sheet for each type of FET.
- Be aware of the differences between the dc analysis of the various types of FETs.




FETs vs BJT's


- FET's (Field – Effect Transistors) are much like BJT's (Bipolar Junction Transistors).
- **Similarities:**
 - Amplifiers
 - Switching devices
 - Impedance matching circuits
- **Differences:**
 - FET's are voltage controlled devices whereas BJT's are current controlled devices.
 - FET's are unipolar devices whereas BJT's are bipolar devices.
 - FET's also have a higher input impedance, but BJT's have higher gains.
 - FET's are less sensitive to temperature variations and because of their construction they are more easily integrated into IC's.



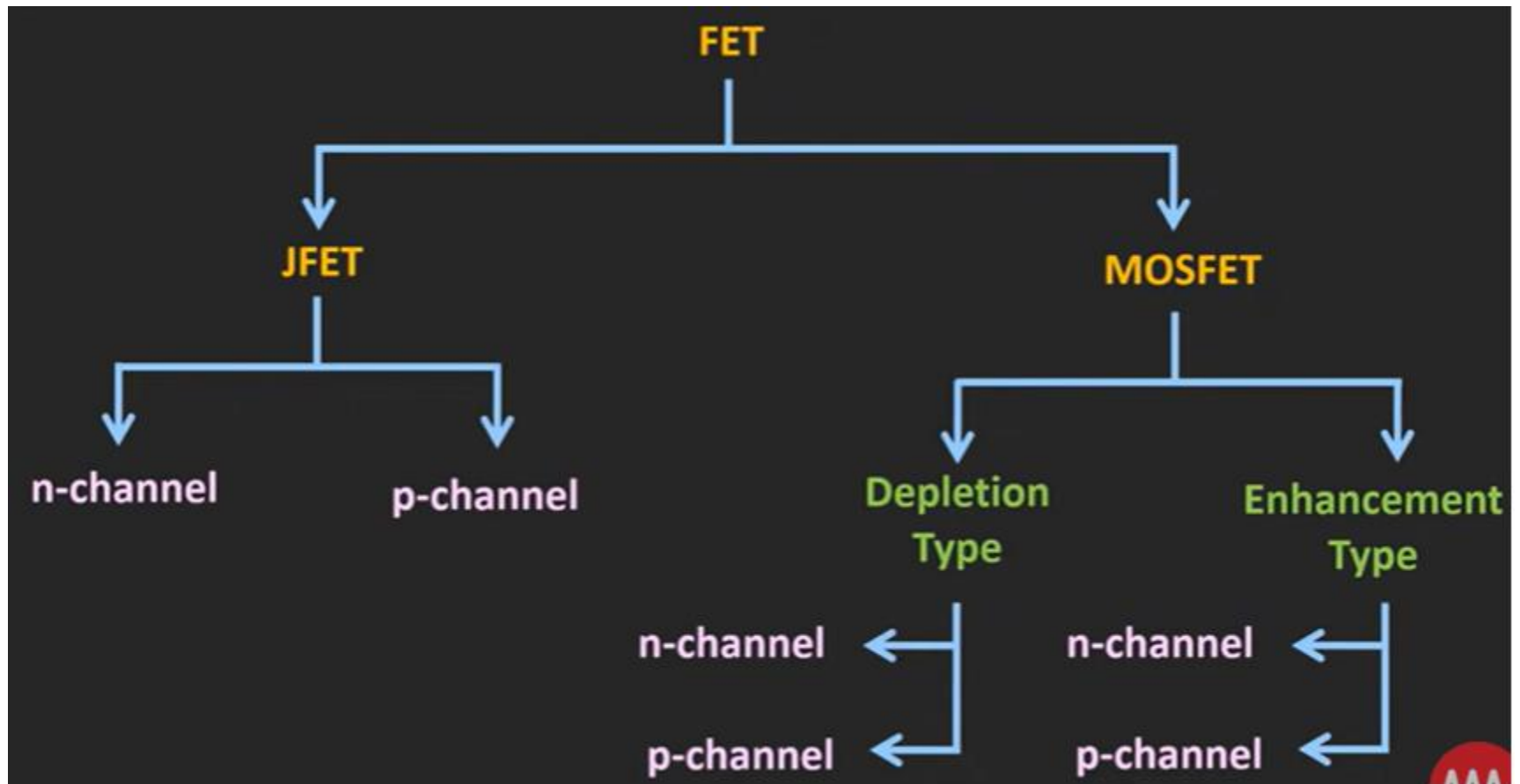


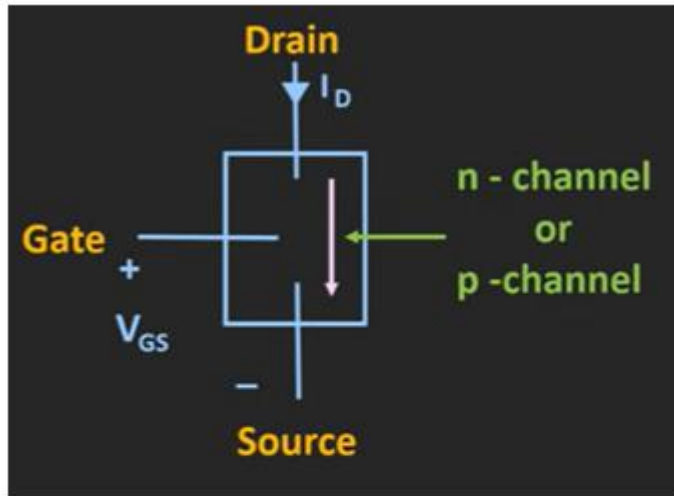

Junction Field Effect Transistor (JFET)

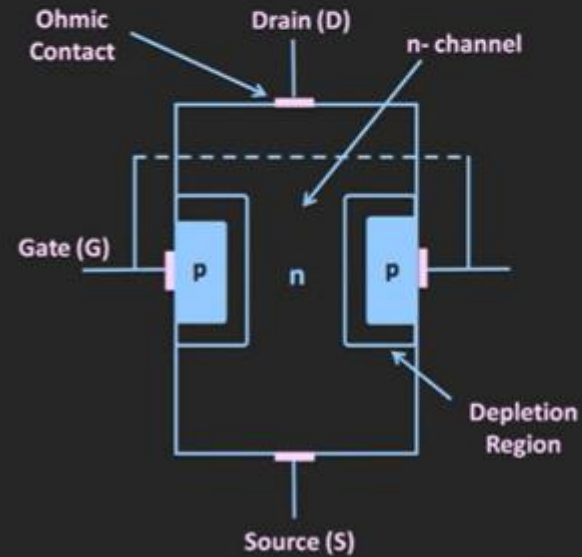


n-channel JFET

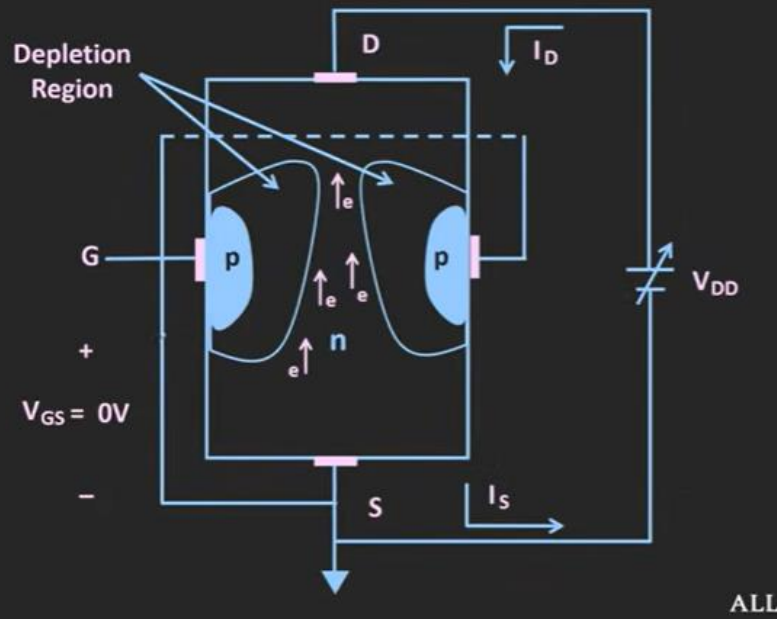


$$I_D = I_S$$

$$V_{GS} = 0 \text{ and } V_{DS} > 0$$

$$I_G = 0$$

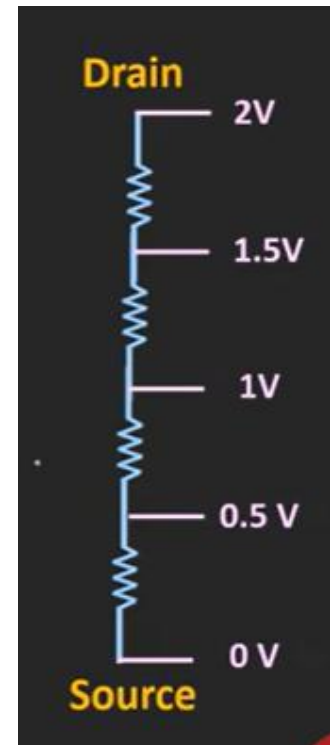

Pinch-off Condition in JFET

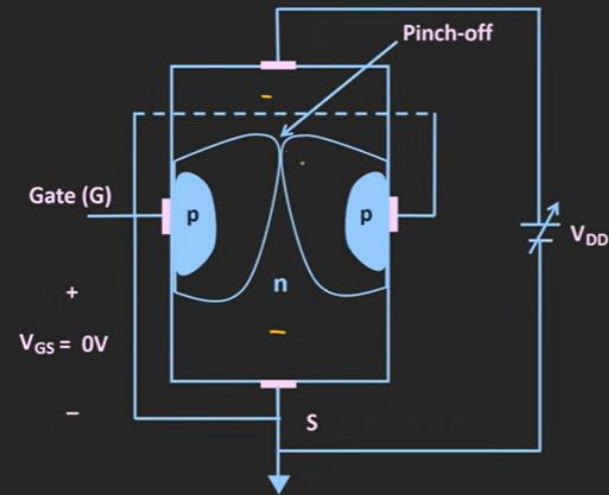


$$V_{GS} = 0 \text{ and } V_{DS} > 0$$

$$V_P$$


$$V_{DS} > V_P$$

n-channel JFET Output Characteristics

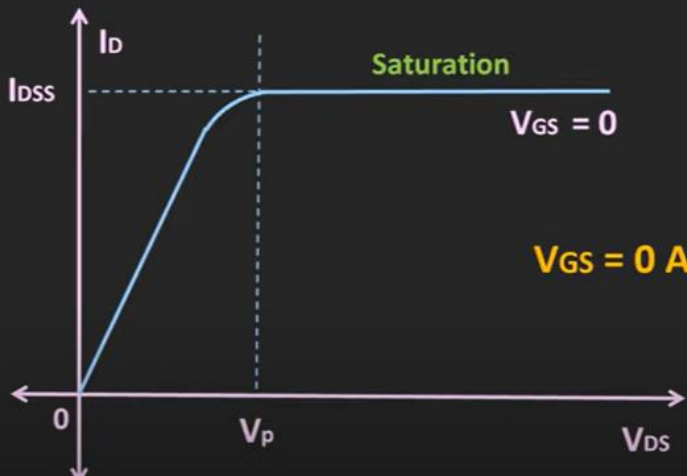

$$V_{GS} = 0 \text{ And } V_{DS} > V_P$$


n-channel JFET Output Characteristics

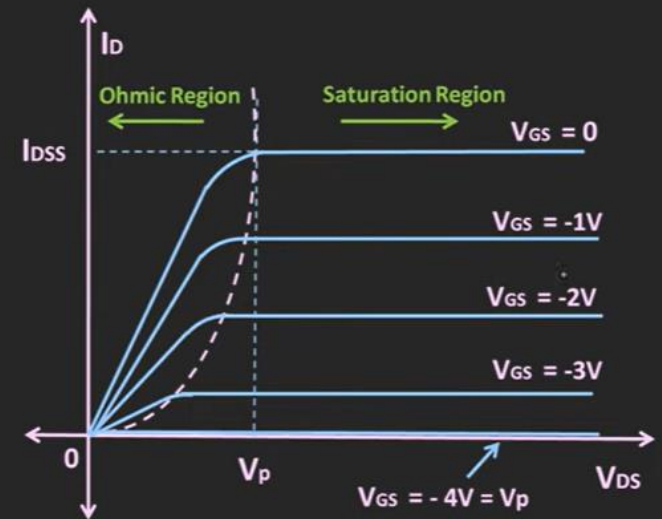


- Ohmic Region = JFET will work as a resistor.
- For Fixed value of V_{gs} it will provide constant resistance.
- Increase V_{gs} resistance will increase. So it can work as variable resistor.
- $V_{gs} \geq V_p$, $I_d=0$. cut off device is off.




n-channel JFET Output Characteristics

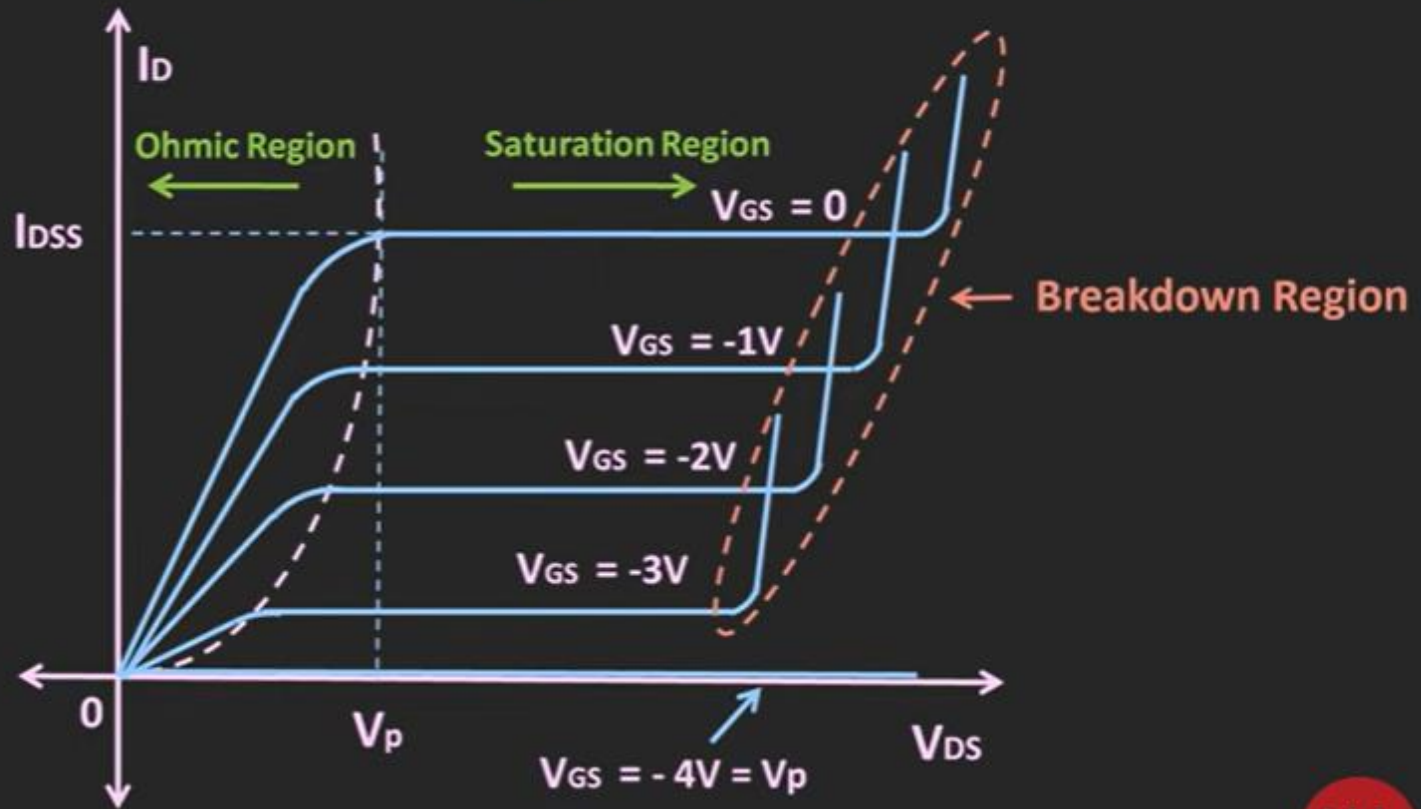


p-channel JFET

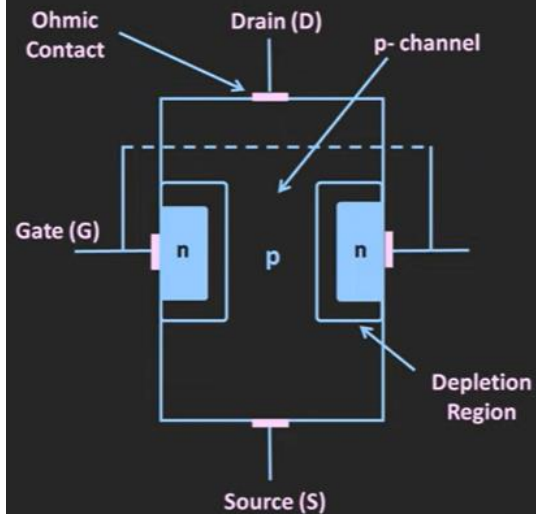

p-channel JFET

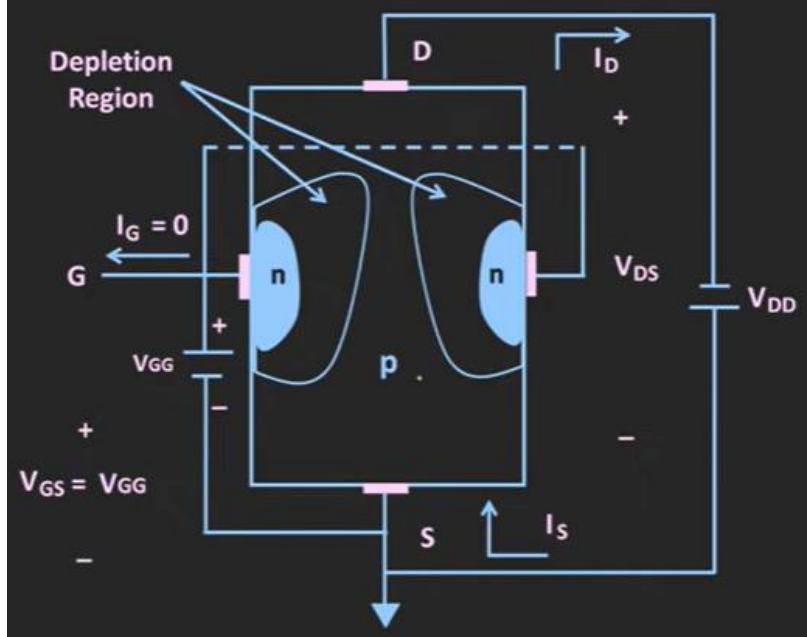

p-channel JFET Output Characteristics

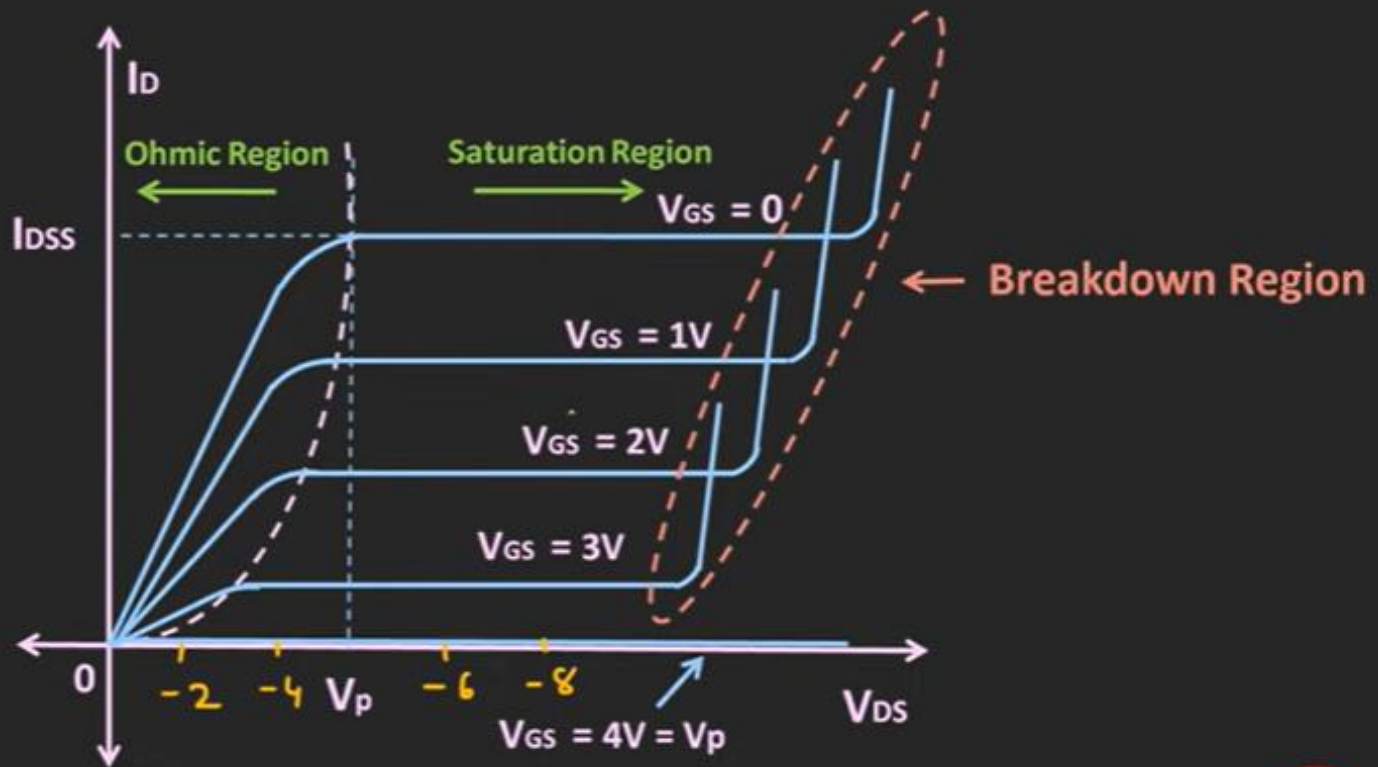

JFET OPERATING CHARACTERISTICS: VOLTAGE CONTROLLED RESISTOR

- The region to the left of the pinch-off point is called the ohmic region.
- The slope of each curve and therefore the resistance of the device between drain and source for $V_{DS} < V_P$ is a function of the applied voltage V_{GS} .
- As V_{GS} becomes more negative, the resistance (r_d) increases.
- The JFET can be used as a variable resistor, where V_{GS} controls the drain-source resistance (r_d).

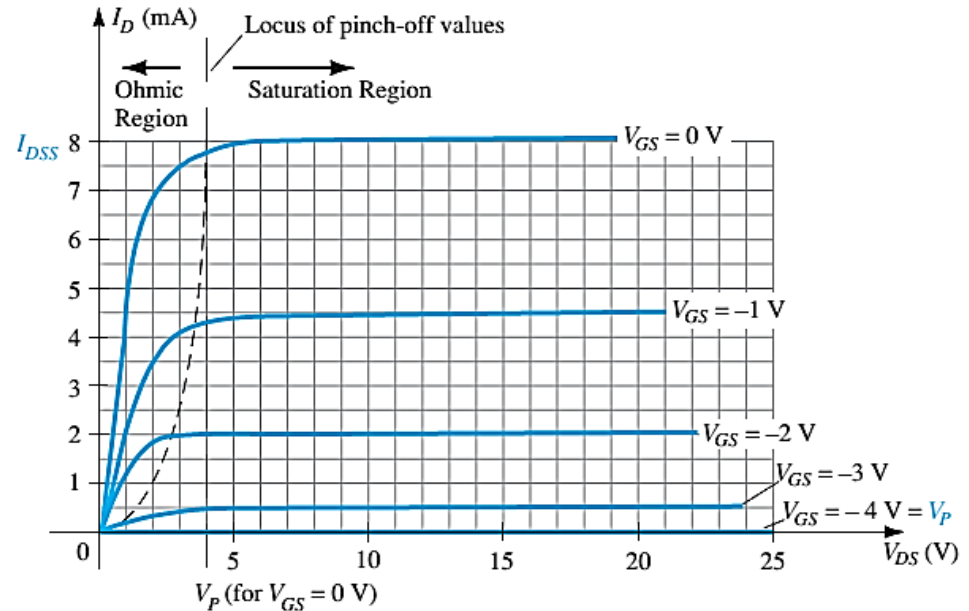


FIG. 6.11

n-Channel JFET characteristics with $I_{DSS} = 8\text{ mA}$ and $V_P = -4\text{ V}$.

$$r_d = \frac{r_o}{(1 - V_{GS}/V_P)^2}$$

Graphical Symbol



n- channel JFET



p- channel JFET

Graphical Symbol



n- channel JFET



p- channel JFET

