

Review Last Class



APPLICATION OF COMPLEX NUMBERS IN AC CIRCUIT

Instantaneous Form (Time Domain) Equation:

$$\begin{aligned} e(t) &= E_m \sin(\omega t + \theta_e) \text{ V} \\ v(t) &= V_m \sin(\omega t + \theta_v) \text{ V} \\ i(t) &= I_m \sin(\omega t + \theta_i) \text{ A} \end{aligned}$$

Phasor Form (Polar Form) Equation:

$$\begin{aligned} \mathbf{E} = \vec{E} &= E_{rms} \angle \theta_e = E \angle \theta_e \text{ V} \\ \mathbf{V} = \vec{V} &= V_{rms} \angle \theta_v = V \angle \theta_v \text{ V} \\ \mathbf{I} = \vec{I} &= I_{rms} \angle \theta_i = I \angle \theta_i \text{ A} \end{aligned}$$

Rectangular Form (Cartesian Form) Equation:

$$\begin{aligned} \mathbf{E} = \vec{E} &= E_r + jE_i \text{ V} \\ \mathbf{V} = \vec{V} &= V_r + jV_i \text{ V} \\ \mathbf{I} = \vec{I} &= I_r + jI_i \text{ A} \end{aligned}$$

IMPEDANCE

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = Z \angle \theta_z = R + jX \ \Omega$$

$$Z = \frac{V_m}{I_m} = \frac{V_{rms}}{I_{rms}} = \frac{V}{I} \ \Omega$$

$$\theta_z = \theta_v - \theta_i$$

$$X_L = \omega L = 2\pi fL \ [\Omega]$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} \ [\Omega]$$

ADMITTANCE

$$\mathbf{Y} = \frac{1}{\mathbf{Z}} = \frac{\mathbf{I}}{\mathbf{V}} = Y \angle \theta_y = G + jB \text{ S}$$

$$Y = \frac{1}{Z} = \frac{I_m}{V_m} = \frac{I_{rms}}{V_{rms}} = \frac{I}{V} \text{ S}$$

$$\theta_y = -\theta_z = \theta_i - \theta_v$$

$$G = \frac{1}{R} = Y \cos \theta_y \text{ S}$$

$$B = \frac{1}{X} = Y \sin \theta_y \text{ S}$$

$$B_L = \frac{1}{X_L} = \frac{1}{\omega L} = \frac{1}{2\pi fL} \text{ [S]}$$

$$B_C = \frac{1}{X_C} = \omega C = 2\pi fC \text{ [S]}$$

EXAMPLE The supply voltage and impedance of a circuit are $v(t) = 282.84\cos 314t$ V and $Z = 20\Omega\angle 60^\circ$. Find the current $i(t)$.

Solution: Converting voltage from cosine to sine, we have: $v(t) = 282.84\sin(314t+90^\circ)$ V.

Now, $V_m = 282.84$ V, $\theta_v = 90^\circ$ and $Z = 20\Omega$, $\theta_z = 60^\circ$

We know that: $Z = \frac{V_m}{I_m}$ $\theta_z = \theta_v - \theta_i$

$$I_m = \frac{V_m}{Z} = \frac{282.84}{20} = 14.142 \text{ A}$$

$$\theta_i = \theta_v - \theta_z = 90^\circ - 60^\circ = 30^\circ$$

Thus, $i(t) = 14.142\sin(314t + 30^\circ)$ A

EXAMPLE The supply current and impedance of a circuit are $i(t) = 15\sin 377t$ V and $Z = 17.32 + j10\Omega$. Find the voltage $v(t)$.

Solution: Converting impedance from Cartesian to Polar form:

$$Z = 17.32 + j10\Omega = 20\Omega\angle 30^\circ$$

Now, $I_m = 15$ V, $\theta_i = 0^\circ$ and $Z = 20\Omega$, $\theta_z = 30^\circ$

We know that: $Z = \frac{V_m}{I_m}$ $\theta_z = \theta_v - \theta_i$

$$V_m = ZI_m = 20 \times 15 = 300 \text{ V}$$

$$\theta_v = \theta_i + \theta_z = 0^\circ + 30^\circ = 30^\circ$$

Thus, $v(t) = 300\sin(377t + 30^\circ)$ V

POWER CALCULATION IN AC CIRCUIT

Instantaneous Power $[p(t)]$

Let, instantaneous voltage and current are:

$$v(t) = V_m \sin(\omega t + \theta_v) \quad [\text{V}]$$

$$i(t) = I_m \sin(\omega t + \theta_i) \quad [\text{A}]$$

By shifting the angle θ_i the instantaneous voltage and current are:

$$v(t) = V_m \sin(\omega t + \theta) \quad [\text{V}]$$

$$i(t) = I_m \sin \omega t \quad [\text{A}]$$

where, $\theta = \theta_z = (\theta_v - \theta_i)$

and θ is called **Power Factor Angle**.

The instantaneous power is as follows:

$$p(t) = v(t)i(t) = V_m \sin(\omega t + \theta) I_m \sin \omega t \quad [\text{W}]$$

After simplification, the instantaneous power can be written as:

$$p(t) = \underbrace{P(1 - \cos 2\omega t)}_{\text{Active Power}} + \underbrace{Q \sin 2\omega t}_{\text{Reactive Power}}$$

$$\text{where, } P = \frac{V_m I_m}{2} \cos \theta \quad \text{W} \qquad Q = P_x = \frac{V_m I_m}{2} \sin \theta \quad \text{Var}$$

$$P = V_{rms} I_{rms} \cos \theta = VI \cos \theta \quad \text{W} \qquad (14.13)$$

$$Q = V_{rms} I_{rms} \sin \theta = VI \sin \theta \quad \text{Var} \qquad (19.12)$$

$$\therefore V = \frac{V_m}{\sqrt{2}} \quad I = \frac{I_m}{\sqrt{2}}$$

The first term [$P(1 - \cos 2\omega t)$] in the preceding equation is called **instantaneous real** [or **true** or **active** or **wattfull** or **useful**] power.

The unit of instantaneous real power is watt [**W**].

The second term [$Q \sin 2\omega t$] in the preceding equation is called **instantaneous reactive volt-ampere** or **instantaneous reactive** [or **imaginary** or **wattless** or **useless** or **quadrature**] power.

The unit of instantaneous reactive power is volt-ampere reactive [**Var**].

Power (or Average or Real or Active or True or Wattfull or Usefull Power)

The average value can be obtained by:

$$P_{ave} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T [P(1 - \cos 2\omega t) + Q \sin 2\omega t] dt = P = \frac{V_m I_m}{2} \cos \theta = VI \cos \theta \quad \text{W}$$

The average power is also called *real/active/true/wattfull/usefull power* or simply **Power**. The **unit** of real power is **watt**. The real power is measured by **wattmeter**.

Real power converts from electrical energy to other form of energy. This is happened in resistive circuit.

Reactive or Imaginary or Quadrature or Wattless or Useless Power (or Reactive Volt-Ampere)

The **peak or maximum value of instantaneous reactive power** (or instantaneous reactive volt-ampere) is called the *reactive/imaginary/quadrature/wattless/useless power* (or *reactive volt-ampere*). The **unit** of reactive power is called **var** (reactive volt-ampere). The reactive power is measured by **varmeter**. It is given by:

$$Q = P_x = \frac{V_m I_m}{2} \sin \theta \quad [\text{var}] = VI \sin \theta \quad [\text{var}]$$

Reactive power is used for storing energy. This is happened in inductive and capacitive circuit.

Reactive power is **positive** (for **Inductive load**) or **negative** (for **Capacitive load**).

Apparent Power or Volt-Ampere

Apparent power is the product of the rms value of voltage and the rms value of current.

The **unit** of apparent power is called **VA (volt-ampere)**.

$$S = \sqrt{P^2 + Q^2} \quad [\text{VA}] = \frac{V_m I_m}{2} \quad [\text{VA}]$$
$$= V_{rms} I_{rms} = VI \quad [\text{VA}]$$

Power Factor

Cosine θ ($\cos \theta$) which is a factor, by which volt-amperes are multiplied to give power, is called power factor. Power factor is always **positive**. Power factor can be given by:

$$pf = F_p = \cos \theta = \cos \theta_z = \frac{P}{S} \quad 0 \leq pf \leq 1$$

Unity Power Factor: If $\theta = \theta_z = \theta_v - \theta_i = 0^\circ$ the **power factor is 1** which is called **unity power factor**.

Lagging Power Factor: If $\theta = \theta_z = \theta_v - \theta_i > 0^\circ$ then **current lags** voltage which is called **lagging power factor**.

Leading Power Factor: If $\theta = \theta_z = \theta_v - \theta_i < 0^\circ$ then **current leads** voltage which is called **leading power factor**.

Reactive Factor

Sine θ ($\sin \theta$) which is a factor, by which volt-amperes are multiplied to give reactive power, is called reactive factor.

Reactive factor may be **positive** (for Inductive load) or **negative** (for Capacitive load). Reactive factor can be given by:

$$rf = F_q = \sin \theta = \sin \theta_z = \frac{Q}{S} \quad -1 \leq rf \leq 1$$

Complex Power

Voltage and Current in Cartesian Form

$$V = V\angle\theta_v = V \cos \theta_v + jV \sin \theta_v = V_r + jV_i$$

$$V_r = V \cos \theta_v; \quad V_i = V \sin \theta_v$$

$$I = I\angle\theta_i = I \cos \theta_i + jI \sin \theta_i = I_r + jI_i$$

$$I_r = I \cos \theta_i; \quad I_i = I \sin \theta_i$$

Real or Active or Average Power

$$P = VI \cos \theta = VI \cos(\theta_v - \theta_i)$$

$$= VI \cos \theta_v \cos \theta_i + VI \sin \theta_v \sin \theta_i = V_r I_r + V_i I_i$$

Reactive or Imaginary or Quadrature Power

$$Q = VI \sin \theta = VI \sin(\theta_v - \theta_i)$$

$$= VI \sin \theta_v \cos \theta_i - VI \cos \theta_v \sin \theta_i = V_i I_r - V_r I_i$$

Complex Power by Conjugate Current

Using the previous equations of P and Q , the complex power can be written as follows:


$$S = P + jQ = (V_r I_r + V_i I_i) + j(V_i I_r - V_r I_i)$$

$$S = P + jQ = (V_r + jV_i)(I_r - jI_i) = \mathbf{VI}^* = S\angle\theta_s$$


$$P = \text{Re}[S] = \text{Re}[\mathbf{VI}^*]; \quad Q = \text{Im}[S] = \text{Im}[\mathbf{VI}^*]$$

Power Triangle

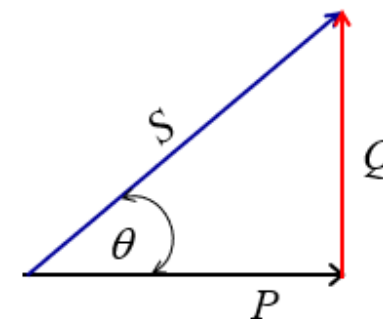Graphical representation of **active power**, **reactive power**, and **apparent power** in a complex plane is called power triangle.



When Q is Positive

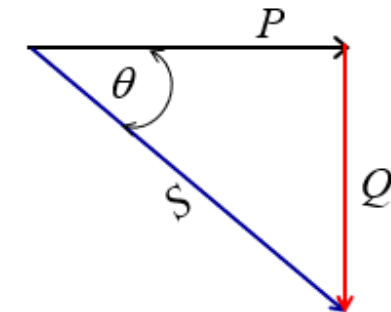

When Q is Negative

EXAMPLE Determine the power factor, the reactive factor and indicate whether power factor is leading or lagging for the following input voltage and current pairs of a network:

(a) $v(t) = 150\sin(377t + 70^\circ) \text{ V}$

$i(t) = 3\sin(377t + 10^\circ) \text{ A}$

(b) $v(t) = 100\sin(314t - 50^\circ) \text{ V}$

$i(t) = 12\sin(314t + 40^\circ) \text{ A}$

(c) $v(t) = 120\sin(157t + 30^\circ) \text{ V}$

$i(t) = 8\cos(157t - 110^\circ) \text{ A}$

(d) $v(t) = -80\cos(200t + 60^\circ) \text{ V}$

$i(t) = 5\sin(200t - 30^\circ) \text{ A}$

Solution: (a) Here, $\theta_v = 70^\circ$ and $\theta_i = 10^\circ$, thus
 $\theta = \theta_v - \theta_i = 70^\circ - 10^\circ = 60^\circ$

$pf = \cos \theta = \cos(60^\circ) = \mathbf{0.5 \text{ lagging}}$

$rf = \sin \theta = \sin(60^\circ) = \mathbf{0.866}$

(b) Here, $\theta_v = -50^\circ$ and $\theta_i = 40^\circ$, thus

$\theta = \theta_v - \theta_i = -50^\circ - (40^\circ) = -90^\circ$

$pf = \cos \theta = \cos(-90^\circ) = \mathbf{0 \text{ leading power factor}}$

$rf = \sin \theta = \sin(-90^\circ) = \mathbf{-1}$

(c) $i(t) = 8\cos(157t - 110^\circ) = 8\sin(157t + 90^\circ - 150^\circ) \text{ A}$

$i(t) = 8\sin(157t - 60^\circ) \text{ A}$

Here, $\theta_v = 30^\circ$ and $\theta_i = -60^\circ$, thus

$\theta = \theta_v - \theta_i = 30^\circ - (-60^\circ) = 90^\circ$

$pf = \cos \theta = \cos(90^\circ) = \mathbf{0 \text{ lagging power factor}}$

$rf = \sin \theta = \sin(90^\circ) = \mathbf{1}$

(d) $v(t) = -80\cos(200t + 60^\circ) = 80\sin(200t - 90^\circ + 60^\circ) \text{ V}$

$v(t) = 80\sin(200t - 30^\circ) \text{ V}$

Here, $\theta_v = -30^\circ$ and $\theta_i = -30^\circ$, thus

$\theta = \theta_v - \theta_i = -30^\circ - (-30^\circ) = 0^\circ$

$pf = \cos \theta = \cos(0^\circ) = \mathbf{1 \text{ unity power factor}}$

$rf = \sin \theta = \sin(0^\circ) = \mathbf{0}$

EXAMPLE The supply voltage and current of a circuit are $v(t) = 100\sin(314t + 80^\circ)$ V and $i(t) = 12\sin(377t + 50^\circ)$ A.

- (a) Calculate the power factor, the reactive factor and comment on the power factor.
- (b) Calculate the power, the reactive power and the apparent power delivered by source.
- (c) Write the instantaneous power equation.
- (d) Draw the power triangle.

Solution: (a) Here, $\theta_v = 80^\circ$ and $\theta_i = 50^\circ$, thus
 $\theta = \theta_v - \theta_i = 80^\circ - 50^\circ = 30^\circ$

$$pf = \cos \theta = \cos(30^\circ) = \mathbf{0.866}$$

$$rf = \sin \theta = \sin(30^\circ) = \mathbf{0.5}$$


$$(b) P = \frac{V_m I_m}{2} \cos \theta = VI \cos \theta = \frac{100 \times 12}{2} \times 0.866 = \mathbf{519.6 \text{ W}}$$

$$Q = \frac{V_m I_m}{2} \sin \theta = VI \sin \theta = \frac{100 \times 12}{2} \times 0.5 = \mathbf{300 \text{ Var}}$$

$$S = \frac{V_m I_m}{2} = VI = \frac{100 \times 12}{2} = \mathbf{600 \text{ VA}}$$

$$(c) p(t) = P(1 - \cos 2\omega t) + Q \sin 2\omega t \text{ W} \\ = 519.6(1 - \cos 754t) + 300 \sin 754t \text{ W}$$

(d) Power triangle:

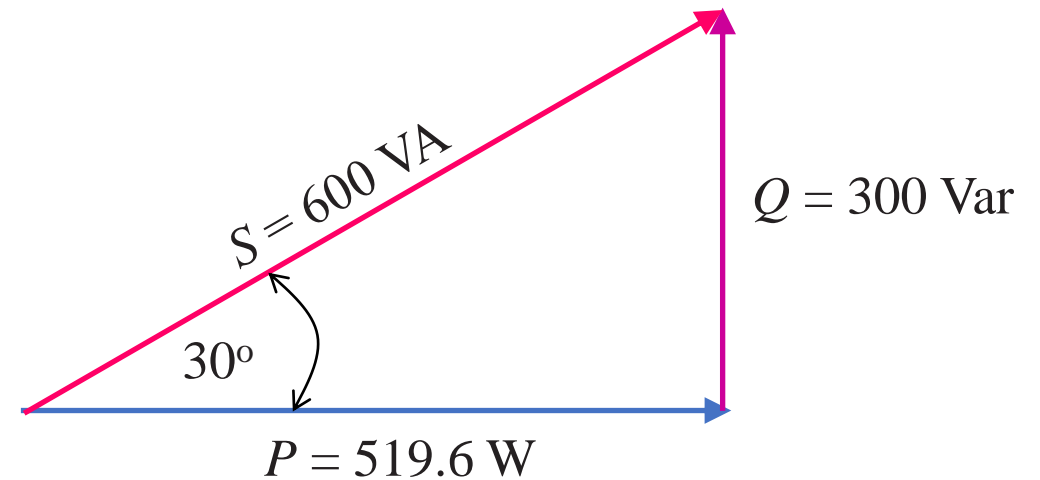

EXAMPLE The supply voltage and current of a circuit are $V = 150V \angle 50^\circ$ and $I = 5A \angle 110^\circ$.

- (a) Calculate the complex power and represent it in both polar and cartesian forms.
- (b) From the result of (a), find the real power, the reactive power and the apparent power.
- (c) Calculate the power factor and the reactive factor and make comment on power factor.
- (d) Write the instantaneous power equation for the 400 rad/s of source voltage.
- (e) Draw the power triangle.

Solution: (a) $S = VI^* = (150V \angle 50^\circ)(5A \angle 110^\circ)^*$
 $= (150V \angle 50^\circ)(5A \angle -110^\circ)$
 $= 750VA \angle -60^\circ$
 $= 375 - j649.52 VA = P + jQ$

(b) From (a) we have:


$$P = 375 \text{ W}, Q = -649.52 \text{ Var and } S = 750 \text{ VA}$$

(c) $pf = \frac{P}{S} = \frac{375 \text{ W}}{750 \text{ VA}} = \mathbf{0.5 \text{ Leading}}$

$$rf = \frac{Q}{S} = \frac{-649.52 \text{ Var}}{750 \text{ VA}} = \mathbf{-0.866}$$


(d) $p(t) = P(1 - \cos 2\omega t) + Q\sin 2\omega t \text{ W}$
 $= 375(1 - \cos 800t) - 649.52\sin 800t \text{ W}$

(e) Power triangle:

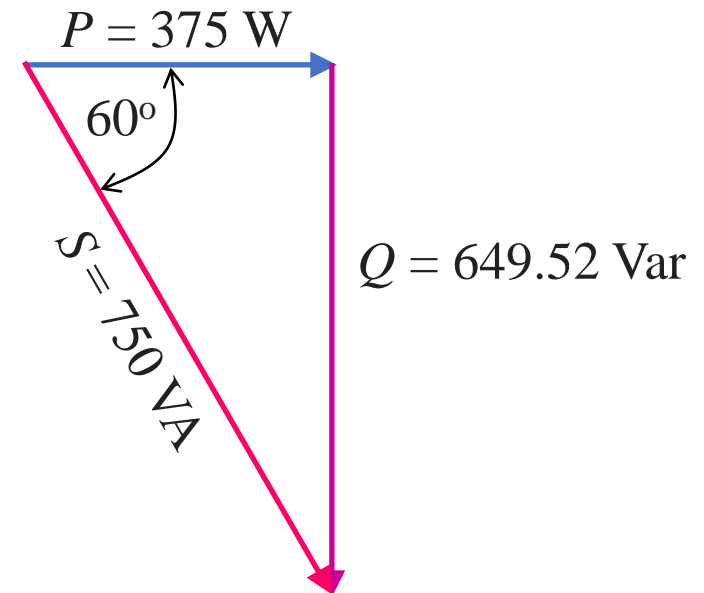


Theory Related To
Pure Resistive, Pure Inductive and
Pure Capacitive Circuits
Based on Instantaneous Equations


PURE RESISTIVE CIRCUIT

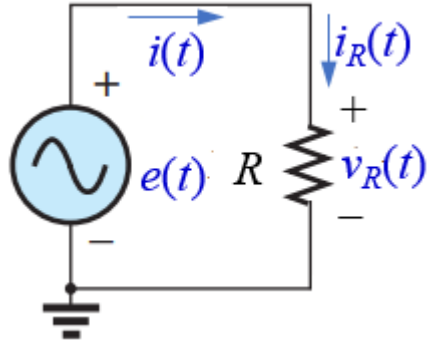

PURE INDUCTIVE CIRCUIT

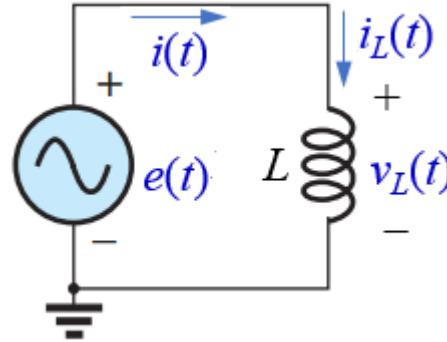

PURE CAPACITIVE CIRCUIT

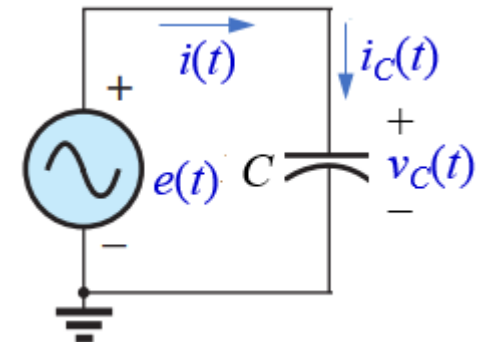

Instantaneous or Transient or Time-domain Voltage and Current Relation

$$v_R(t) = Ri_R(t) \quad i_R(t) = \frac{v_R(t)}{R}$$

$$v_R(t) = e(t) \quad i_R(t) = i(t)$$

$$v_L(t) = L \frac{di_L(t)}{dt} \quad i_L(t) = \frac{1}{L} \int v_L(t) dt$$

$$v_L(t) = e(t) \quad i_L(t) = i(t)$$

$$v_C(t) = \frac{1}{C} \int i_C(t) dt \quad i_C(t) = C \frac{dv_C(t)}{dt}$$

$$v_C(t) = e(t) \quad i_C(t) = i(t)$$

Let, the input is $e(t) = E_m \sin(\omega t + \theta_e)$ V; according to KVL and KCL, we have:

$$i(t) = \frac{E_m}{R} \sin(\omega t + \theta_e)$$

$$i(t) = \frac{E_m}{L} \int \sin(\omega t + \theta_e) dt$$

$$= \frac{E_m}{X_L} \sin(\omega t + \theta_e - 90^\circ)$$


where, $X_L = \omega L = 2\pi fL \, \Omega$

$$i(t) = C \frac{d}{dt} [E_m \sin(\omega t + \theta_e)]$$


$$= \frac{E_m}{X_C} \sin(\omega t + \theta_e + 90^\circ)$$

where, $X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC} \, \Omega$


PURE RESISTIVE CIRCUIT

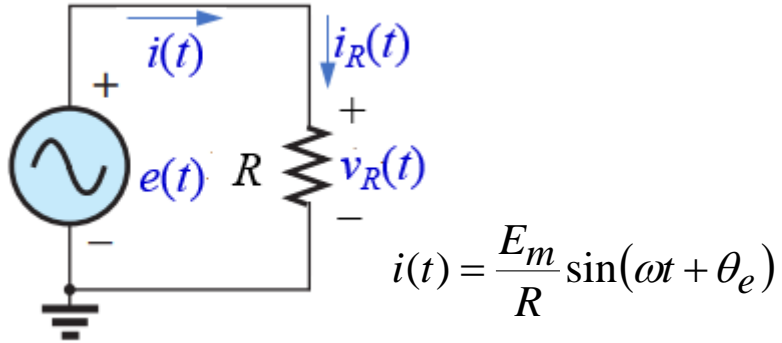

PURE INDUCTIVE CIRCUIT

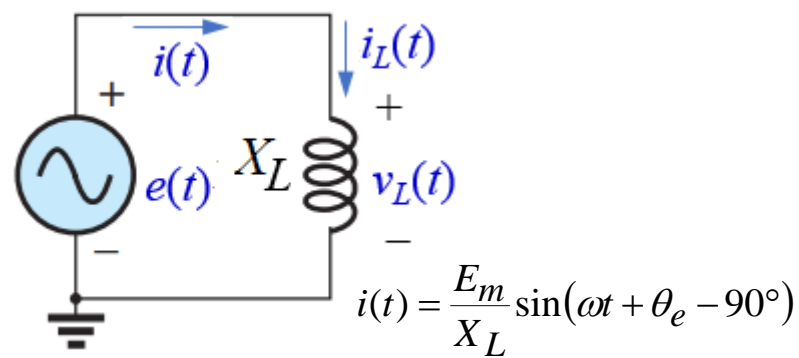

PURE CAPACITIVE CIRCUIT

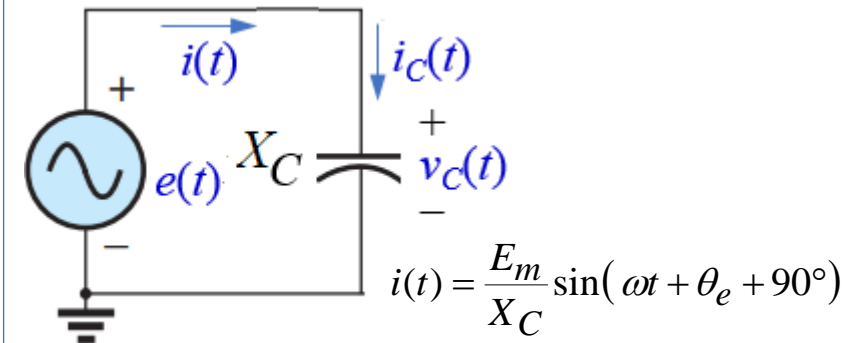

Compare the obtained current equation with **general current equation** of $i(t) = I_m \sin(\omega t + \theta_i)$ A, we have

$$I_m = \frac{E_m}{R} = \frac{V_{Rm}}{R}; \quad \theta_i = \theta_e$$

$$E_m = V_{Rm} = R I_{Rm} = R I_m$$

$$\theta_{vR} = \theta_{iR}$$

V_{Rm} : Peak value of resistor voltage

I_{Rm} : Peak value of resistor current

$$I_m = \frac{E_m}{X_L}; \quad \theta_i = \theta_e - 90^\circ$$

$$E_m = V_{Lm} = X_L I_{Lm} = X_L I_m$$

$$\theta_e = \theta_i + 90^\circ \quad \theta_{vL} = \theta_{iL} + 90^\circ$$

V_{Lm} : Peak value of inductor voltage

I_{Lm} : Peak value of inductor current

$$I_m = \frac{E_m}{X_C}; \quad \theta_i = \theta_e + 90^\circ$$

$$E_m = V_{Cm} = X_C I_{Cm} = X_C I_m$$

$$\theta_e = \theta_i - 90^\circ \quad \theta_{vC} = \theta_{iC} + 90^\circ$$

V_{Cm} : Peak value of capacitor voltage

I_{Cm} : Peak value of capacitor current


Impedance Magnitude and Impedance Angle

$$Z = \frac{E_m}{I_m} = R; \quad \theta_z = \theta_e - \theta_i = 0^\circ$$


$$Z = \frac{E_m}{I_m} = X_L; \quad \theta_z = \theta_e - \theta_i = 90^\circ$$

$$Z = \frac{E_m}{I_m} = X_C; \quad \theta_z = \theta_e - \theta_i = -90^\circ$$


PURE RESISTIVE CIRCUIT

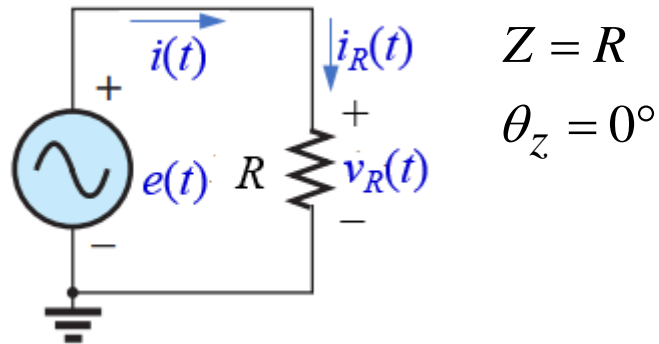


PURE INDUCTIVE CIRCUIT

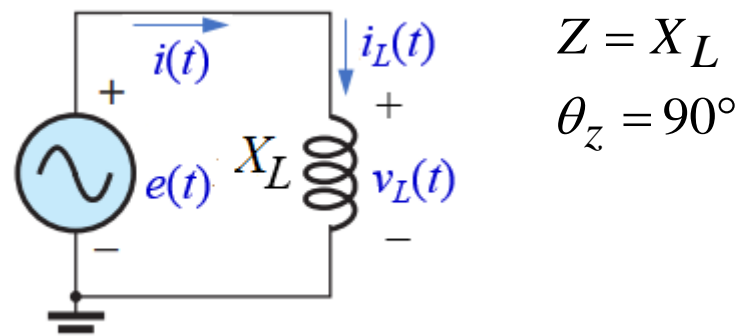


PURE CAPACITIVE CIRCUIT

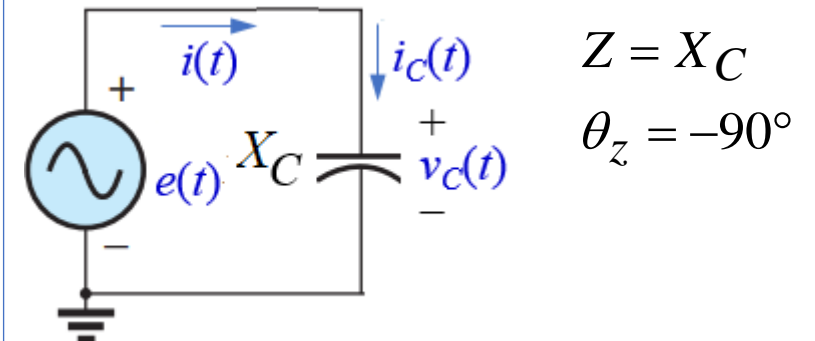

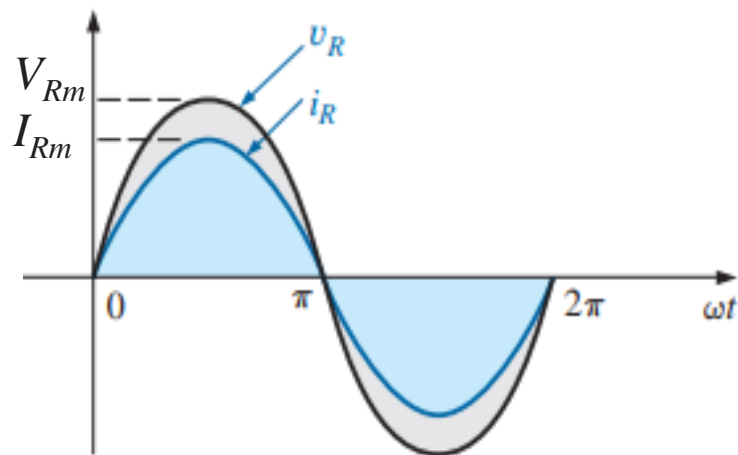
Phase Relation Between Voltage and Current



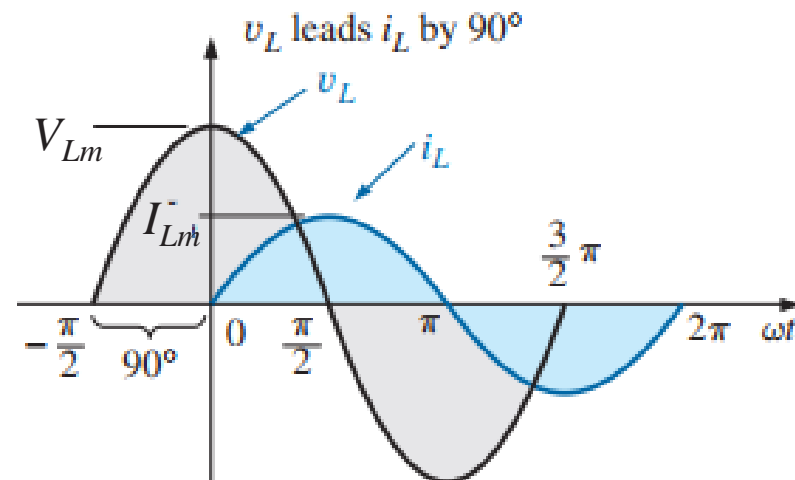The phase difference $v_R(t)$ and $i_R(t)$ is **0°**. $v_R(t)$ and $i_R(t)$ are **in phase**.



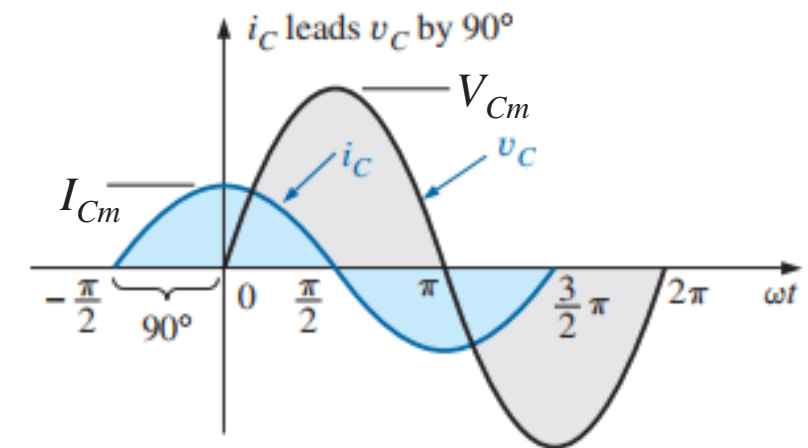The phase difference $v_L(t)$ and $i_L(t)$ is **90°**. $v_L(t)$ **leads** and $i_L(t)$ or $i_L(t)$ **lags** $v_L(t)$.



The phase difference $v_C(t)$ and $i_C(t)$ is **90°**. $v_C(t)$ **lags** and $i_C(t)$ or $i_C(t)$ **leads** $v_C(t)$.

X_L VERSUS FREQUENCY (f) CURVE

Inductive reactance is **directly proportional** to frequency ($X_L \propto f$) so the inductive reactance versus frequency curve is a straight line with slope equal to $2\pi L$.

If frequency **decreases**, inductive reactance will be **decreases**.
If frequency **increases**, inductive reactance will be **increases**.

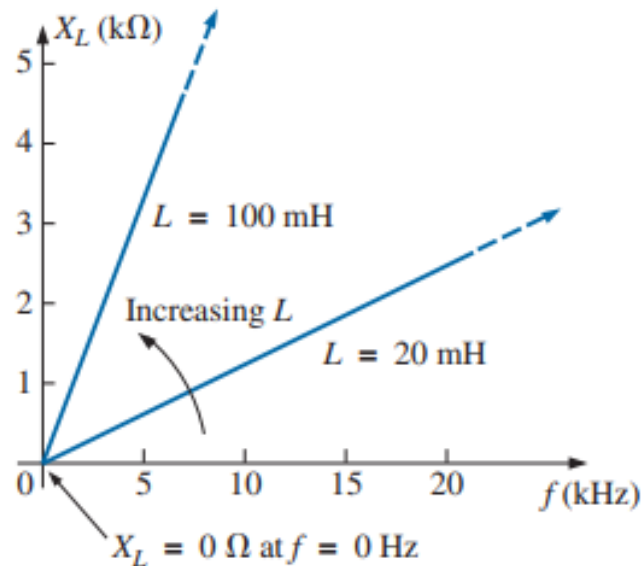


FIG. 14.20 X_L versus frequency.

Inductive Reactance With DC Supply

For DC voltage the **frequency is zero** so inductive reactance with DC supply is **zero** that means inductor behave as a **short-circuit** with DC input.

X_C VERSUS FREQUENCY (f) CURVE

Capacitive reactance is **inversely proportional** to frequency ($X_C \propto 1/f$) so the capacitive reactance versus frequency curve is a *rectangular hyperbola*.

If frequency **decreases**, capacitive reactance will be **increases**.
If frequency **increases**, capacitive reactance will be **decreases**.

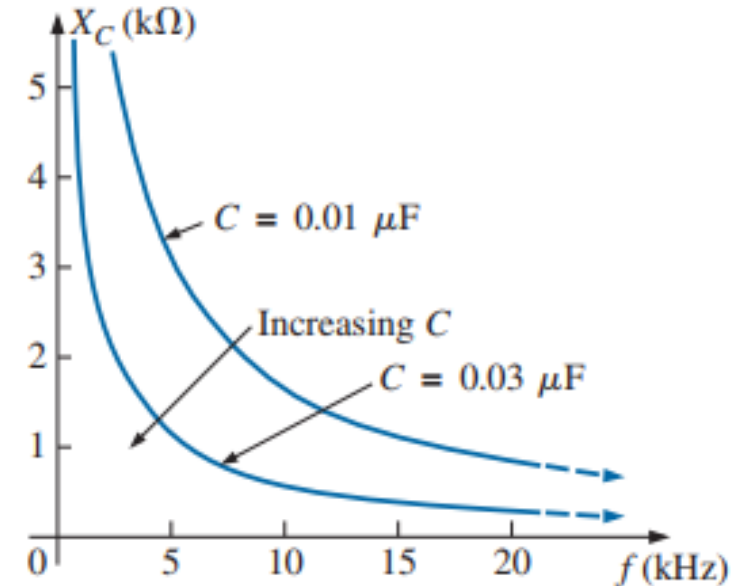


FIG. 14.22 X_C versus frequency.

Capacitive Reactance With DC Supply

For DC voltage the frequency is zero so capacitive reactance with DC supply is **infinity** that means capacitor behave as an **open-circuit** with DC input.

EXAMPLE 14.1 The voltage across a resistor is indicated. Find the sinusoidal expression for the current if the resistor is $10\ \Omega$. Sketch the curves for $v(t)$ and $i(t)$.

$$v(t) = 100\sin 377t\ \text{V}$$

Solution: (a) Given, $V_m = 100\ \text{V}$, $\theta_v = 0^\circ$, $\omega = 377\ \text{rad/s}$ and $R = 10\ \Omega$

For a resistive circuit, we know that

$$I_m = \frac{V_m}{R} \qquad \theta_i = \theta_v$$

$$\text{thus } I_m = \frac{100\text{V}}{10\Omega} = 10\text{ A} \qquad \theta_i = \theta_v = 0^\circ$$

The sinusoidal expression of current is:

$$i(t) = 10\sin 377t\ \text{A}$$

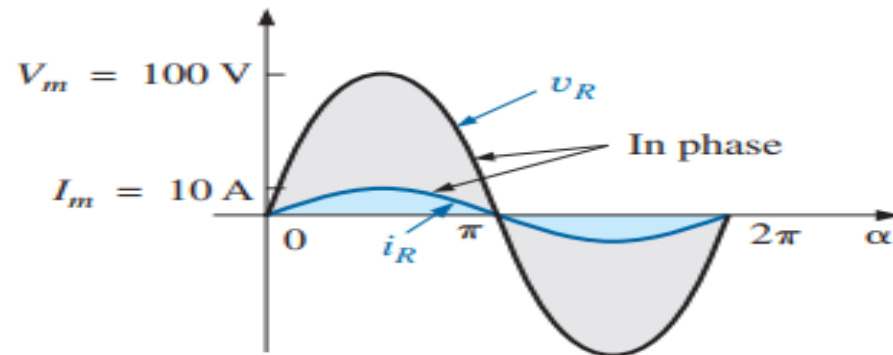


FIG. 14.13 Example 14.1(a).

EXAMPLE 14.2 The current through a $5\ \Omega$ resistor is given. Find the sinusoidal expression for the voltage across the resistor for:

$$i(t) = 40\sin(377t + 30^\circ)\ \text{A}.$$

Solution:

(a) Given, $I_m = 40\ \text{A}$, $\theta_i = 30^\circ$, $\omega = 377\ \text{rad/s}$ and $R = 5\ \Omega$

$$\text{We know that } I_m = \frac{V_m}{R}; \quad \theta_i = \theta_v$$

$$\text{thus } V_m = RI_m = (5\Omega)(40\text{ A}) = 200\ \text{V}$$

$$\theta_v = \theta_i = 30^\circ$$

The sinusoidal expression of voltage is:

$$v(t) = 200\sin(377t + 30^\circ)\ \text{V}$$

Practice Book Problems [Ch. 14] 4 and 5

EXAMPLE 14.3(a) The current through a 0.1 H coil is provided. Find the sinusoidal expression for the voltage across the coil for $i(t) = 10\sin 377t$ A. Sketch the curves for $v(t)$ and $i(t)$.

Solution: (a) Given, $I_m = 10$ A, $\theta_i = 0^\circ$, $\omega = 377$ rad/s and $L = 0.1$ H

We know that, $X_L = \omega L = (377 \text{ rad/s})(0.1 \text{ H}) = 37.3 \Omega$

We know that $I_m = \frac{V_m}{X_L}$; $\theta_i = \theta_v - 90^\circ$

thus $V_m = X_L I_m = (37.3 \Omega)(10 \text{ A}) = 373 \text{ V}$

$$\theta_v = \theta_i + 90^\circ = 90^\circ$$

The sinusoidal expression of voltage is:

$$v(t) = 373\sin(377t + 90^\circ) \text{ V}$$

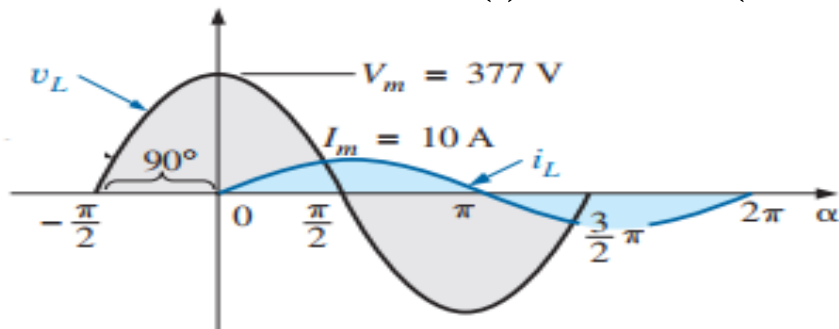


FIG. 14.15 Example 14.3(a).

EXAMPLE 14.4 The voltage across a 0.5 H coil is provided. Find the sinusoidal expression for the current through the coil for $v(t) = 100\sin(20t + 30^\circ)$ V.

Solution: (a) Given, $V_m = 100$ V, $\theta_v = 30^\circ$, and $\omega = 20$ rad/s and $L = 0.5$ H

$$X_L = \omega L = (20 \text{ rad/s})(0.5 \text{ H}) = 10 \Omega$$

We know that $I_m = \frac{V_m}{X_L}$; $\theta_i = \theta_v - 90^\circ$

$$\text{thus } I_m = \frac{100 \text{ V}}{10 \Omega} = 10 \text{ A} \quad \theta_i = 30^\circ - 90^\circ = -60^\circ$$

The sinusoidal expression of current is:

$$i(t) = 10\sin(20t - 60^\circ) \text{ A}$$

Practice Book Problems [Ch. 14] 6 and 12

EXAMPLE 14.5 The voltage across a $1\ \mu\text{F}$ capacitor is provided. Find the sinusoidal expression for the current through the capacitor for $v(t) = 30\sin 400t\ \text{V}$. Sketch the curves for $v(t)$ and $i(t)$.

Solution: (a) Given, $V_m = 30\ \text{V}$, $\theta_v = 0^\circ$, $\omega = 400\ \text{rad/s}$ and $C = 1\ \mu\text{F} = 1 \times 10^{-6}\ \text{F}$

We know that,
$$X_C = \frac{1}{\omega C} = \frac{1}{(400\ \text{rad/s})(1 \times 10^{-6}\ \text{F})} = \frac{10^6}{400}\ \Omega = 2500\ \Omega$$

We know that $I_m = \frac{V_m}{X_C}$; $\theta_i = \theta_v + 90^\circ$

thus
$$I_m = \frac{30\ \text{V}}{2500\ \Omega} = 0.012\ \text{A} = 12\ \text{mA}$$

$$\theta_i = 0^\circ + 90^\circ = 90^\circ$$

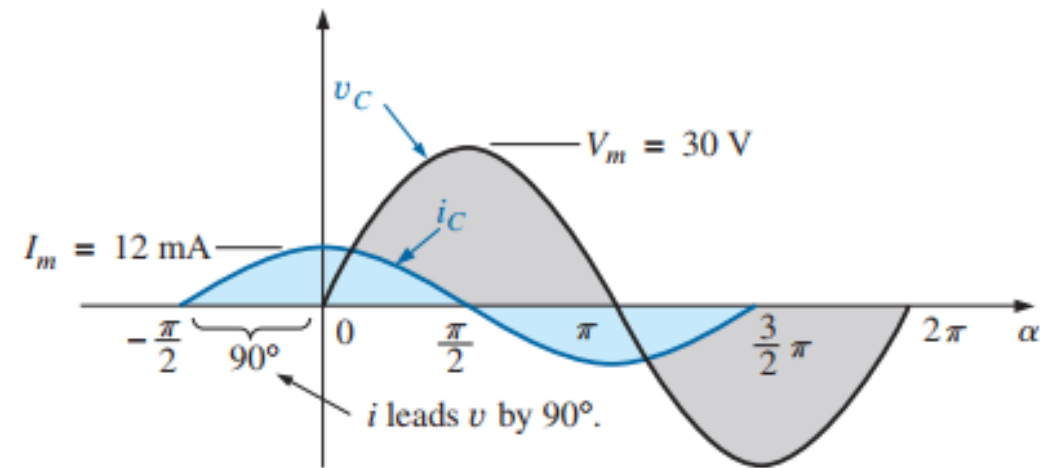


FIG. 14.17 Example 14.5.

The sinusoidal expression of current is:

$$i(t) = 12\sin(20t + 90^\circ)\ \text{mA} = 12 \times 10^{-3}\sin(20t + 90^\circ)\ \text{A}$$

EXAMPLE 14.6 The current through a 100 μF capacitor is given. Find the sinusoidal expression for the voltage across the capacitor for $i(t) = 40\sin(500t + 60^\circ)$ A. Sketch the curves for $v(t)$ and $i(t)$.

Solution: (a) Given, $I_m = 40$ A, $\theta_i = 60^\circ$, $\omega = 500$ rad/s and $C = 100 \mu\text{F} = 100 \times 10^{-6}$ F

$$\text{We know that, } X_C = \frac{1}{\omega C} = \frac{1}{(500 \text{ rad/s})(100 \times 10^{-6} \text{ F})} = \frac{10^6}{5 \times 10^4} \Omega = \frac{10^2}{5} \Omega = 20 \Omega$$

$$\text{We know that } I_m = \frac{V_m}{X_C}; \quad \theta_i = \theta_v + 90^\circ$$

$$\text{thus } V_m = X_C I_m = (20 \Omega)(40 \text{ A}) = 800 \text{ V}$$

$$\theta_v = \theta_i - 90^\circ = 60^\circ - 90^\circ = -30^\circ$$

The sinusoidal expression of voltage is: $v(t) = 800\sin(500t - 30^\circ)$ V

Practice Book Problems [Ch. 14] 13 and 19

EXAMPLE 14.7 For the following pairs of voltages and currents, determine whether the element involved is a capacitor, an inductor, or a resistor. Determine the value of C , L , or R if sufficient data are provided (Fig. 14.18):

- $v = 100 \sin(\omega t + 40^\circ)$
 $i = 20 \sin(\omega t + 40^\circ)$
- $v = 1000 \sin(377t + 10^\circ)$
 $i = 5 \sin(377t - 80^\circ)$
- $v = 500 \sin(157t + 30^\circ)$
 $i = 1 \sin(157t + 120^\circ)$
- $v = 50 \cos(\omega t + 20^\circ)$
 $i = 5 \sin(\omega t + 110^\circ)$

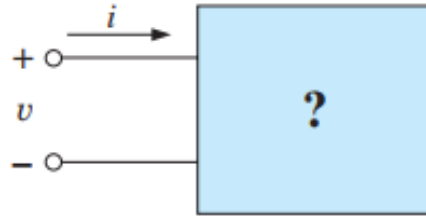


FIG. 14.18 Example 14.7.

Solutions:

- Since v and i are *in phase*, the element is a *resistor*, and

$$R = \frac{V_m}{I_m} = \frac{100 \text{ V}}{20 \text{ A}} = \mathbf{5 \Omega}$$

- Since v *leads* i by 90° , the element is an *inductor*, and

$$X_L = \frac{V_m}{I_m} = \frac{1000 \text{ V}}{5 \text{ A}} = 200 \Omega$$

so that $X_L = \omega L = 200 \Omega$ or

$$L = \frac{200 \Omega}{\omega} = \frac{200 \Omega}{377 \text{ rad/s}} = \mathbf{0.53 \text{ H}}$$

- Since i *leads* v by 90° , the element is a *capacitor*, and

$$X_C = \frac{V_m}{I_m} = \frac{500 \text{ V}}{1 \text{ A}} = 500 \Omega$$

so that $X_C = \frac{1}{\omega C} = 500 \Omega$ or

$$C = \frac{1}{\omega 500 \Omega} = \frac{1}{(157 \text{ rad/s})(500 \Omega)} = \mathbf{12.74 \mu F}$$

- $v = 50 \cos(\omega t + 20^\circ) = 50 \sin(\omega t + 20^\circ + 90^\circ)$
 $= 50 \sin(\omega t + 110^\circ)$

Since v and i are *in phase*, the element is a *resistor*, and

$$R = \frac{V_m}{I_m} = \frac{50 \text{ V}}{5 \text{ A}} = \mathbf{10 \Omega}$$

Practice Book Problems [Ch. 14] 20 and 21


Theory Related To
Pure Resistive, Pure Inductive and
Pure Capacitive Circuits
Based on Complex or Phasor Algebra

PURE RESISTIVE CIRCUIT

PURE INDUCTIVE CIRCUIT

PURE CAPACITIVE CIRCUIT

Circuit in Phasor Notation

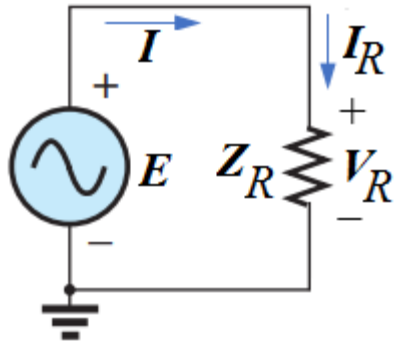


$$\begin{aligned} V_R &= E \\ I_R &= I \\ Z &= Z_R = \frac{V_R}{I_R} \end{aligned}$$

$$V_R = V_R \angle \theta_{vR} \quad I_R = I_R \angle \theta_{iR}$$

$$Z_R = Z_R \angle \theta_{zR} \quad Z_R = \frac{V_R}{I_R} = R$$

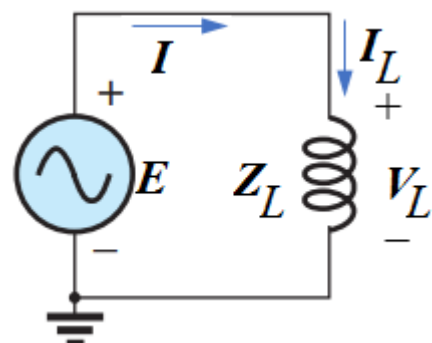V_R : rms value of resistor voltage
 I_R : rms value of resistor current




$$\begin{aligned} V_L &= E \\ I_L &= I \\ Z &= Z_L = \frac{V_L}{I_L} \end{aligned}$$

$$V_L = V_L \angle \theta_{vL} \quad I_L = I_L \angle \theta_{iL}$$

$$Z_L = Z_L \angle \theta_{zL} \quad Z_L = \frac{V_L}{I_L} = X_L$$

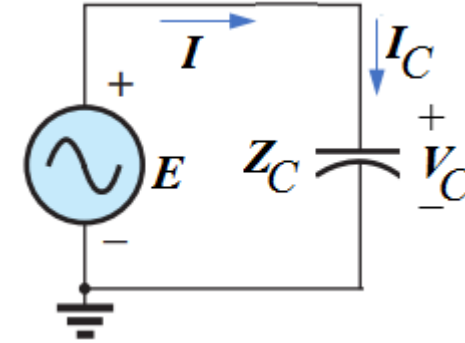V_L : rms value of inductor voltage
 I_L : rms value of inductor current



$$\begin{aligned} V_C &= E \\ I_C &= I \\ Z &= Z_C = \frac{V_C}{I_C} \end{aligned}$$

$$V_C = V_C \angle \theta_{vC} \quad I_C = I_C \angle \theta_{iC}$$

$$Z_C = Z_C \angle \theta_{zC} \quad Z_C = \frac{V_C}{I_C} = X_C$$

V_C : rms value of capacitor voltage
 I_C : rms value of capacitor current

Impedance in Both Polar Form and Cartesian or Rectangular Form

$$Z = Z_R = \frac{V_R}{I_R} \Omega$$




$$Z = Z_R = R \angle 0^\circ \Omega = R + j0 \Omega$$

$$Z = Z_L = \frac{V_L}{I_L} \Omega$$

$$Z = Z_L = X_L \angle 90^\circ \Omega = 0 + jX_L \Omega$$

$$Z = Z_C = \frac{V_C}{I_C} \Omega$$

$$Z = Z_C = X_C \angle -90^\circ \Omega = 0 - jX_C \Omega$$

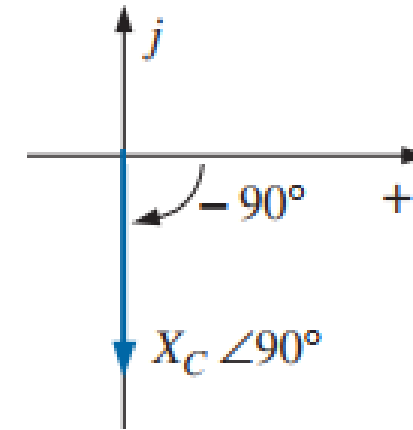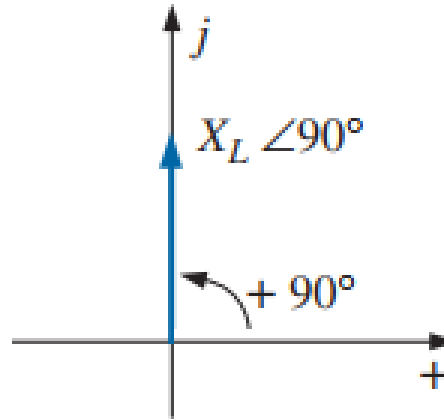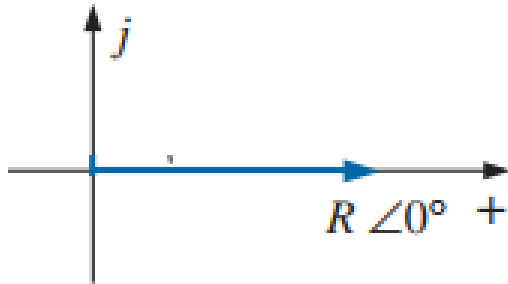PURE RESISTIVE CIRCUIT**PURE INDUCTIVE CIRCUIT****PURE CAPACITIVE CIRCUIT****Impedance Diagram****Admittance in Both Polar Form and Cartesian or Rectangular Form**

$$Y = Y_R = \frac{I_R}{V_R} = \frac{1}{Z_R}$$

$$Y = Y_R = G \angle 0^\circ \text{ S} = G + j0 \text{ S}$$

$$\text{where, } G = \frac{1}{R} \text{ S}$$

$$Y = Y_L = \frac{I_L}{V_L} = \frac{1}{Z_L}$$

$$Y = Y_L = B_L \angle -90^\circ \text{ S} = 0 - jB_L \text{ S}$$

$$\text{where, } B_L = \frac{1}{X_L} \text{ S}$$

$$Y = Y_C = \frac{I_C}{V_C} = \frac{1}{Z_C}$$

$$Y = Y_C = B_C \angle 90^\circ \text{ S} = 0 + jB_C \text{ S}$$




$$\text{where, } B_C = \frac{1}{X_C} \text{ S}$$

PURE RESISTIVE CIRCUIT

PURE INDUCTIVE CIRCUIT

PURE CAPACITIVE CIRCUIT

Admittance Diagram

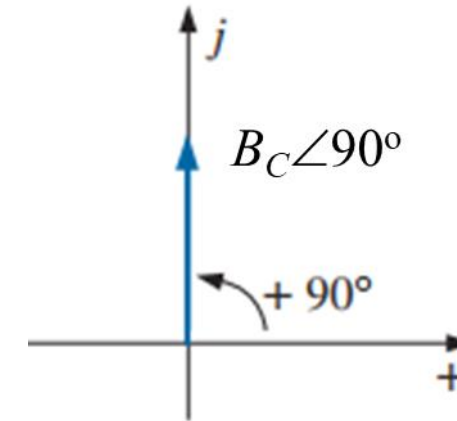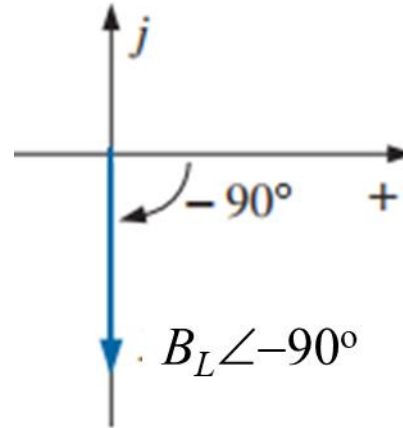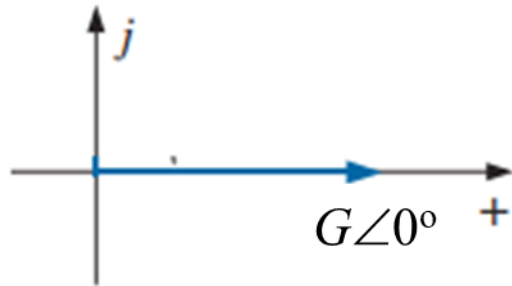

Phasor Diagram

