

REVIEW ON THE LAST CLASS

SOURCE CONVERSIONS

MESH ANALYSIS

NODAL ANALYSIS



8.9 NODAL ANALYSIS (GENERAL APPROACH)

EXAMPLE 8.21 Determine the nodal voltages for the network in Fig. 8.54.


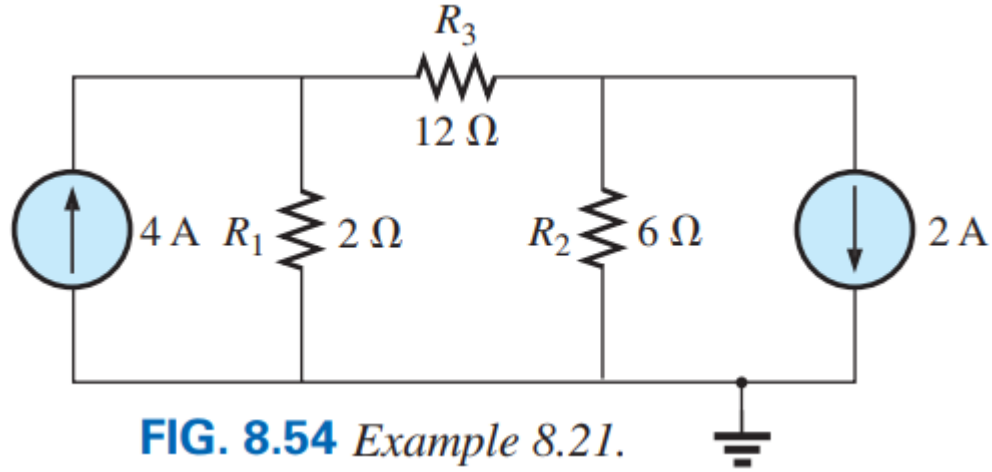


FIG. 8.54 Example 8.21.

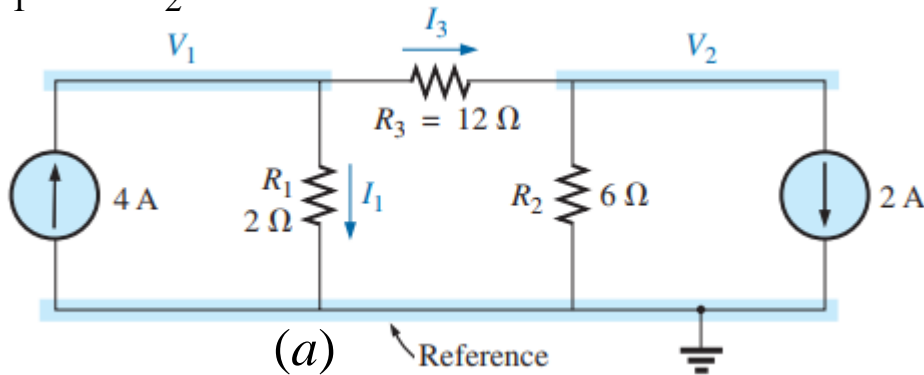
Step 1 and 2: The network has three nodes with the bottom node defined as the reference node (at ground potential, or zero volts), and the other nodes as V_1 and V_2 .



Step 3: For node V_1 , the currents are defined as shown in the following Figure (a) and Kirchhoff's current law is applied:

$$I_1 + I_3 = 4 \quad \left(\frac{1}{2} + \frac{1}{12}\right)V_1 - \left(\frac{1}{12}\right)V_2 = 4 \quad 7V_1 - V_2 = 48$$

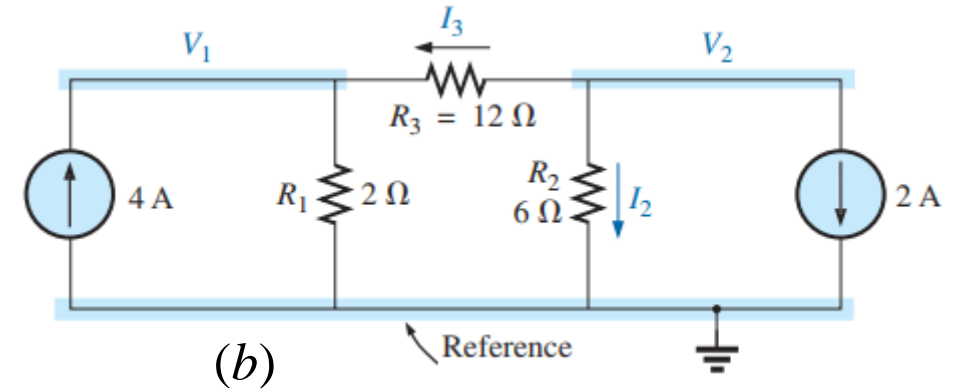For node V_2 , the currents are defined as shown in the following Figure (b) and Kirchhoff's current law is applied:



$$I_2 + I_3 = -2$$

$$\left(\frac{1}{12} + \frac{1}{6}\right)V_2 - \left(\frac{1}{12}\right)V_1 = -2 \quad 3V_2 - V_1 = -24$$

$$7V_1 - V_2 = 48$$

$$-V_1 + 3V_2 = -24$$


$$D = \begin{vmatrix} 7 & -1 \\ -1 & 3 \end{vmatrix} = 21 - 1 = 20$$

$$D_1 = \begin{vmatrix} 48 & -1 \\ -24 & 3 \end{vmatrix} = 144 - 24 = 120$$

$$D_2 = \begin{vmatrix} 7 & 48 \\ -1 & -24 \end{vmatrix} = -168 + 48 = -120$$

$$V_1 = \frac{D_1}{D} = \frac{120}{20} = \mathbf{6 \text{ V}}$$
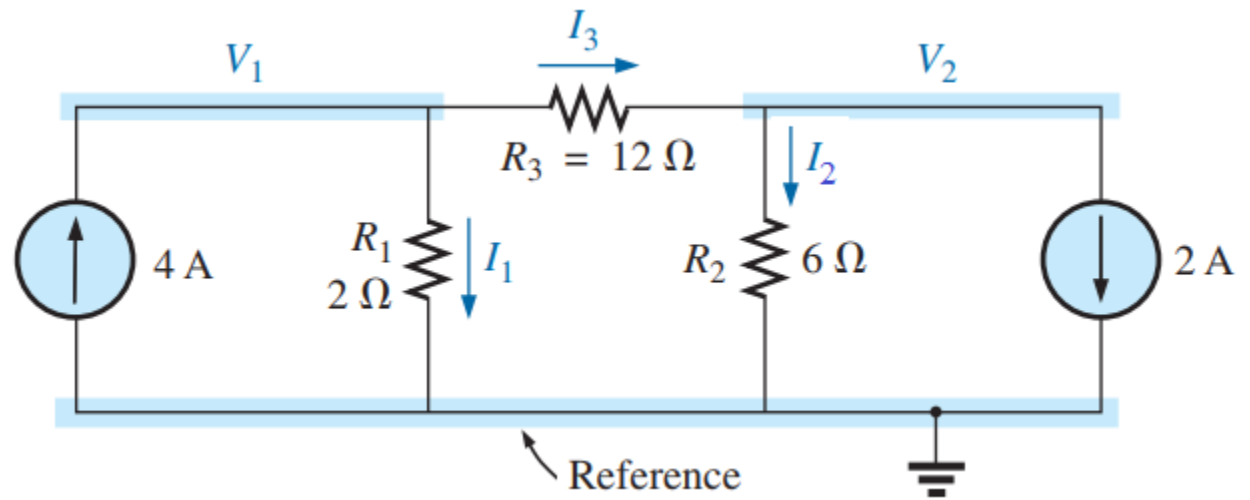
$$V_2 = \frac{D_2}{D} = \frac{-120}{20} = \mathbf{-6 \text{ V}}$$



Here, $V_1 > V_2$

$$I_{R_1} = \frac{V_{R_1}}{R_1} = \frac{V_1}{R_1} = \frac{6 \text{ V}}{2 \Omega} = \mathbf{3 \text{ A}}$$

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{V_2}{R_2} = \frac{6 \text{ V}}{6 \Omega} = \mathbf{1 \text{ A}}$$

$$I_{R_3} = \frac{V_1 - V_2}{R_3} = \frac{6 \text{ V} - (-6 \text{ V})}{12 \Omega} = \frac{12 \text{ V}}{12 \Omega} = \mathbf{1 \text{ A}}$$

EXAMPLE 8.24 Find the voltage across the $3\ \Omega$ resistor in Fig. 8.61 by nodal analysis.


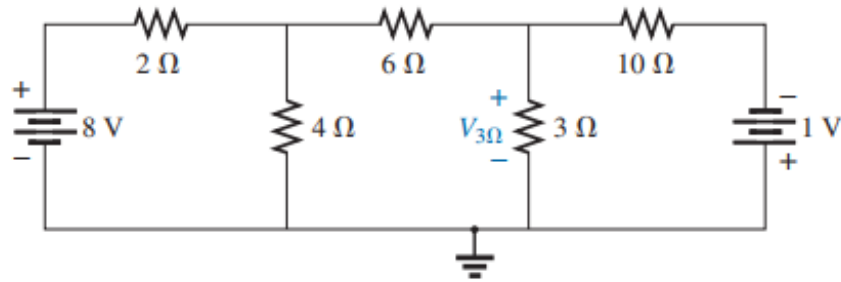


FIG. 8.61 Example 8.24.

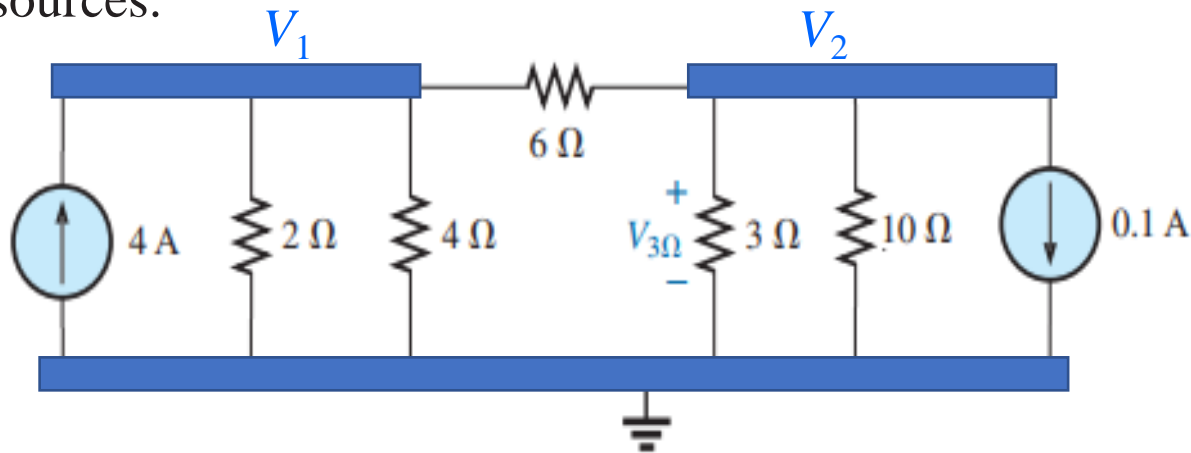Solution: First convert two voltage sources to current sources.



Step 1 and 2: The network has three nodes with the bottom node defined as the reference node (at ground potential, or zero volts), and the other nodes as V_1 and V_2 .

Step 3: For node V_1 , the currents are defined as shown in the following Figure (b) and Kirchhoff's current law is applied:

$$\left(\frac{1}{2} + \frac{1}{4} + \frac{1}{6}\right)V_1 - \left(\frac{1}{6}\right)V_2 = 4 \quad 11V_1 - 2V_2 = 48$$

For node V_2 :

$$\left(\frac{1}{6} + \frac{1}{3} + \frac{1}{10}\right)V_2 - \left(\frac{1}{6}\right)V_1 = -0.1 \quad 18V_2 - 5V_1 = -3$$

Simplified form:

$$11V_1 - 2V_2 = 48$$

$$-5V_1 + 18V_2 = -3$$

$$D = \begin{vmatrix} 11 & -2 \\ -5 & 18 \end{vmatrix} = 198 - 10 = 188$$

$$11V_1 - 2V_2 = 48$$


$$-5V_1 + 18V_2 = -3$$

$$D_1 = \begin{vmatrix} 48 & -2 \\ -3 & 18 \end{vmatrix} = 864 - 6 = 858$$

$$D_2 = \begin{vmatrix} 11 & 48 \\ -5 & -3 \end{vmatrix} = -33 + 240 = 207$$

$$V_1 = \frac{D_1}{D} = \frac{858}{188} = \mathbf{4.56 \text{ V}}$$
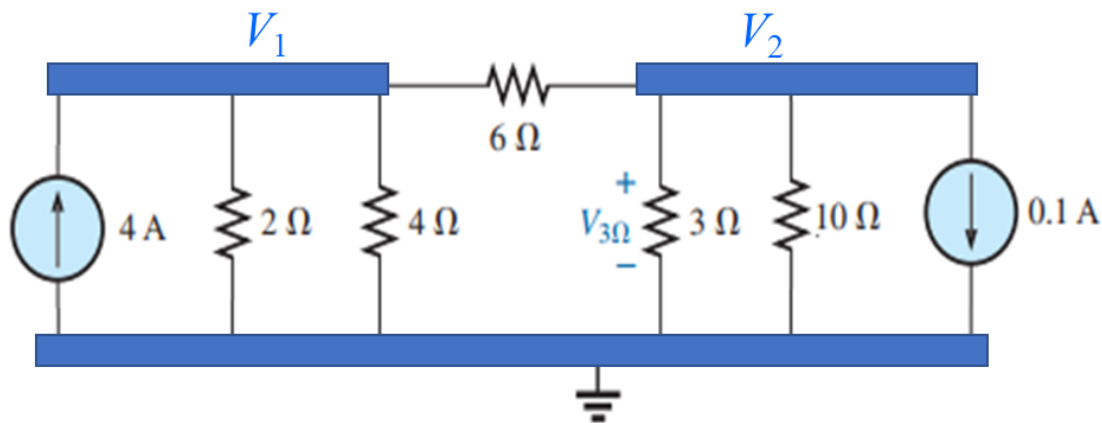
$$V_2 = V_{3\Omega} = \frac{D_2}{D} = \frac{207}{188} = \mathbf{1.1 \text{ V}}$$



Current of branches:

$$I_{2\Omega} = \frac{V_1}{2\Omega} = \frac{4.56 \text{ V}}{2\Omega} = \mathbf{2.28 \text{ A}}$$

$$I_{4\Omega} = \frac{V_1}{4\Omega} = \frac{4.56 \text{ V}}{4\Omega} = \mathbf{1.14 \text{ A}}$$


$$I_{6\Omega} = \frac{V_1 - V_2}{6\Omega} = \frac{4.56 \text{ V} - 1.1 \text{ V}}{6\Omega} = \mathbf{0.577 \text{ A}}$$

$$I_{3\Omega} = \frac{V_2}{3\Omega} = \frac{1.1 \text{ V}}{3\Omega} = \mathbf{0.367 \text{ A}}$$

$$I_{10\Omega} = \frac{V_2}{10\Omega} = \frac{1.1 \text{ V}}{10\Omega} = \mathbf{0.11 \text{ A}}$$

Write the nodal equations for the following networks.

Practice Book [Ch 8] Problem: 41 ~ 44

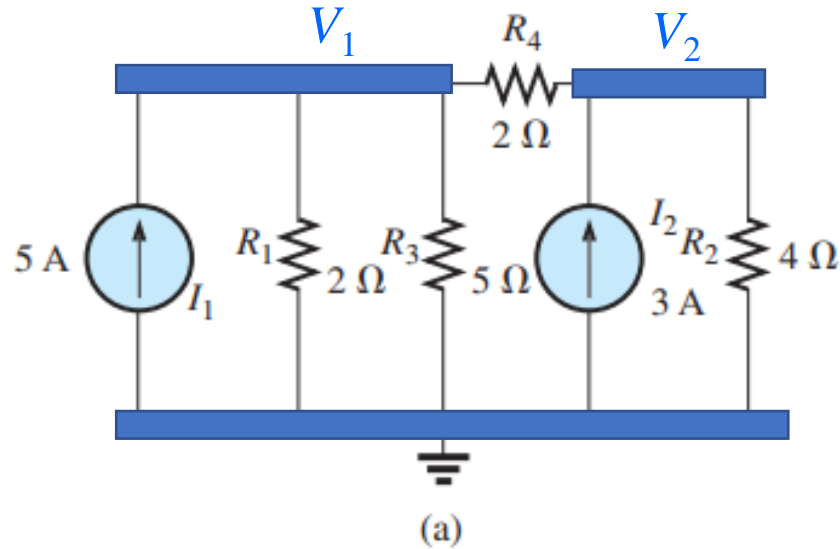


$$\left(\frac{1}{2} + \frac{1}{5} + \frac{1}{2}\right)V_1 - \left(\frac{1}{2}\right)V_2 = 5$$

$$\left(\frac{5+2+5}{10}\right)V_1 - \left(\frac{1}{2}\right)V_2 = 5 \quad 12V_1 - 5V_2 = 50$$

$$\left(\frac{1}{2} + \frac{1}{4}\right)V_2 - \left(\frac{1}{2}\right)V_1 = 3$$
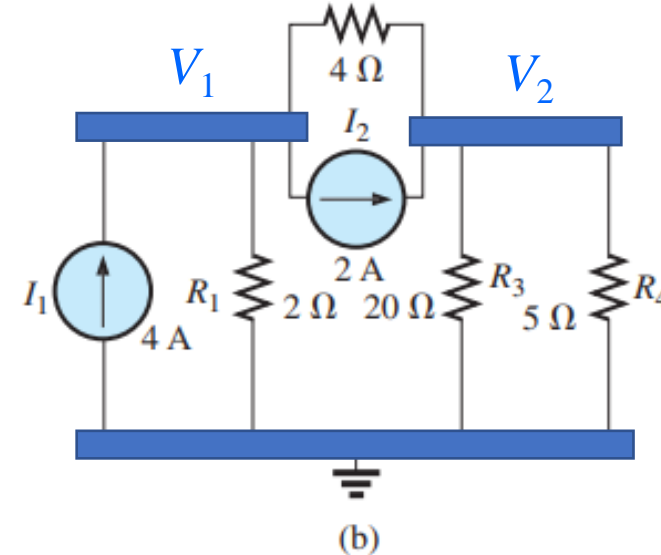
$$\left(\frac{2+1}{4}\right)V_2 - \left(\frac{1}{2}\right)V_1 = 3 \quad 3V_2 - 2V_1 = 6$$



$$\left(\frac{1}{2} + \frac{1}{4}\right)V_1 - \left(\frac{1}{4}\right)V_2 = 4 - 2$$

$$\left(\frac{2+1}{4}\right)V_1 - \left(\frac{1}{4}\right)V_2 = 2 \quad 3V_1 - V_2 = 8$$





$$\left(\frac{1}{4} + \frac{1}{20} + \frac{1}{5}\right)V_2 - \left(\frac{1}{4}\right)V_1 = 2$$

$$\left(\frac{5+1+4}{20}\right)V_2 - \left(\frac{1}{4}\right)V_1 = 2 \quad 10V_2 - 5V_1 = 40$$





8.12 Y– Δ (T– Π) and Δ –Y (Π –T) CONVERSIONS

Circuit configurations are often encountered in which the resistors do **not appear to be in series or parallel**. Under these conditions, it may be necessary to convert the circuit from one form to another [*i.e.* convert from **Y/T** to **Δ/Π** **or** **Δ/Π** to **Y/T**] to solve for any unknown quantities




Y (Wye)

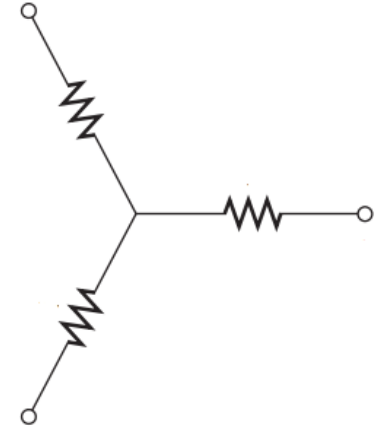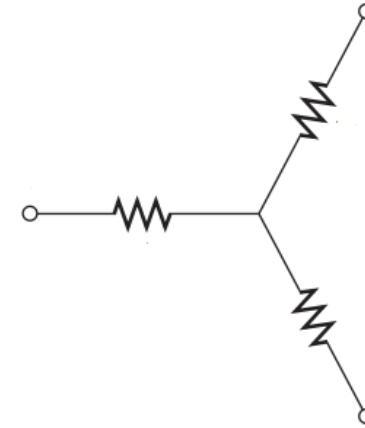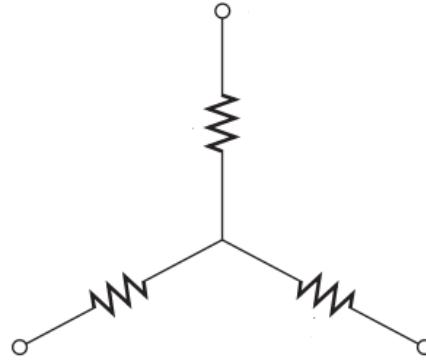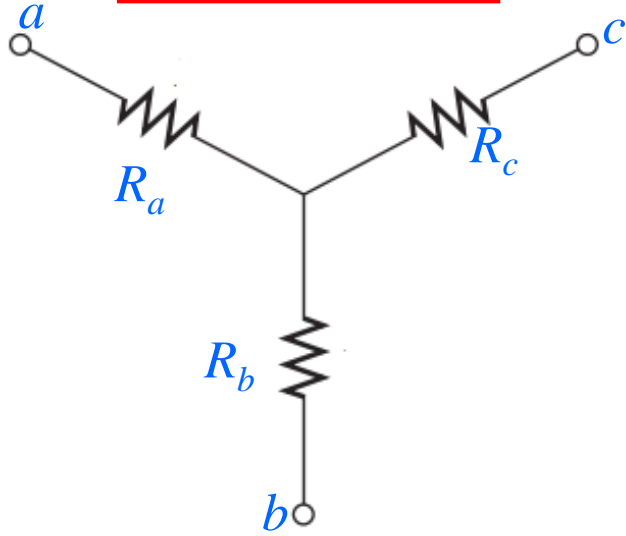





T (Tee)

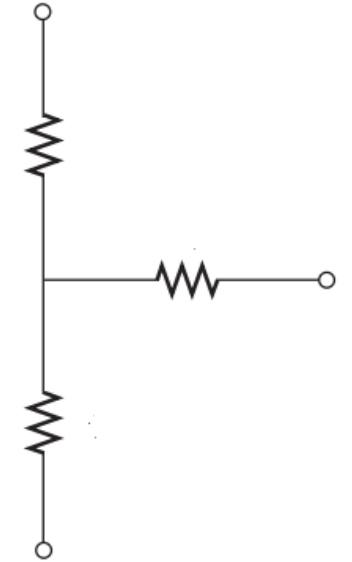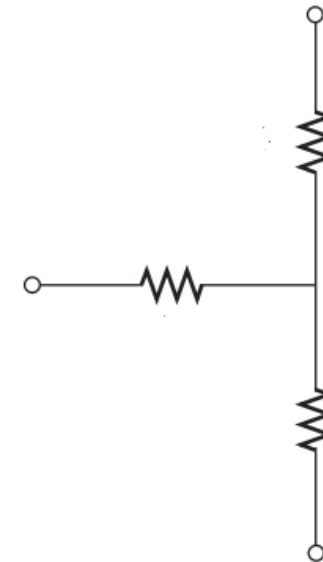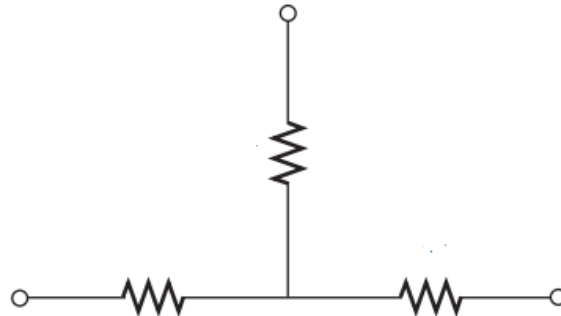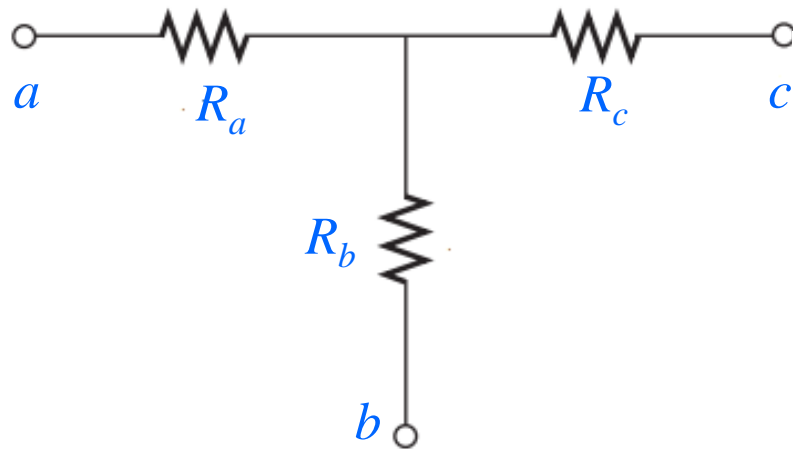


Δ (Delta)

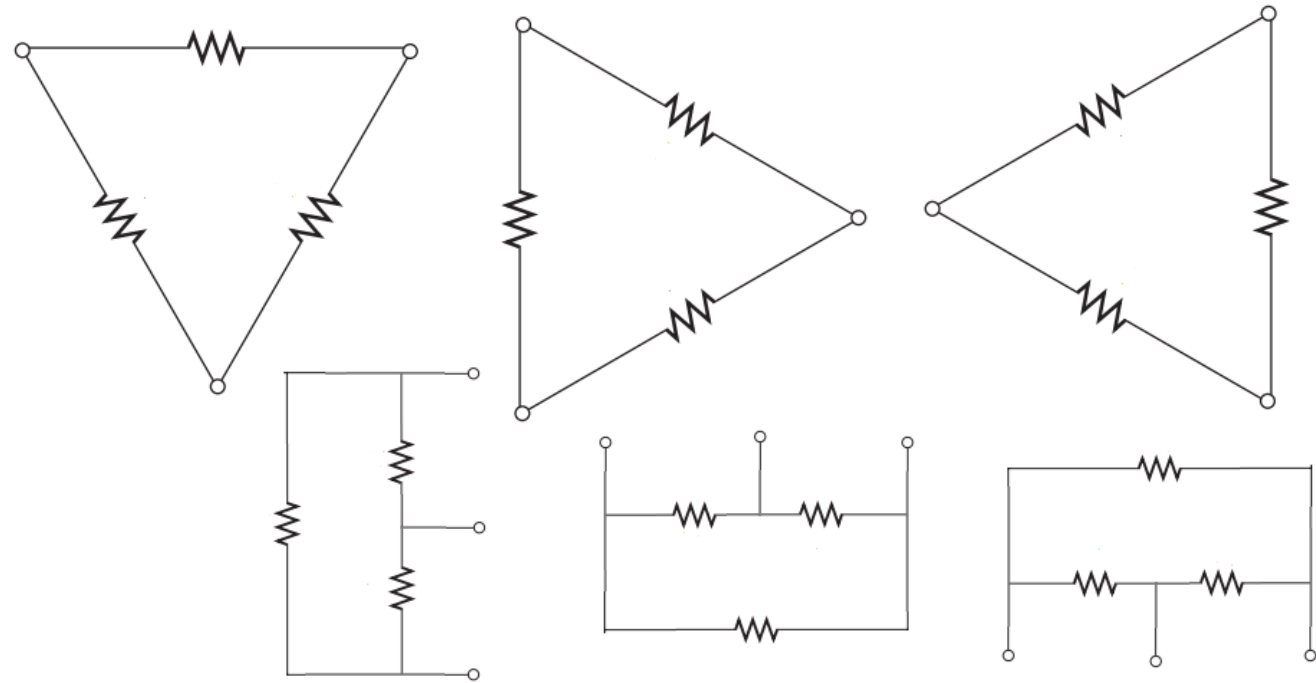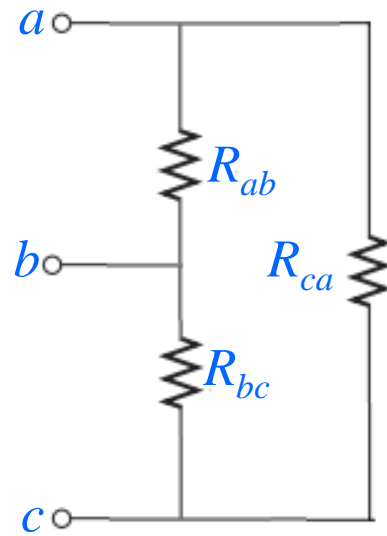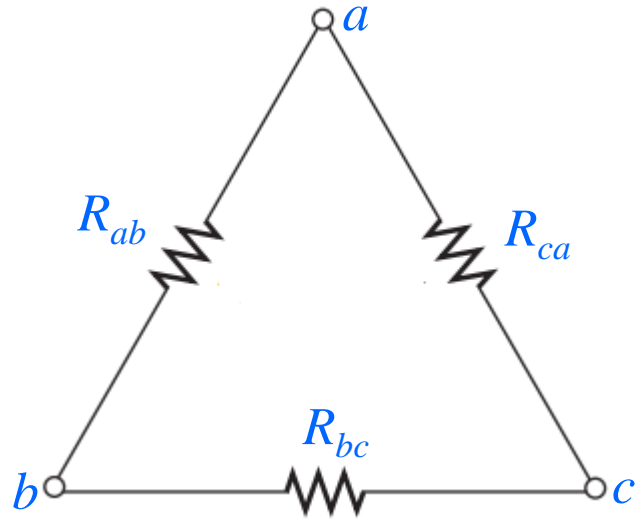

Π (Pai)

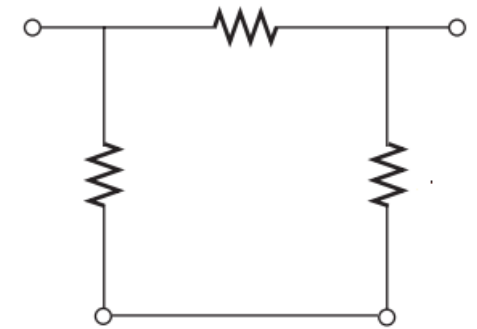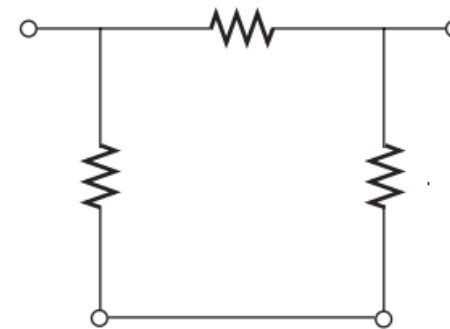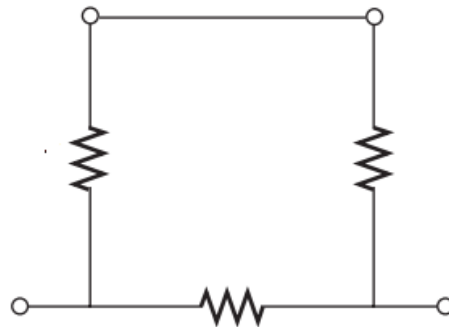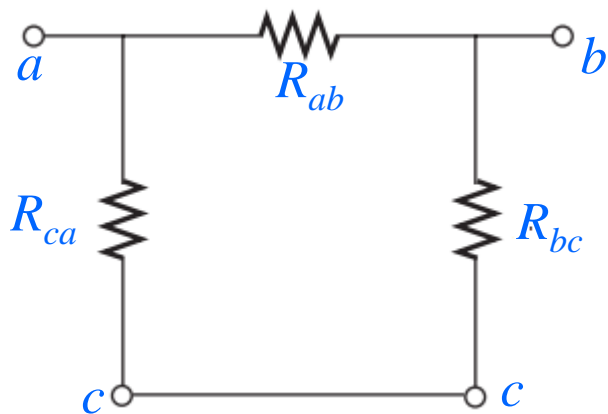

Conversion from Y (T) to Δ (Π)

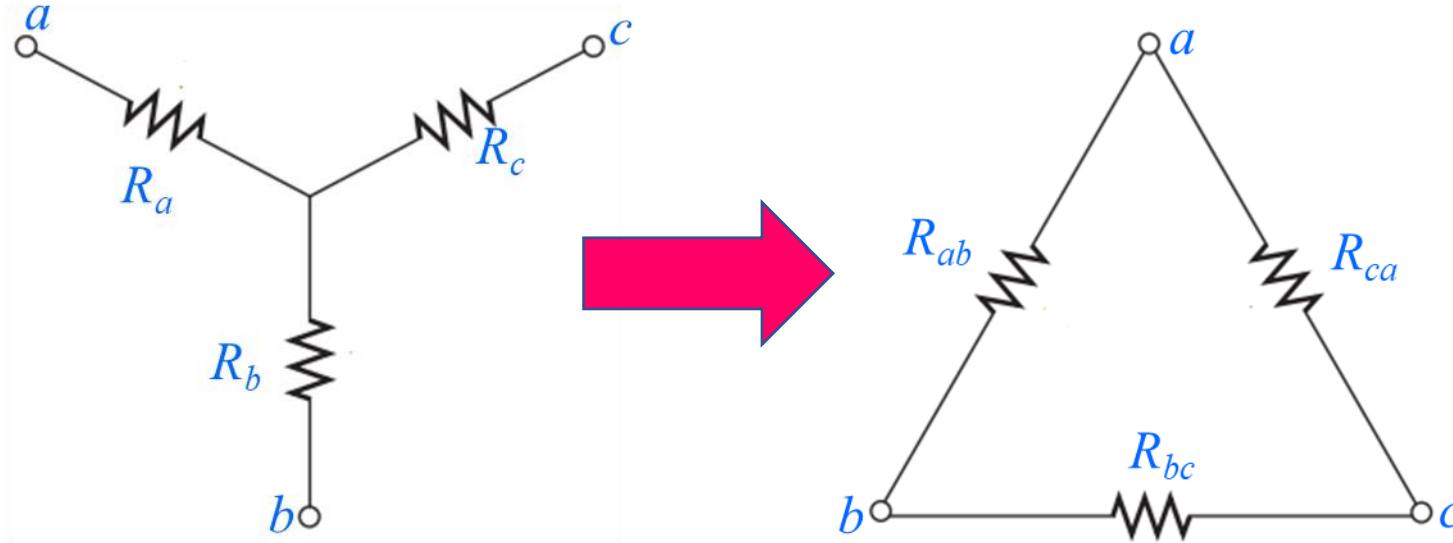

Here, R_a , R_b and R_c are known.

If $R_a = R_b = R_c = R_Y$ then $R_{ab} = R_{bc} = R_{ca} = R_{\Delta} = 3R_Y$

Calculate R_{ab} , R_{bc} and R_{ca}

$$R_{abc} = R_a R_b + R_b R_c + R_c R_a$$


$$R_{ab} = \frac{R_{abc}}{R_c} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

$$R_{bc} = \frac{R_{abc}}{R_a} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$$R_{ca} = \frac{R_{abc}}{R_b} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

For derivation of these equations go through Eq. (8.3a) to (8.4 c)

Conversion from Δ (Π) to Y (T)

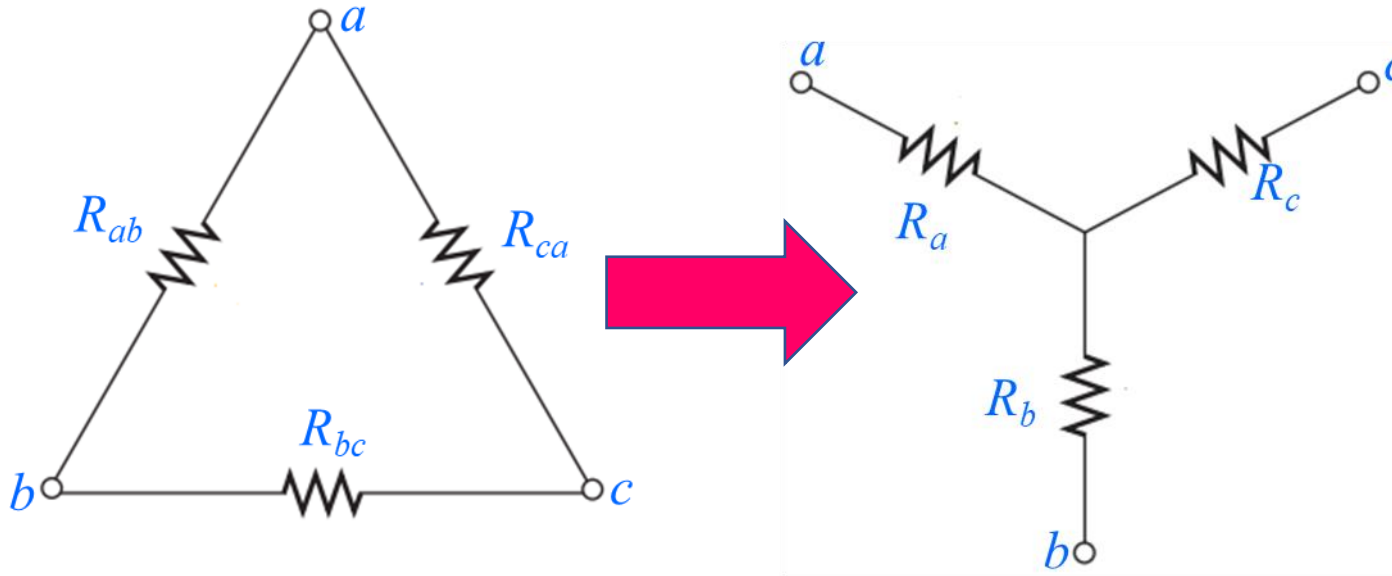

Here, R_{ab} , R_{bc} and R_{ca} are known.

Calculate R_a , R_b and R_c

$$R_{abc} = R_{ab} + R_{bc} + R_{ca}$$

$$R_a = \frac{R_{ab}R_{ca}}{R_{abc}} = \frac{R_{ab}R_{ca}}{R_{ab} + R_{bc} + R_{ca}}$$


$$R_b = \frac{R_{bc}R_{ab}}{R_{abc}} = \frac{R_{bc}R_{ab}}{R_{ab} + R_{bc} + R_{ca}}$$

$$R_c = \frac{R_{ca}R_{bc}}{R_{abc}} = \frac{R_{ca}R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$$

If $R_{ab} = R_{bc} = R_{ca} = R_{\Delta}$ then $R_{ab} = R_{bc} = R_{ca} = R_Y = \frac{R_{\Delta}}{3}$

For derivation of these equations go through Eq. (8.5a) to (8.5c)

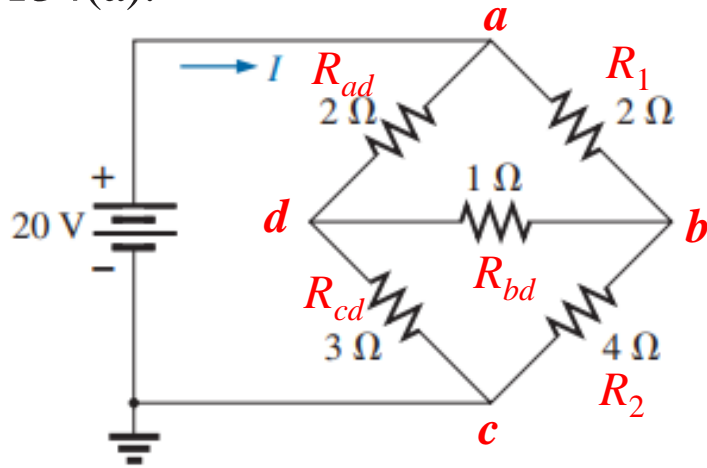Problem 51(a) [P. 342]. Using a Δ -Y or Y- Δ conversion, find the current I in each of the networks in Fig. 8.134(a).



Solution: First, marked four nodes (a , b , c , and d) in the circuit.

Let, $R_{ad} = 2\ \Omega$, $R_{bd} = 1\ \Omega$, $R_{cd} = 3\ \Omega$, $R_1 = 2\ \Omega$, and $R_2 = 4\ \Omega$


Here, R_{ad} , R_{bd} , and R_{cd} made Y connection where d is common point. So, this Y connection is going to convert Δ connection.

$$\begin{aligned} R_{abc} &= R_{ad}R_{bd} + R_{bd}R_{cd} + R_{cd}R_{ad} \\ &= (2\Omega)(1\Omega) + (1\Omega)(3\Omega) + (3\Omega)(2\Omega) \\ &= 2\Omega + 3\Omega + 6\Omega = 11\Omega \end{aligned}$$

$$R_{ab} = \frac{R_{abc}}{R_{cd}} = \frac{11\Omega}{3\Omega} = 3.67\Omega$$

$$R_{bc} = \frac{R_{abc}}{R_{ad}} = \frac{11\Omega}{2\Omega} = 5.5\Omega$$

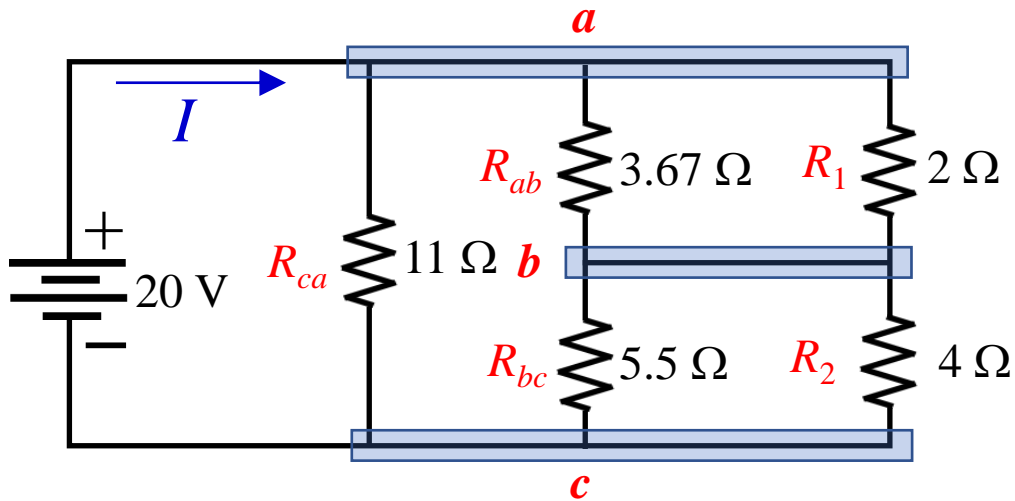
$$R_{ca} = \frac{R_{abc}}{R_{bd}} = \frac{11\Omega}{1\Omega} = 11\Omega$$



$$\begin{aligned}
 R_T &= (R_{ca}) // \{ (R_{ab} // R_1) + (R_{bc} // R_2) \} \\
 &= (11\ \Omega) // \{ (3.67\ \Omega // 2\ \Omega) + (5.5\ \Omega // 4\ \Omega) \} \\
 &= (11\ \Omega) // \{ 1.29\ \Omega + 2.32\ \Omega \} \\
 &= (11\ \Omega) // \{ 3.61\ \Omega \} \\
 &= 2.72\ \Omega
 \end{aligned}$$

$$I = \frac{E}{R_T} = \frac{20\text{ V}}{2.72\ \Omega} = 7.35\text{ V}$$

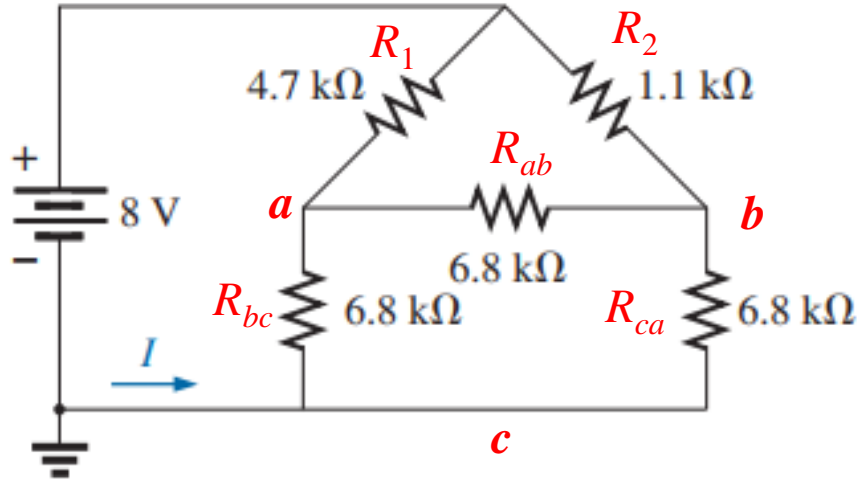Problem 51(b) [P. 342]. Using a Δ -Y or Y- Δ conversion, find the current I in each of the networks in Fig. 8.134(b).




Solution: First, marked four nodes (a , b , and c) in the circuit.


Let, $R_1=4.7 \text{ k}\Omega$, $R_2=1.1 \text{ k}\Omega$, $R_{ab}=R_{bc}=R_{ca}= 6.8 \text{ k}\Omega$

Here, R_{ab} , R_{bc} , and R_{ca} made Δ connection. So, this Δ connection is going to convert Y connection.

Here, $R_{ab} = R_{bc} = R_{ca} = R_{\Delta} = 6.8 \text{ k}\Omega$
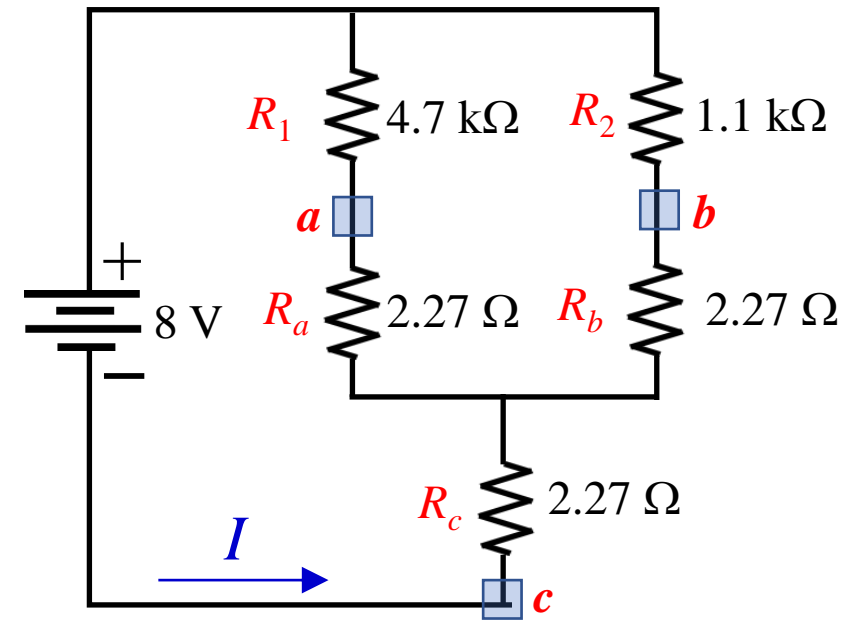
$$\text{so, } R_a = R_b = R_c = R_Y = \frac{R_{\Delta}}{3} \\ = \frac{6.8 \text{ k}\Omega}{3} = 2.27 \text{ k}\Omega$$



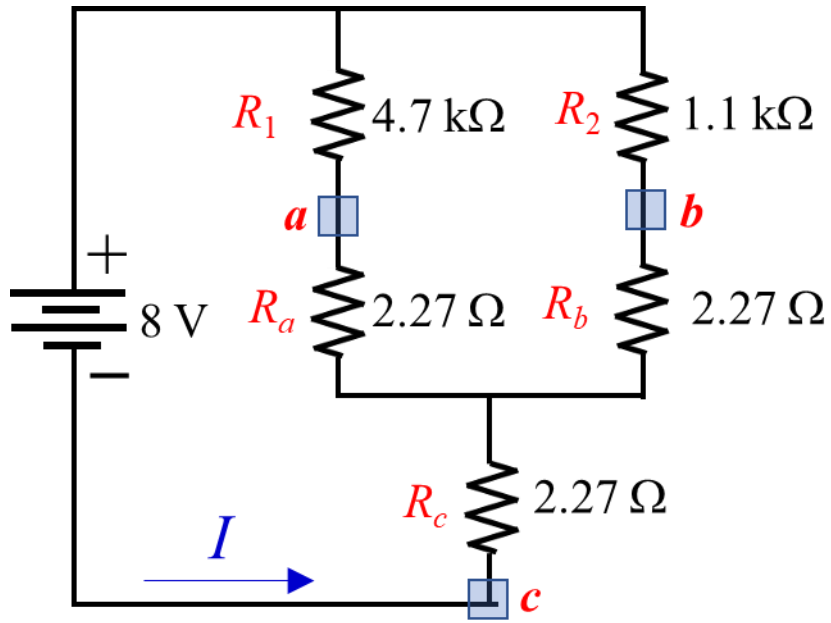

$$\begin{aligned}
 R_T &= [(R_1 + R_a) // (R_2 + R_b)] + R_c \\
 &= [(4.7\text{k}\Omega + 2.27\text{k}\Omega) // (1.1\text{k}\Omega + 2.27\text{k}\Omega)] + 2.27\text{k}\Omega \\
 &= [(6.97\text{k}\Omega) // (3.37\text{k}\Omega)] + 2.27\text{k}\Omega \\
 &= 2.27\text{k}\Omega + 2.27\text{k}\Omega \\
 &= 4.54\text{k}\Omega
 \end{aligned}$$

$$I = \frac{E}{R_T} = \frac{8\text{ V}}{4.54\text{ k}\Omega} = 1.76\text{ mA}$$

Practice Book [Ch 8] Problem: 51 ~ 56

8.11 BRIDGE NETWORKS


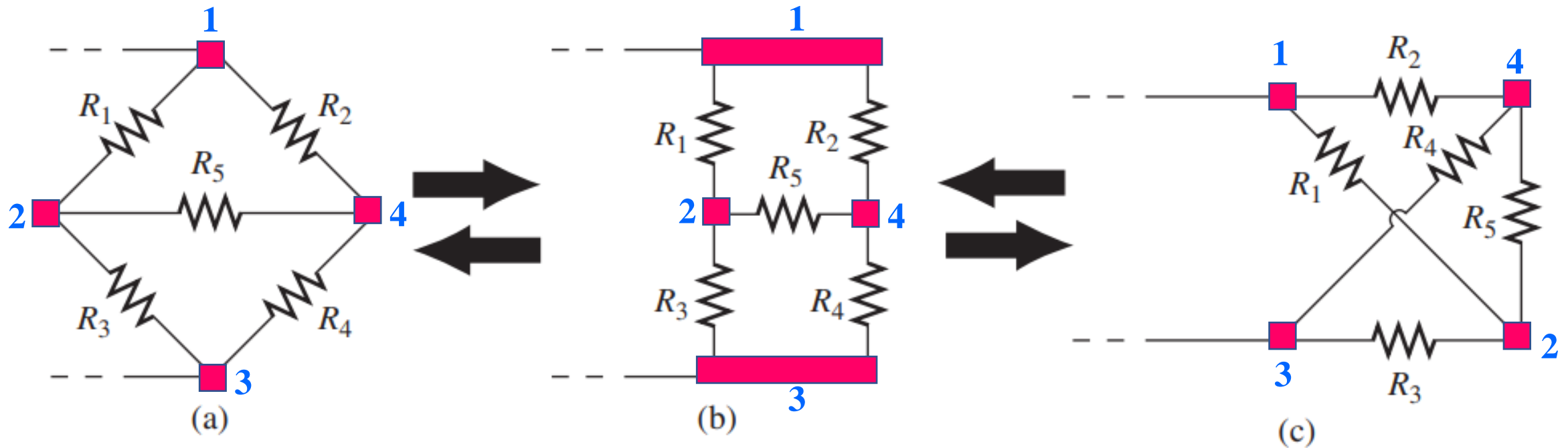


FIG. 8.69 Various formats for a bridge network.


Balanced Bridge Network

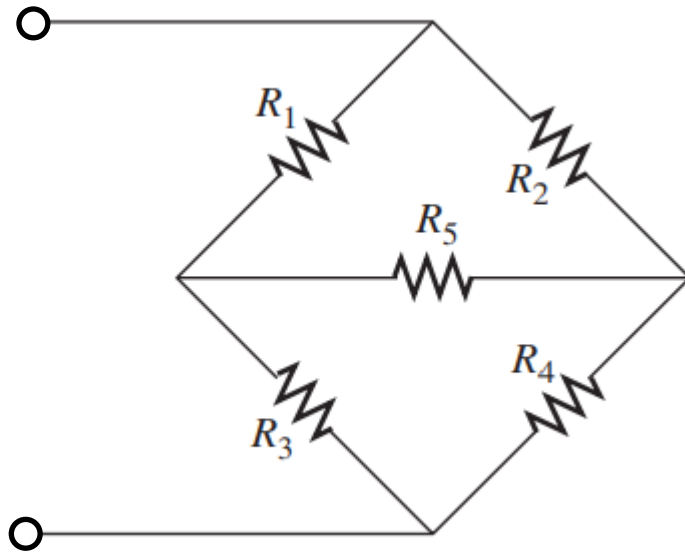

If the ratio of R_1 to R_3 is equal to that of R_2 to R_4 , the bridge is balanced, and $I = 0$ A or $V = 0$ V.

$$\frac{R_1}{R_3} = \frac{R_2}{R_4}$$




(8.2)

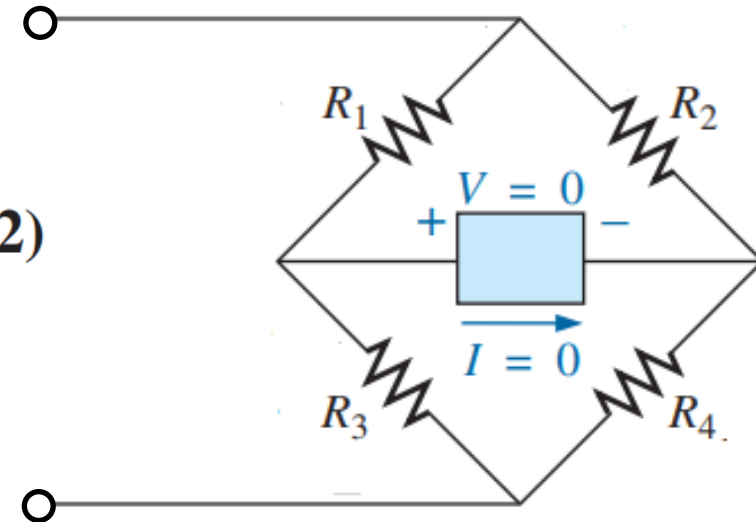

If this condition is not satisfied, to solve the bridge circuit use the other techniques.

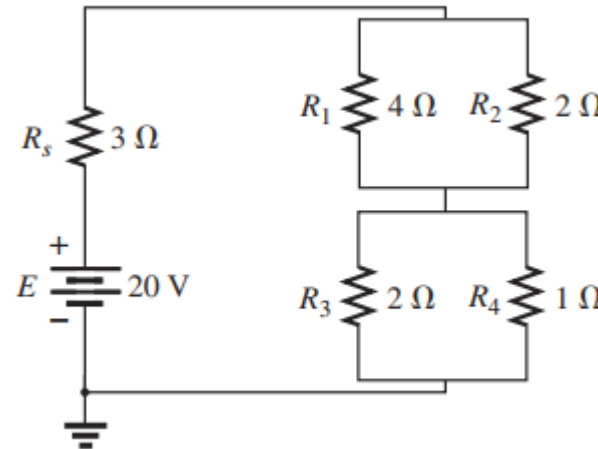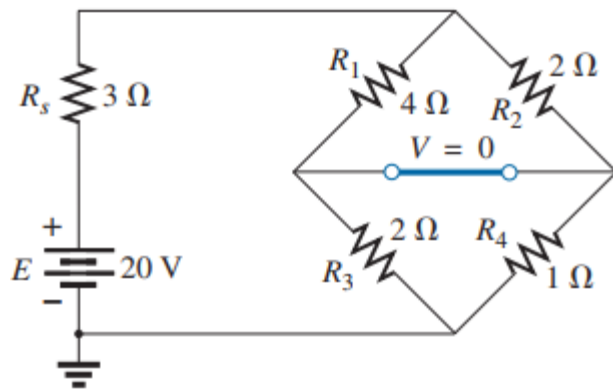
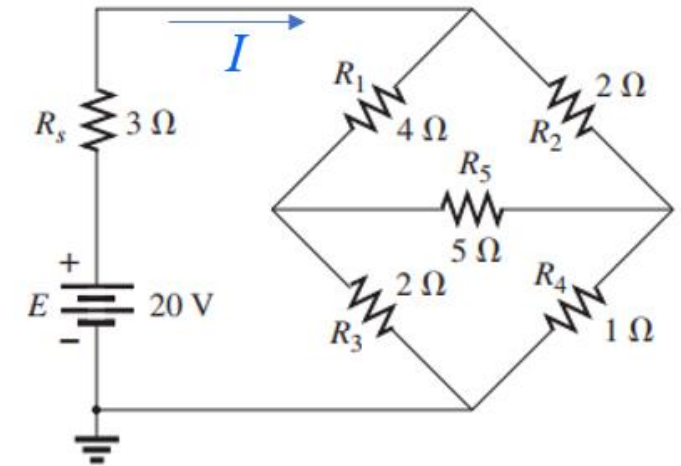
Example 8.11.1: Find the current I for the following network.

Solution: Here: $\frac{R_1}{R_3} = \frac{4\Omega}{2\Omega} = 2$ and $\frac{R_2}{R_4} = \frac{2\Omega}{1\Omega} = 2$ so $\frac{R_1}{R_3} = \frac{R_2}{R_4}$



$$R_T = 3\Omega + (4\Omega // 2\Omega) + (2\Omega // 1\Omega) = 5\Omega$$
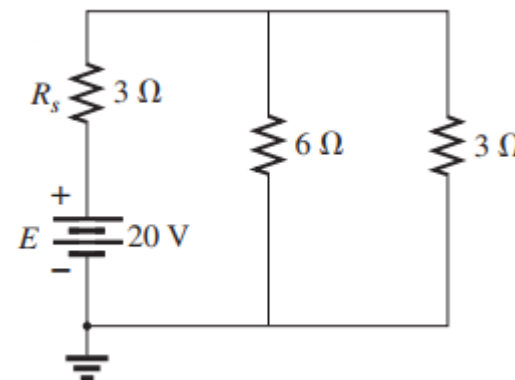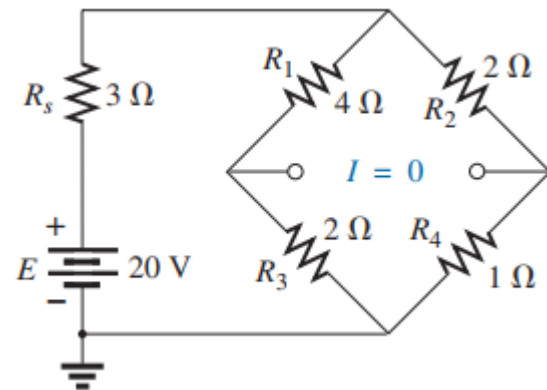
$$I = \frac{E}{R_T} = \frac{20\text{ V}}{5\Omega} = 4\text{ A}$$



$$R_T = 3\Omega + (6\Omega // 3\Omega) = 5\Omega$$

$$I = \frac{E}{R_T} = \frac{20\text{ V}}{5\Omega} = 4\text{ A}$$

Chapter 9

Network Theorems (DC)




9.2 SUPERPOSITION THEOREM

Statement of Superposition Theorem

The current through, or voltage across, an element in a linear bilateral network is equal to the algebraic sum of the currents or voltages produced independently by each source.


Steps to Apply Superposition Theorem

- Step 1:** Select a single source acting alone. **Short the other voltage sources to make voltage is zero** and **open the current sources to make current is zero**, if internal impedances are not known. If known, replace them by their internal impedances.
- Step 2:** Find the current through or the voltage across the required element, due to the source under consideration, using a suitable simplification technique.
- Step 3:** Repeat the above two steps for all the sources.
- Step 4:** Add all the individual effects produced by individual sources, to obtain the total current in or voltage across the element.

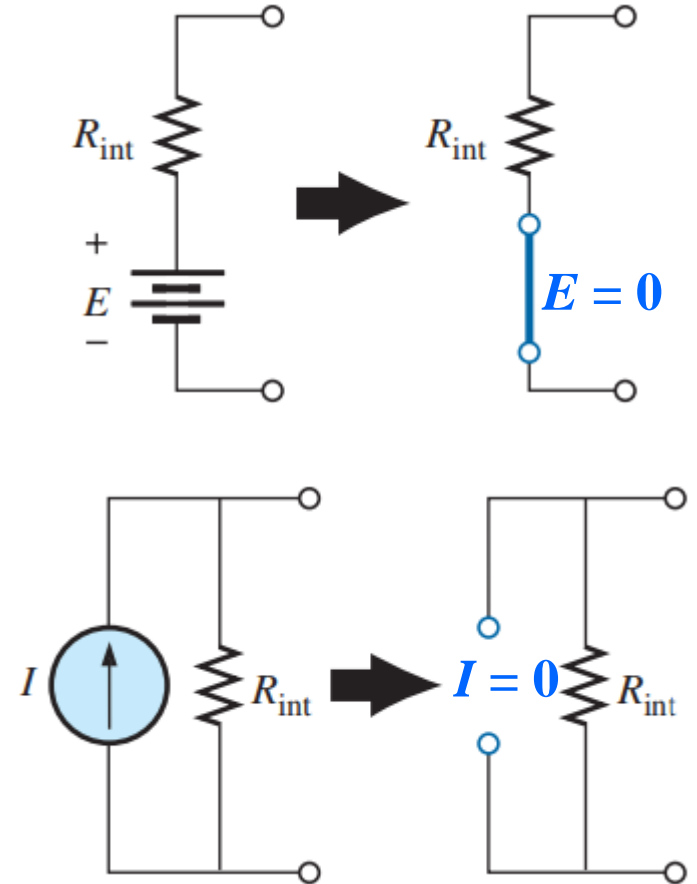

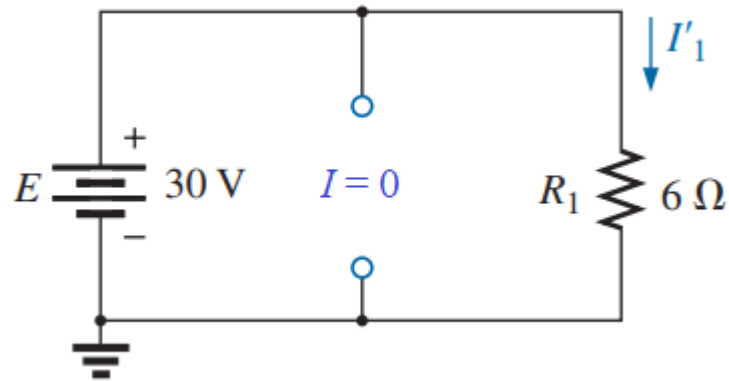
EXAMPLE 9.1 Using the superposition theorem, determine current I_1 for the network in Fig. 9.2.

Solution: Consider E then and $I = 0$ A (**open**).



$$I'_1 = \frac{E}{R_1} = \frac{30 \text{ V}}{6 \Omega} = 5 \text{ A}$$

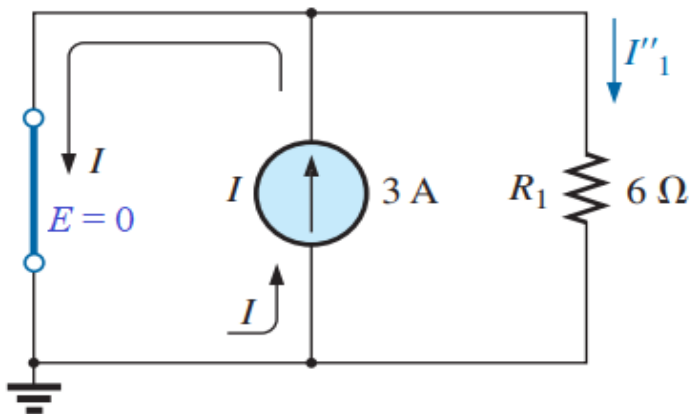Consider I then and $E = 0$ V (**shorted**).



$$I''_1 = \frac{R_{sc} I}{R_{sc} + R_1} = \frac{(0 \Omega) I}{0 \Omega + 6 \Omega} = 0 \text{ A}$$

According to Superposition Theorem:

$$I_1 = I'_1 + I''_1 = 5 \text{ A} + 0 \text{ A} = 5 \text{ A}$$

